

THE No 1 UK MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EPE EVERYDAY PRACTICAL ELECTRONICS

www.epemag.com

DELUXE 3-CHANNEL UHF ROLLING CODE REMOTE CONTROL


High-security UHF transmitter/receiver for keyless entry, garage door or lighting control



**WIN A
MICROCHIP
MPLAB
Starter Kit**

SD CARD MUSIC & SPEECH RECORDER/PLAYER

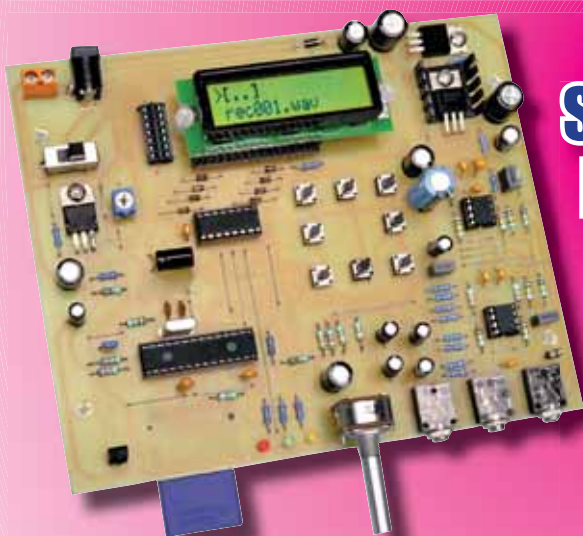- Free-standing recorder, or works with Windows, Mac or Linux PC
- Use as a jukebox or sound effects player



INPUT ATTENUATOR FOR THE DIGITAL AUDIO MILLIVOLTMETER

An add-on project for measuring AC voltages to 140V RMS



PLUS

TEACH-IN 2011 – PART 10
Construction and testing

\$8.99US £4.25UK
AUGUST 2011 PRINTED IN THE UK



Low-Power Microcontrollers for Battery-Friendly Design

Microchip Offers Lowest Currents for Active and Sleep Modes



Extend the battery life in your application using PIC® microcontrollers with nanoWatt XLP Technology and get the industry's lowest currents for Active and Sleep modes.

Microchip's new peripheral-rich PIC12F182X, PIC16F182X and PIC16F19XX families offer active currents of less than 50 μ A and sleep currents down to 20 nA. These products enable you to create battery-friendly designs that also incorporate capacitive touch sensing, LCD, communications and other functions which help differentiate your products in the marketplace.

Microchip's Enhanced Mid-range 8-bit architecture provides up to 50% increased performance and 14 new instructions that result in up to 40% better code execution over previous-generation 8-bit PIC16 MCUs.

PIC12F182X and PIC16F182X families include:

- Packages ranging from 8 to 64 pins
- mTouch™ capacitive touch-sensing
- Multiple communications peripherals
- Dual I²C™/SPI interfaces
- PWM outputs with independent time bases
- Data signal modulator

PIC16F19XX family includes:

- mTouch capacitive touch-sensing
- LCD drive
- Multiple communications peripherals
- More PWM channels, with independent timers
- Up to 28 KB of Flash program memory
- Enhanced data EEPROM
- 32-level bandgap reference
- Three rail-to-rail input comparators

GET STARTED IN 3 EASY STEPS

1. View the Low Power Comparison videos
2. Download the Low Power Tips 'n Tricks
3. Order samples and development tools

www.microchip.com/XLP




PIC16F193X 'F1' Evaluation Platform - DM164130-1

Intelligent Electronics start with Microchip

microchip
DIRECT
www.microchipdirect.com

www.microchip.com/xlp

 **MICROCHIP**

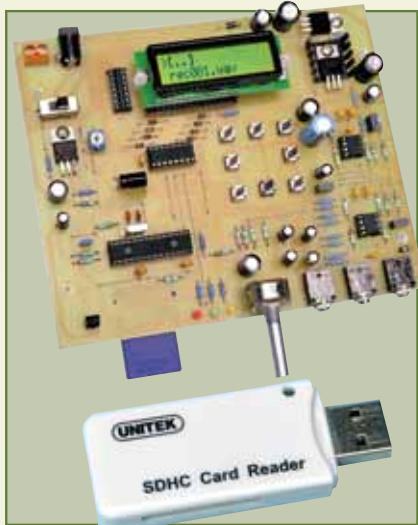

© Wimborne Publishing Ltd 2011. Copyright in all drawings, photographs and articles published in *EVERYDAY PRACTICAL ELECTRONICS* is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our September 2011 issue will be published on Thursday 11 August 2011, see page 80 for details.

Everyday Practical Electronics, August 2011

Projects and Circuits

- SD CARD MUSIC AND SPEECH RECORDER/PLAYER** By Mauro Grassi **10**
Store WAV files on SD cards – standalone, or on any Windows, Mac or Linux PC
- INPUT ATTENUATOR FOR THE DIGITAL AUDIO MILLIVOLTMETER** **26**
by Jim Rowe
Use our Digital Audio Millivoltmeter to measure AC voltages up to 140V RMS
- DELUXE 3-CHANNEL UHF ROLLING CODE REMOTE CONTROL – PART 1** by John Clarke **30**
High-security UHF system for keyless entry, garage door control and external lighting

Series and Features

- TECHNO TALK** by Mark Nelson **24**
The coming revolution
- TEACH-IN 2011** by Mike and Richard Tooley **42**
Part 10: Electronic circuit construction and testing
- PIC N' MIX** by Mike Hibbett **56**
MPLAB-X
- CIRCUIT SURGERY** by Ian Bell **60**
What's all this noise about?
- INTERFACE** by Robert Penfold **64**
Long-lived converters
- MAX'S COOL BEANS** by Max The Magnificent **68**
Interesting times... Tornado warning...
- NET WORK** by Alan Winstanley **74**
Mobile content is king... 2D or not 2D...

Regulars and Services

- EDITORIAL** **7**
How safe are your digits?
- NEWS** – Barry Fox highlights technology's leading edge **8**
Plus everyday news from the world of electronics
- SUBSCRIBE TO EPE** and save money **25**
- EPE BACK ISSUES CD-ROM** Did you miss these? **40**
- MICROCHIP READER OFFER** **41**
EPE Exclusive – Win a Microchip MPLAB Starter Kit For PIC24H MCUs
- EPE BACK ISSUES** Did you miss these? **59**
- CD-ROMS FOR ELECTRONICS** **69**
A wide range of CD-ROMs for hobbyists, students and engineers
- READOUT** – Matt Pulzer addresses general points arising **72**
- DIRECT BOOK SERVICE** **75**
A wide range of technical books available by mail order, plus more CD-ROMs
- EPE PCB SERVICE** **78**
PCBs for *EPE* projects
- ADVERTISERS INDEX** **79**

Copyright © 2010, Wimborne Publishing Ltd
(Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU, UK)
and TechBites Interactive Inc.,
(PO Box 857, Madison, Alabama 35758, USA)
All rights reserved.

WARNING!

The materials and works contained within *EPE Online* — which are made available by Wimborne Publishing Ltd and TechBites Interactive Inc — are copyrighted. You are permitted to make a backup copy of the downloaded file and one (1) hard copy of such materials and works for your personal use.

International copyright laws, however, prohibit any further copying or reproduction of such materials and works, or any republication of any kind. TechBites Interactive Inc and Wimborne Publishing Ltd have used their best efforts in preparing these materials and works. However, TechBites Interactive Inc and Wimborne Publishing Ltd make no warranties of any kind, expressed or implied, with regard to the documentation or data contained herein, and specifically disclaim, without limitation, any implied warranties of merchantability and fitness for a particular purpose. Because of possible variances in the quality and condition of materials and workmanship used by readers, *EPE Online*, its publishers and agents disclaim any responsibility for the safe and proper functioning of reader-constructed projects based on or from information published in these materials and works. In no event shall TechBites Interactive Inc or Wimborne Publishing Ltd be responsible or liable for any loss of profit or any other commercial damages, including but not limited to special, incidental, consequential, or any other damages in connection with or arising out of furnishing, performance, or use of these materials and works.

01279

**Credit Card
Sales**

467799

PIC & ATMEL Programmings

We have a wide range of low cost PIC and ATMEL Programmings. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £14.95
18Vdc Power supply (PSU121) £24.95
Leads: Parallel (LDC136) £3.95 / Serial (LDC441) £3.95 / USB (LDC644) £2.95

USB & Serial Port PIC Programmer

USB/Serial connection. Header cable for ICSP. Free Windows XP software. See website for PICs supported. ZIF Socket and USB lead extra. 18Vdc.

Kit Order Code: 3149EKT - £49.95
Assembled Order Code: AS3149E - £59.95

Assembled with ZIF socket Order Code: AS3149EZIF - £74.95

USB Flash/OTP PIC Programmer

USB PIC programmer for a wide range of Flash & OTP devices—see website for details. Free Windows Software. ZIF Socket and USB lead not included. Supply: 16-18Vdc.

Assembled Order Code: AS3150 - £49.95
Assembled with ZIF socket Order Code: AS3150ZIF - £64.95

ATMEL 89xxx Programmer

Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16Vdc.

Kit Order Code: 3123KT - £28.95
Assembled Order Code: AS3123 - £39.95

Introduction to PIC Programming

Go from complete beginner to burning a PIC and writing code in no time! Includes 49 page step-by-step PDF Tutorial Manual, Programming Hardware (with LED test section), Win 3.11—XP Programming Software (Program, Read, Verify & Erase), and 1rewritable PIC16F84A that you can use with different code (4 detailed examples provided for you to learn from). PC parallel port. Kit Order Code: 3081KT - £16.95
Assembled Order Code: AS3081 - £24.95

PIC Programmer Board

Low cost PIC programmer board supporting a wide range of Microchip® PIC™ microcontrollers. Requires PC serial port. Windows interface supplied. Kit Order Code: K8076KT - £39.95

PIC Programmer & Experimenter Board

The PIC Programmer & Experimenter Board with test buttons and LED indicators to carry out educational experiments, such as the supplied programming examples. Includes a 16F627 Flash Microcontroller that can be reprogrammed up to 1000 times for experimenting at will. Software to compile and program your source code is included. Kit Order Code: K8048KT - £39.95

Assembled Order Code: VM111 - £59.95



Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. 12Vdc PSU for all units: Order Code PSU303 £9.95

USB Experiment Interface Board

5 digital input channels and 8 digital output channels plus two analogue inputs and two analogue outputs with 8 bit resolution.

Kit Order Code: K8055KT - £39.95
Assembled Order Code: VM110 - £64.95



Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two & Ten Channel versions also available. Kit Order Code: 3180KT - £54.95
Assembled Order Code: AS3180 - £64.95



Computer Temperature Data Logger

Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor. Kit Order Code: 3145KT - £24.95
Assembled Order Code: AS3145 - £31.95
Additional DS1820 Sensors - £4.95 each



Remote Control Via GSM Mobile Phone

Place next to a mobile phone (not included). Allows toggle or auto-timer control of 3A mains rated output relay from any location with GSM coverage. Kit Order Code: MK160KT - £14.95



Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).

4-Ch DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12Vdc.

Kit Order Code: 3140KT - £79.95

Assembled Order Code: AS3140 - £94.95



8-Ch Serial Port Isolated I/O Relay Module

Computer controlled 8 channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130x100x30mm. Power: 12Vdc/500mA. Kit Order Code: 3108KT - £74.95

Assembled Order Code: AS3108 - £89.95



Infrared RC 12-Channel Relay Board

Control 12 onboard relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm. Supply: 12Vdc/0.5A

Kit Order Code: 3142KT - £64.95
Assembled Order Code: AS3142 - £74.95



Audio DTMF Decoder and Display

Detect DTMF tones from tape recorders, receivers, two-way radios, etc using the built-in mic or direct from the phone line. Characters are displayed on a 16 character display as they are received and up to 32 numbers can be displayed by scrolling the display. All data written to the LCD is also sent to a serial output for connection to a computer. Supply: 9-12V DC (Order Code PSU303). Main PCB: 55x95mm. Kit Order Code: 3153KT - £37.95
Assembled Order Code: AS3153 - £49.95



3x5Amp RGB LED Controller with RS232

3 independent high power channels. Preprogrammed or user-editable light sequences. Standalone option and 2-wire serial interface for microcontroller or PC communication with simple command set. Suitable for common anode RGB LED strips, LEDs and incandescent bulbs. 56 x 39 x 20mm. 12A total max. Supply: 12Vdc. Kit Order Code: 3191KT - £27.95
Assembled Order Code: AS3191 - £37.95



Hot New Products!

Here are a few of the most recent products added to our range. See website or join our email Newsletter for all the latest news.

4-Channel Serial Port Temperature Monitor & Controller Relay Board

4 channel computer serial port temperature monitor and relay controller with four inputs for Dallas DS18S20 or DS18B20 digital thermometer sensors (£3.95 each). Four 5A rated relay channels provide output control. Relays are independent of sensor channels, allowing flexibility to setup the linkage in any way you choose. Commands for reading temperature and relay control sent via the RS232 interface using simple text strings. Control using a simple terminal / comms program (Windows HyperTerminal) or our free Windows application software. Kit Order Code: 3190KT - **£84.95**
Assembled Order Code: AS3190 - **£99.95**



40 Second Message Recorder

Feature packed non-volatile 40 second multi-message sound recorder module using a high quality Winbond sound recorder IC. Stand-alone operation using just six onboard buttons or use onboard SPI interface. Record using built-in microphone or external line in. 8-24 Vdc operation. Just change one resistor for different recording duration/sound quality. sampling frequency 4-12 kHz. Kit Order Code: 3188KT - **£29.95**
Assembled Order Code: AS3188 - **£37.95**
120 second version also available



Bipolar Stepper Motor Chopper Driver

Get better performance from your stepper motors with this dual full bridge motor driver based on SGS Thompson chips L297 & L298. Motor current for each phase set using on-board potentiometer. Rated to handle motor winding currents up to 2 Amps per phase. Operates on 9-36Vdc supply voltage. Provides all basic motor controls including full or half stepping of bipolar steppers and direction control. Allows multiple driver synchronisation. Perfect for desktop CNC applications. Kit Order Code: 3187KT - **£39.95**
Assembled Order Code: AS3187 - **£49.95**



Video Signal Cleaner

Digitally cleans the video signal and removes unwanted distortion in video signal. In addition it stabilises picture quality and luminance fluctuations. You will also benefit from improved picture quality on LCD monitors or projectors. Kit Order Code: K8036KT - **£32.95**
Assembled Order Code: VM106 - **£49.95**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

Motor Speed Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full details.

DC Motor Speed Controller (100V/7.5A)



Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - **£19.95**
Assembled Order Code: AS3067 - **£27.95**

Computer Controlled / Standalone Unipolar Stepper Motor Driver

Drives any 5-35Vdc 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps. Provides speed and direction control. Operates in stand-alone or PC-controlled mode for CNC use. Connect up to six 3179 driver boards to a single parallel port. Board supply: 9Vdc. PCB: 80x50mm. Kit Order Code: 3179KT - **£16.95**
Assembled Order Code: AS3179 - **£23.95**



Computer Controlled Bi-Polar Stepper Motor Driver

Drive any 5-50Vdc, 5 Amp bi-polar stepper motor using externally supplied 5V levels for STEP and DIRECTION control. Opto-isolated inputs make it ideal for CNC applications using a PC running suitable software. Board supply: 8-30Vdc. PCB: 75x85mm. Kit Order Code: 3158KT - **£24.95**
Assembled Order Code: AS3158 - **£34.95**



Bidirectional DC Motor Speed Controller

Control the speed of most common DC motors (rated up to 32Vdc/10A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections. Kit Order Code: 3166v2KT - **£23.95**
Assembled Order Code: AS3166v2 - **£33.95**



AC Motor Speed Controller (600W)

Reliable and simple to install project that allows you to adjust the speed of an electric drill or 230V AC single phase induction motor rated up to 600 Watts. Simply turn the potentiometer to adjust the motors RPM. PCB: 48x65mm. Not suitable for use with brushless AC motors. Kit Order Code: 1074KT - **£15.95**
Assembled Order Code: AS1074 - **£23.95**



See www.quasarelectronics.com for lots more motor controllers



The Electronic Kit Specialists Since 1993

Credit Card Sales
01279 467 799

Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

500-in-1 Electronic Project Lab

Top of the range. Complete self-contained electronics course. Takes you from beginner to 'A' Level standard and beyond! Contains all the hardware and manuals to assemble 500 projects. You get 3 comprehensive course books (total 368 pages) - *Hardware Entry Course*, *Hardware Advanced Course* and a microprocessor based *Software Programming Course*. Each book has individual circuit explanations, schematic and connection diagrams. Suitable for age 12+. Order Code EPL500 - **£199.95**
Also available: 30-in-1 **£19.95**, 50-in-1 **£29.95**, 75-in-1 **£39.95** £130-in-1 **£49.95** & 300-in-1 **£89.95** (see website for details)



Tools & Test Equipment

We stock an extensive range of soldering tools, test equipment, power supplies, inverters & much more - please visit website to see our full range of products.

Advanced Personal Scope 2 x 240MS/s

Features 2 input channels - high contrast LCD with white backlight - full auto set-up for volt/div and time/div - recorder roll mode, up to 170h per screen - trigger mode: run - normal - once - roll ... - adjustable trigger level and slope and much more. Order Code: APS230 - ~~£499.95~~ **£399.95**



Personal Scope 10MS/s

The Personal Scope is not a graphical multimeter but a complete portable oscilloscope at the size and the cost of a good multimeter. Its high sensitivity - down to 0.1mV/div - and extended scope functions make this unit ideal for hobby, service, automotive and development purposes. Because of its exceptional value for money, the Personal Scope is well suited for educational use. Order Code: HPS10 - ~~£189.95~~ **£159.95**



See website for more super deals!



www.quasarelectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads



Everyday Practical Electronics

FEATURED KITS

AUGUST 2011

Everyday Practical Electronics Magazine has been publishing a series of popular kits by the acclaimed Silicon Chip Magazine Australia. These projects are 'bullet proof' and already tested Down Under. All Jaycar kits are supplied with specified board components, quality fibreglass tinned PCBs and have clear English instructions. Watch this space for future featured kits.

240V 10A Deluxe Motor Speed Controller Kit

KC-5478 £36.25 plus postage & packing

The deluxe motor speed controller kit allows the speed of a 240VAC motor to be controlled smoothly from near zero to full speed. The advanced design provides improved speed regulation & low speed operation. Also features soft-start, interferences suppression, fuse protection and over-current protection. Kit supplied with all parts including pre-cut metal case.

Note: Requires UK mains socket or adaptor

Featured in EPE May 2011



SMS Controller Module

KC-5400 £21.25 plus postage & packing

Control appliances or receive alert notification from anywhere. By sending plain text messages this kit will allow you to control up to eight devices. At the same time, it can also monitor four digital inputs. It works with old Nokia handsets such as the 5110, 6110, 3210, and 3310, which can be bought inexpensively.

- Kit supplied with PCB, pre-programmed microcontroller and all electronics components with manual
- Requires a Nokia data cable which can be readily found in mobile phone accessory stores

Featured in EPE: March 2007



Automotive Kits

Voltage Monitor Kit

KC-5424 £8.50 plus postage & packing

This versatile kit will allow you to monitor the battery voltage, the airflow meter or oxygen sensor in your car. The kit features 10 LEDs that illuminate in response to the measured voltage, preset 9-16V, 0-5V or 0-1V ranges, complete with a fast response time, high input impedance and auto dimming for night time driving. Kit includes PCB with overlay, LED bar graph and all electronic components.

- PCB: 74 x 47mm
- 12VDC

Featured in EPE September 2010




Ignition Kit

KC-5442 £34.50 plus postage & packing

This advanced and versatile ignition system is suited for both two & four stroke engines. Used to modify the factory ignition timing or as the basis for a stand-alone ignition system with variable ignition timing, electronic coil control and anti-knock sensing (available separately).

- Timing retard & advance over a wide range
- Suitable for single coil systems
- Dwell adjustment
- Single or dual mapping ranges
- Max & min RPM adjustment
- Kit includes PCB with overlay, programmed micro, all electronic components and die cast box

Featured in EPE November 2009

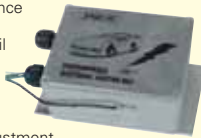

Water Tanks Kits

PIC Based Water Tank Level Meter Kit

KC-5460 £39.50 plus postage & packing

This PIC-based unit uses a pressure sensor to monitor water level and will display tank level via an RGB LED at the press of a button. The kit can be expanded to include and optional wireless remote display panel that can monitor up to ten separate tanks (KC-5461) or you can add a wireless remote controlled mains power switch (KC-5462) to control remote water pumps. Kit includes electronic components, case, screen printed PCB & pressure sensor.

Featured in EPE May 2010

Also available: KC-5461

Remote display kit £31.00



Remote Control Mains Switch Kit

KC-5462 £36.25 plus postage & packing

Commercial remote control mains switches are available but these are generally limited to a range of less than 20m. This UHF system will operate up to 200m and is perfect for remote power control systems etc. The switch can be activated using the included hand held controller. Kit supplied with case, screen printed PCB, RF modules and all electronic components.

Note: Requires UK mains socket or adaptor.

Featured in EPE May 2010



Hand held remote control!

Low Cost Programmable Interval Timer

KC-5464 £12.75 plus postage & packing

Here's a new and completely updated version of the 'Flexitimer' shown to the right. It is link programmed for either a single ON, or continuous ON/OFF cycling for up to 48 on/off time periods. Selectable periods are from 1 to 80 seconds, minutes, or hours and it can be restarted at any time. Kit includes PCB and all specified electronic components.

- Power requirement: 12VDC
- PCB Dimensions: 102 x 42mm

Featured in EPE August 2010



Luxeon Star LED Driver Kit

KC-5389 £11.00 plus postage & packing

Luxeon high power LEDs are some of the brightest LEDs available in the world. They offer up to 120 lumens per unit, and will last up to 100,000 hours! This kit allows you to power the fantastic 1W, 3W, and 5W Luxeon Star LEDs from 12VDC. This means that you can take advantage of what these fantastic LEDs have to offer, and use them in your car, boat, or caravan.

- Kit supplied with PCB, and all electronic components

Featured in EPE April 2007




Delta Throttle Timer Kit

KC-5373 £9.25 plus postage & packing

This brilliant design will trigger a relay when the accelerator is pressed or lifted quickly. Used for automatic transmission switching of economy to power modes or trigger electronic blow-off valves on quick throttle lifts etc. It is completely adjustable, and uses the output of a standard throttle position sensor.

Featured in EPE November 2006

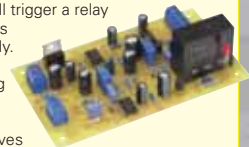

The 'Flexitimer' Timer Kit

KA-1732 £7.25 plus postage & packing

This kit uses a handful of components to accurately time intervals from a few seconds to a whole day. It can switch a number of different output devices and can be powered by a battery or mains plugpack.

- Kit includes PCB and all components
- Power requirement 12 - 15VDC

Featured in EPE May/June 2008




45 Second Voice Recorder Module

KC-5454 £16.00 plus postage & packing

This kit has been improved and can now be set up easily to record two, four or eight different messages for random-access playback or a single message for 'tape mode' playback. Also, it now provides cleaner and glitch-free line-level audio output suitable for feeding an amplifier or PA system. It can be powered from any source of 9-14V DC.

- Supplied with silk screened and solder masked PCB and all electronic components.
- PCB: 120 x 58mm

Featured in EPE February 2011

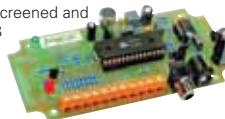

3V to 9V DC to DC Converter Kit

KC-5391 £6.00 plus postage & packing

This great little converter allows you to use regular Ni-Cd or Ni-MH 1.2V cells, or Alkaline 1.5V cells for 9V applications. Using low cost, high capacity rechargeable cells, the kit will pay for itself in no-time! You can use any 1.2-1.5V cells you desire. Imagine the extra capacity you would have using two 9000mAh D cells in replacement of a low capacity 9V cell.

• PCB Dimensions: 59 x 29mm
Featured in EPE June 2007



Jaycar
Electronics

Freecall order: 0800 032 7241

Best Selling Kits for Electronic Enthusiasts

KIT OF THE MONTH

Ultrasonic Antifouling Kit for Boats

KC-5498 £90.50 plus postage & packing

Marine growth electronic antifouling systems can cost thousands. This project uses the same ultrasonic waveforms and virtually identical ultrasonic transducers mounted in sturdy polyurethane housings. By building yourself (which includes some potting) you save a fortune! Standard unit consists of control electronic kit and case, ultrasonic transducer, potting and gluing components and housings. The single transducer design of this kit is suitable for boats up to 10m (32ft); boats longer than about 14m will need two transducers and drivers. Basically all parts supplied in the project kit including wiring. (Price includes epoxies).

Don't just sit there BUILD SOMETHING!

- 12VDC
- Suitable for power or sail
- Could be powered by a solar panel/ wind generator
- PCB: 78 x 104mm

Best Seller




Theremin Synthesiser Kit MkII

KC-5475 £27.25 plus postage & packing

The ever-popular Theremin is better than ever. It's easier to set up with extra test points for volume adjustment and power supply measurement and it now runs on AC to avoid the interference switchmode plugpacks can cause. It's also easier to build with PCB-mounted switches and pots to reduce wiring to just the hand plate, speaker and antenna and has the addition of a skew control to vary the audio tone from distorted to clean.

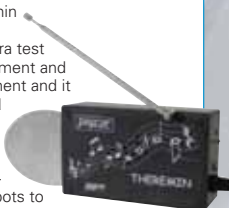- Complete kit contains PCB with overlay, pre-machined case and all specified components



SLA Battery Health Checker Kit

KC-5482 £29.00 plus postage & packing

The first versions of the battery zapper included a checker circuit. The Mk III battery zapper (KC-5479) has a separate checker circuit - and this is it. It checks the health of SLA batteries prior to charging or zapping with a simple LED condition indication of fair, poor, good etc.

- Overlay PCB and electronic components
- Case with machined and silk-screened front panel
- PCB Dimensions: 185 x 101mm



SD/MMC Card Webserver Kit in a Box

KC-5489 £32.75 plus postage & packing

Host your own website on a common SD/MMC card with this compact Web server In a Box (WIB). Connecting to the Internet via your modem/router, it features inbuilt HTTP server, FTP server, SMTP email client, dynamic DNS client, RS232 serial port, four digital outputs and four analogue inputs. Requires a SD memory card, some SMD soldering and a 6-9VDC adaptor. Kit includes PCB, case and electronic components.

- PCB Dimensions: 123 x 74mm



Remote Control Digital Timer Kit

KC-5496 £14.50 plus postage & packing

Remote-controlled digital timer with a bright 20mm-high 7-segment red LED display. It can count up or down from one second to 100 hours in 1-second increments. Its timing period can either be set and controlled using the remote control or it can be automatically controlled via external trigger/reset inputs. An internal relay and buzzer activate when the unit times out. The relay contacts can be used to switch devices rated up to 30VDC or 24VAC and the project can be powered from a plugpack or a battery. Short form kit only - you'll need to add your own universal remote, power supply and enclosure.

- 9-12VDC @300mA
- PCB and components included



"Minivox" Voice Operated Relay Kit

KC-5172 £6.00 plus postage & packing

Voice operated relays are used for 'hands free' radio communications and some PA applications etc. Instead of pushing a button, this device is activated by the sound of a voice. This tiny kit fits in the tightest spaces and has almost no turn-on delay. 12VDC @ 35mA required. Kit is supplied with PCB electret mic, and all specified components.

- PCB Dimensions: 47 x 44mm



Audio Amplifier Kits

"The Champ" Audio Amplifier Kit

KC-5152 £3.00 plus postage & packing

This tiny module uses the LM386 audio IC, and will deliver 0.5W into 8 ohms from a 9 volt supply making it ideal for all those basic audio projects. It features variable gain, will happily run from 4-12VDC and is smaller than a 9 volt battery, allowing it to fit into the tightest of spaces. PCB & all electronic components included.

"Pre-Champ" Versatile Preamplifier

KC-5166 £3.50 plus postage & packing

Designed to be used with the 'Champ' amplifier KC-5152. Unless you have a signal of sufficient amplitude the 'Champ' will not produce its maximum power output. The 'Pre-Champ' is the answer with a gain in excess of 40dB, which is more than enough for most applications. You can vary the gain by changing a resistor and there is even provision on the PCB for an electret microphone.

- Power requirement 6 - 12VDC
- Kit includes PCB and electronic components

50 Watt Amplifier Module

KC-5150 £11.00 plus postage & packing

This 50 watt unit uses a single chip module and provides 50W RMS @ 8 ohms with very low distortion. PC Board and all electronic components supplied. Requires heatsink. See website for full specs.

- PCB Dimensions: 84 x 58mm
- Heatsink to suit HH-8590 £7.00



An excellent way for new comers to dip their toes into the wonders of electronics!

SHORT CIRCUITS - VOLUME 1

This volume will teach you everything you need to get started in electronics and is suitable for ages 8+. We give you the option of buying the book on its own, or together with the accompanying kit that contains the components for each of the 20-odd projects described in the book. Some of the exciting projects include a Police Siren, Electronic Organ, Sound Effects Unit, Light Chaser and many, many more! The full colour 96 page book, is lavishly illustrated with over 100 drawings and diagrams. No prior knowledge of electronics is needed, projects are fun and totally safe to build.

Short Circuits Book
BJ-8502 £3.75

Short Circuits Project Kit
KJ-8504 £12.50

Short Circuits Book and Project Kit
KJ-8502 £16.50



MORE INFO
AVAILABLE ONLINE

AGES 8+



Post & Packing Charges

Order Value	Cost
£10 - £49.99	£5
£50 - £99.99	£10
£100 - £199.99	£20
£200 - £499.99	£30
£500+	£40

Note: Products are despatched from Australia, so local customs duty & taxes may apply.

- All pricing in Pounds Sterling
- Minimum order £10

Prices valid until 31/8/2011

Max weight 12lb (5kg)
Heavier parcels POA
Minimum order £10

HOW TO ORDER

WEB: www.jaycarelectronics.co.uk
PHONE: 0800 032 7241*
FAX: +61 2 8832 3118*
EMAIL: techstore@jaycarelectronics.co.uk
POST: P.O. Box 107, Rydalmere NSW 2116 Australia

*Australian Eastern Standard Time
(Monday - Friday 09.00 to 17.30 GMT + 10 hours)
Expect 10-14 days for air parcel delivery



Order online: www.jaycarelectronics.co.uk

Jaycar
Electronics



velleman®

UK's No 1 source for VELLEMAN® Kits

Digital Echo Chamber Kit
A compact sound effects kit, with built-in mic or line in, line out or speaker (500mW). 4 Adjustment controls.
Power: 9Vdc 150mA

MK182 Velleman kit £11.43



3rd Brake Light Flasher Kit
Works with any incandescent or LED rear centre brake light. Flashes at 7Hz for 5 or 10 times, adjustable re-triggering.
Power: 12Vdc max load 4A

MK178 Velleman kit £6.30




Digital Clock Mini Kit
Red 7 Segment display in attractive enclosure, automatic time base selection, battery back-up, 12 or 24hr modes.
Power: 9Vac or dc

MK151 Velleman kit £15.09



Proximity Card Reader Kit
A simple security kit with many applications. RFID technology activates a relay, either on/off or timed. Supplied with 2 cards, can be used with up to 25 cards. Power: 9Vac or dc

MK179 Velleman kit £14.25

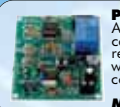

Running Microbug Kit

Powered by two subminiature motors, this robot will run towards any light source. Novel shape PCB with LED eyes.
Power: 2 x AAA Batteries

MK127 Velleman kit £9.02



200W Power Amplifier
A high quality audio power amp. 200W music power @ 4Ω 3-200kHz. Available as a kit without heatsink or module including heatsink.
K8060 Velleman kit £12.85
Heatsink for kit £9.95
VM100 Module £38.54



MP3 Player Kit
Plays MP3 files from an SD card, supports ID3 tag which can be displayed on optional LCD. Line & headphone output. Remote control add-on. Power: 12Vdc 100mA

K8095 Velleman kit £39.99



DC to Pulse width Modulator
A handy kit to accurately control DC motors etc. Overload & short circuit protection. Input voltage 2.5-35Vdc. Max output 6.5A.
Power: 8-35Vdc

K8004 Velleman kit £9.95



Audio Analyser Kit
A small spectrum analyser with LCD. Suitable for use on 2, 4 or 80 systems. 300mW to 1200W (20) 20-20kHz. Panel mounting, back-lit display. Power: 12Vdc 75mA

K8098 Velleman kit £31.65



USB DMX Interface
512 DMX Channels controlled by PC via USB. Software & case included. Available as a kit or ready assembled module.

K8062 Velleman kit £47.90
VM116 Module £67.15



USB Interface Board
Featuring 5 in, 8 digital outputs, 2 in & 2 analogue outputs. Supplied with software. Available as a kit or ready assembled module.

K8055 Velleman kit £24.80
VM110 Module £34.90



8 Channel USB Relay Board
PC Controlled 16A relays with toggle, momentary or timed action. Test buttons included, available in a kit or assembled.

K8090 Velleman kit £39.95
VM8090 Module £58.40



0845 251 4363

Kit Catalogue Available

Self Assembly Kits & Ready made Modules - See our web site for details on the whole range, Data sheets, Software and more.
www.esr.co.uk

Multifunction Up/Down Counter
An up or down counter via on-board button or ext input. Time display feature. Alarm count output. 0-9999 display.
Power: 9-12Vdc 150mA

K8035 Velleman kit £17.85



Nixie Clock Kit
Gas filled nixie tubes with their distinctive orange glow. HH:MM display, automatic power sync 50/60Hz.
Power: 9-12Vdc 300mA

K8099 Velleman kit £64.96



Mini USB Interface Board
New from Velleman this little interface module with 15 inputs/outputs inc digital & analogue in, PWM outputs. USB Powered 50mA. Software supplied

VM167 Module £26.80



Thermostat Mini Kit
General purpose low cost thermostat kit. +5 to +30°C Easily modified temperature range/min/max/hysteresis 3A Relay.
Power: 12Vdc 100mA

MK138 Velleman Kit £4.55



Velleman Function Generator
PC Based USB controlled function generator. 0.01Hz to 2MHz Pre-defined & waveform editor. Software supplied. See web site for full feature list.

PCGU1000 Velleman £118.38



Velleman PC Scope
PC Based USB controlled 2 channel 60MHz oscilloscope with spectrum analyser & Transient recorder. 2 Scope probes & software included. See web site for full feature list.

PCSU1000 Velleman £249.00



Velleman PC Scope/Generator
PC Based USB controlled 2 channel oscilloscope AND Function generator. Software included. See web site for full feature list.

PCSGU250 Velleman £113.67




RF Remote Control Transmitter
Single channel RF keyfob transmitter with over 13,122 combinations. Certified radio frequency 433.92MHz. Power: 12Vdc 2mA (inc) For use with TL-1,2,3,4 receivers.

TL-5 Cebek Module £14.64



RF Remote Control Receiver
Single channel RF receiver with relay output. Auto or manual code setup. Momentary output, 3A relay.
Power: 12Vdc 60mA For use with TL-5 or TL-6 transmitters.

TL-1 Cebek Module £28.25

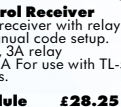


Keypad Access Control
An electronic lock with up to ten 4 digit codes. Momentary or timed (1-60sec/1-60min) output. Relay 5A.
Power: 12Vdc 100mA Keypad included.

DA-03 Cebek Module £54.26



AC Motor Controller
A 230Vac 375W motor speed control unit giving 33 to 98% of full power.
Power: 230Vac

R-8 Cebek Module £12.14

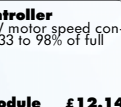

cebek®

Now Available - Cebek Modules
All modules assembled & tested.

Digital Record/Player
Non volatile flash memory. Single 20 sec recording via integral mic, 2W output to 8Ω speaker.
Power: 5Vdc 100mA

C-9701 Cebek Module £7.89



2 Digital Counter
Standard counter 0 to 99 from input pulses or external signal. With reset input, 13.5mm Displays.
Power: 12Vdc 90mA.

CD-9 Cebek Module £12.99



1.8W Mono Amplifier
Compact mono 1.8W RMS 4Ω power stage, short circuit & reverse polarity protection. 30 18kHz. Power: 4-14Vdc 150mA

E-1 Cebek Module £5.87



20W 2 Channel Amplifier
Mono amplifier with 2 channels (Low & High frequency). 20W RMS 4Ω per channel, adjustable high level. 22-22kHz, short circuit & reverse polarity protection. Power: 8-18Vdc 2A

E-14 Cebek Module £22.11



5W Stereo Amplifier
Stereo power stage with 5W RMS 4Ω. 30-18kHz, short circuit & reverse polarity protection.
Power: 6-15Vdc 500mA

E5-2 Cebek Module £21.54



12Vdc Power Supply
Single rail regulated power supply complete with transformer, 130mA max, low ripple, 12Vdc with adjustment.

FE-103 Cebek Module £13.16



1-180 Second Timer
Universal timer with relay output. Time start upon power up or push button. LED indication. 5A Relay.
Power: 12Vdc 60mA

I-1 Cebek Module £12.92



Cyclic Timer
Universal timer with relay output. Time start upon power up or push button. On & Off times 0.3-60 Seconds, LED indication. 5A Relay.
Power: 12Vdc 80mA

I-10 Cebek Module £14.12




Light Detector
Adjustable light sensor operating a relay. Remote sensor & terminals for remote adjustment pot. 5A Relay.
Power: 12Vdc 60mA

I-4 Cebek Module £13.98



Liquid Level Detector
A liquid level controlled relay. Remote sensor operates relay when in contact with a liquid. 5A Relay.
Power: 12Vdc 60mA

I-6 Cebek Module £13.08

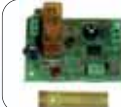

Thermostat
A temperature controlled relay. Adjustable between -10 to 60°C Sensor on remote PCB. Connector for external adjustment pot. 5A Relay.
Power: 12Vdc 60mA

I-8 Cebek Module £12.80



Start / Stop Relay
Simple push button control of a relay. Either 1 or 2 button operation 5A Relay.
Power: 12Vdc 60mA

I-9 Cebek Module £12.83



Components

Hardware

Soldering

Switches

Test Equipment

Transformers

Motors

PCB Equipment

Connectors

Power Supplies

Enclosures

Relays



www.esr.co.uk

Tel: 0191 2514363

Fax: 0191 2522296

sales@esr.co.uk

Station Road
Cullercoats
Tyne & Wear
NE30 4PQ



Prices Exclude Vat @20%.

UK Carriage £2.50 (less than 1kg)

£6.50 greater than 1kg or >£30

Cheques / Postal orders payable to

ESR Electronic Components Ltd

PLEASE ADD CARRIAGE & VAT TO ALL ORDERS

Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS
 EDITORIAL Wimborne Publishing Ltd., 113 Lynwood
 Drive, Merley, Wimborne, Dorset, BH21 1UU
Phone: (01202) 880299. **Fax:** (01202) 843233.
Email: enquiries@wimborne.co.uk
Website: www.epemag.com
 See notes on **Readers' Technical Enquiries** below
 – we regret technical enquiries cannot be answered
 over the telephone.

Advertisement Offices:

Everyday Practical Electronics Advertisements
 113 Lynwood Drive, Merley, Wimborne, Dorset,
 BH21 1UU
Phone: 01202 880299 **Fax:** 01202 843233
Email: stewart.kearn@wimborne.co.uk

Editor:

MATT PULZER

Consulting Editor:

DAVID BARRINGTON

Subscriptions:

MARILYN GOLDBERG

General Manager:

FAY KEARN

Graphic Design:

RYAN HAWKINS

Editorial/Admin:

(01202) 880299

Advertising and**Business Manager:**

STEWART KEARN

(01202) 880299

On-line Editor:

ALAN WINSTANLEY

EPE Online**(Internet version) Editors:**

CLIVE (Max) MAXFIELD

and ALVIN BROWN

MIKE KENWARD

Publisher:**READERS' TECHNICAL ENQUIRIES****Email:** techdept@wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years' old. Letters requiring a personal reply must be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons. We are not able to answer technical queries on the phone.

PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in EPE employ voltages that can be lethal. You should not build, test, modify or renovate any item of mains-powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are bona fide, the magazine and its publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment, as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.

EPE EVERYDAY PRACTICAL ELECTRONICS

How safe are your digits?

I'm sure your fingers are fine, but what about all your ones and zeroes? Although it is still perfectly possible to live without a computer, the Internet, email and a mobile/smart phone, most of us are more than happy to take advantage of the work, social and entertainment opportunities provided by the digital revolution.

These systems (usually) work so effortlessly that it is easy to believe that they are purely benign and only do what we want them to do. However, the increasing number of leaks, hacks and other revelations about the vulnerabilities of digital systems should make all of us keep an eye on what we store and where we store it.

This is about to become all the more important, as 'cloud-based' systems become increasingly prevalent. The main idea with 'clouds' is that you store files on a distant rack of hard drives, and access them as and when you need to from your home or work PC, or increasingly your smartphone. In some ways it's a great idea – you only need one version of a file and you can be sure that your files are backed up effectively. On the other hand, how do you know files are secure? This is still a very new technology, and it's well worth checking that your digital life is properly encrypted and safe from unauthorised access.

Apart from security, there is also the question of reliable access – your files will only be available when you have a working Internet connection. I don't know about your ISP, but mine is really only good enough for about 50 weeks a year. On the face of it, not a bad score, but that still leaves one or two weeks – spread out over a year – when Internet access ranges from poor to abysmal, to non-existent.

I couldn't do my job without email, so I now have a reasonably good 'insurance' system by 'tethering' my smartphone to a laptop. It's not the fastest link, but keeps me going if my cable connection is down because a road digger cuts me off, or the ISP has decided that it needs to 'carry out essential maintenance' and leaves me disconnected for six hours. However, the thought of not only being without email, but also temporarily losing my work files, music, photographs and all the other digital bits and pieces in my computer leaves me cold, and I certainly wouldn't want to access that lot via my smartphone. It may well be that clouds are the way of the future, but I don't think I'll be an 'early adopter'. In the meantime, I do remember – as should you – the old adage: there are only two kinds of hard drives, ones that have failed, and ones that are going to fail. So, wherever your files live, back-up back-up, and back-up again!

Mike



NEWS

A roundup of the latest Everyday News from the world of electronics



Will UltraViolet rain on iCloud's parade? by Barry Fox

Apple grabbed advantage of the record industry's failure to agree a unified strategy on online music download sales, and made iTunes the *de facto* standard. Apple is now hoping to repeat history with online streaming of music, movies, TV shows and electronic books from an iCloud 'digital locker', to subscribers with up to ten iPods, iPads or iPhones. This puts Apple in direct competition with DECE, the Digital Entertainment Content Ecosystem, which promotes the gestating UltraViolet digital locker cloud system.

DECE has been planning and promising a digital locker system since 2008 and has – at least tentative – support of most major hardware and software companies, with the notable exception of Apple. Hard facts on UltraViolet only began to emerge at the *Consumer Electronics Show* in Las Vegas, last January, and the organisation has since been largely silent on progress.

However, by happy coincidence, Tim Wright, VP worldwide, new media and technology, Sony Pictures, and DECE spokesman, had already been scheduled to give a routine progress report on UltraViolet at *Insight 360*, an entertainment industry forum held in London by the Industry Trust for IP Awareness, British Video Association (BVA), Motion Picture Association (MPA) and British Film Institute (BFI) – on a day which turned out to be the day after Apple's surprise announcements.

'Why should dealers and consumers be tied in to a proprietary system, when there is an open system with a wide range of devices?' Wright asked the audience rhetorically. 'We are offering openness and diversity and consistency for the user.

Freedom of entitlement is coming in 2011. UltraViolet is an open and shared system, not the closed approach that others have announced.'

But hard facts on UltraViolet's commercial launch plans remained sparse. After screening the same, or very similar, promotional video shown at CES in January, Tim Wright reiterated that anyone with a free UV account will be able to use purchased 'UV' programming on up to 12 devices, with access by up to six

his talk, without offering the audience an opportunity to ask questions.

Earlier, Chris Law, MD, Warner Bros Entertainment UK, had said: 'It will take 12 to 18 months until there is a robust mass market for digital sell through. UltraViolet is just about to launch in the US and is due in the UK at the end of the year.'

'There is a lot to be done. We want a seamless flexible proposition. It's what's needed for sell through to transition from DVD and Blu-ray. Apple has done a fantastic job with iTunes and there is a lot to be done to get digital sell through into non-Apple products'. The question remains, 'is this too little too late?', as Apple's iCloud appears on the horizon.



Can iCloud repeat the success of iTunes?

household members, with up to three of them streaming simultaneously.

The launch timescale remains only broadly defined, with the US 'first in the fall', the UK and Canada sometime in late 2011 and 'other countries in 2012.'

'We are continuing to build' says Wright. Apps for Windows and Android devices are expected 'within 2011' and devices with embedded UltraViolet capability some time in 2012.

There is still no clear guidance on upgrading existing hardware. 'I suspect many devices can be made UV-compatible by software download' says Wright, without elaborating.

'We look forward to telling you more at future events'; he said as he finished

CHROME-PLATED COMPUTING

If you fancy a change of operating system from the dominant trio of Windows, OSX and Linux then there's good news. Google's Chrome OS has launched in the US with 'Chromebook' laptops from Samsung. The UK launch is slated for August.


Squires catalogue

Component and tool vendor, Squires, has launched their new catalogue. It features a wide range of electronic components, including: batteries, cable, cases, connectors, motors, fuses, LEDs, resistors, semiconductors, transformers, test equipment and much more.

Readers who would like to receive a free copy can phone (01243 842424) or email (sales@squirestools.com) to request one. It can be viewed online at: www.squirestools.com.



WORLD'S FASTEST GRAPHENE TRANSISTOR

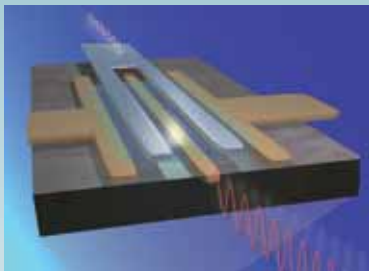

IBM researchers have demonstrated a radio-frequency graphene transistor with the highest cut-off frequency achieved so far for any graphene device – 100GHz. This high frequency record was achieved using wafer-scale, epitaxially grown graphene using processing technology compatible to advanced silicon device fabrication.

This accomplishment is a key milestone in an effort to develop the next-generation of communication devices based on carbon.

'A key advantage of graphene lies in the very high speeds in which electrons propagate, which is essential for achieving high-speed, high-performance next generation transistors,' said Dr TC Chen, vice president, science and technology, IBM Research. 'The breakthrough we are announcing demonstrates clearly that graphene can produce high performance devices and integrated circuits.'

Graphene is a single atom-thick layer of carbon atoms bonded in a hexagonal honeycomb-like arrangement. This two-dimensional form of carbon has unique electrical, optical, mechanical and thermal properties and its technological applications are being explored intensely.

Uniform and high-quality graphene wafers were synthesised by thermal decomposition of a silicon carbide (SiC) substrate. The graphene transistor itself, used a metal top-gate architecture and a novel gate insulator stack involving a polymer and a high dielectric constant oxide. The gate length was modest, 240nm, leaving plenty of space for further optimisation of its performance by scaling down the gate length.

It is noteworthy that the frequency performance of the graphene device already exceeds the cut-off frequency of state-of-the-art silicon transistors of the same gate length (~40GHz). Similar performance was obtained from devices based on graphene obtained from natural graphite, proving that high performance can be obtained from graphene of different origins. Previously, the team had demonstrated graphene transistors with a cut-off frequency of 26GHz using graphene flakes extracted from natural graphite.

Free potentiometer lubricant – an exclusive EPE offer!

Potentiometers and sliding position sensors are electromechanical devices whose performance and operating life can be dramatically improved through lubrication. Each of these devices has a metal wiper that moves along a resistive element or track to regulate current flow to a device, or to indicate when pre-calibrated positions are reached. Lubricating these tracks helps to prevent wear, attenuate electrical noise and extend operating life.

Wear prevention is the primary reason for potentiometer track lubrication. Most importantly, the lubricant film must be strong enough to prevent wear, but thin enough throughout the operating range to prevent contact hydroplaning and resulting intermitencies. When working with small, delicate mechanisms with extremely low starting torque, oils may be required. However, greases, with their important 'stay-in-place' advantage, have been the most successful potentiometer lubricants. Light, low shear greases, some approaching a semi-fluid state, can often be designed for even very low power applications.

EPE and Newgate are giving readers the opportunity to trial a specialist potentiometer/sliding position sensor lubricant for free. For details, see: www.potentiometerlubricant.co.uk

Pico Technology's fastest ever PicoScope!

The new four-channel PicoScope 6404 PC oscilloscope has an analogue bandwidth of 500MHz. This is matched by a real-time sampling rate of 5GS/s, which guarantees accurate representation of signals up to the full bandwidth. The scope also has an ultra-deep 1GS (gigasample) buffer memory that allows capture and analysis of complex waveforms, even when sampling at full speed.

As well as the headline specifications, the scope offers a built-in function generator, arbitrary waveform generator, mask limit testing, switchable bandwidth limiting on each channel, and switchable 1M Ω and 50 Ω inputs. This is in addition to the spectrum analysis, advanced triggering and serial decoding that are already standard features of Pico PC Oscilloscopes.

The scope connects to any Windows XP, Vista or Windows 7 PC with a USB 2.0 port. You can use one with a PC to save space on your workbench, or connect it to a laptop




Picotech's 6404 PC oscilloscope

to create a portable instrument that's perfect for field servicing and on-site demonstrations. The high sampling rate and bandwidth makes this scope ideal for analogue and digital circuit designers, test engineers and installers. If you want to write your own application to control the scope or use it as a digitiser, Pico provides a software development kit, including example code, free of charge.


More information on Pico Technology can be found at www.picotech.com

A Microchip first

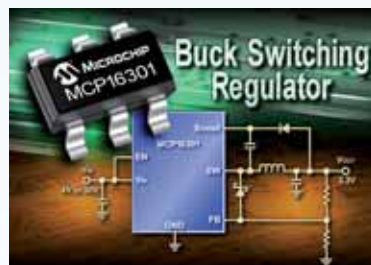


Microchip has announced its first 30V-input buck switching regulator. The MCP16301 combines a wide input voltage range of 4V to 30V, and a 600mA output across a voltage range of 2V to 15V, with up to 95% efficiency. The 'switch' integrated into the 6-pin package minimises the number of external components, enabling an efficient and compact solution for stepping down 12V to 24V DC power rails.

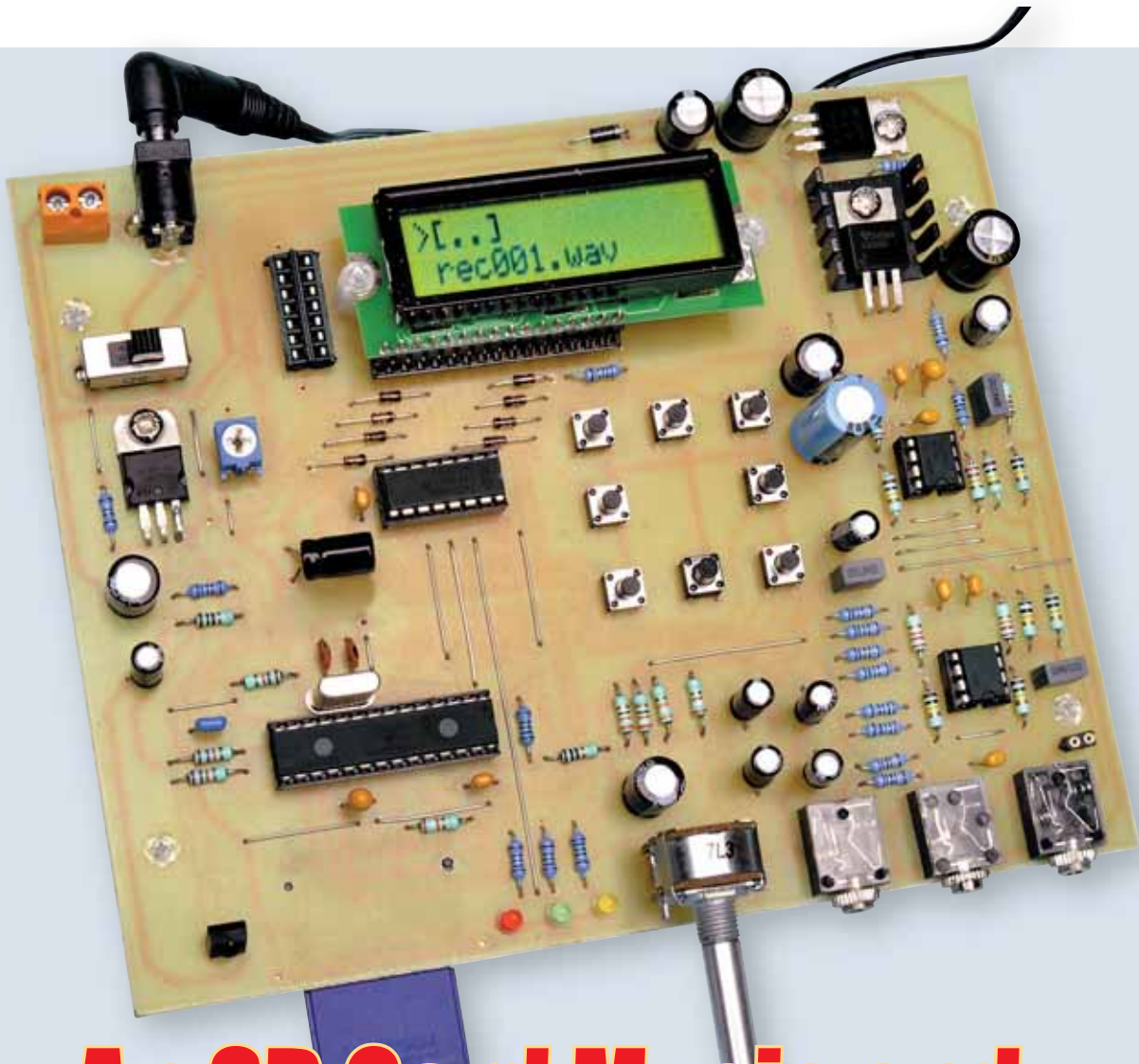Low-cost (\$15 to \$20) demo boards and development resources for fast development are available. For more information visit the Microchip Web site at: www.microchip.com/get/TQEG



An SD Card Music and Speech Recorder/Player

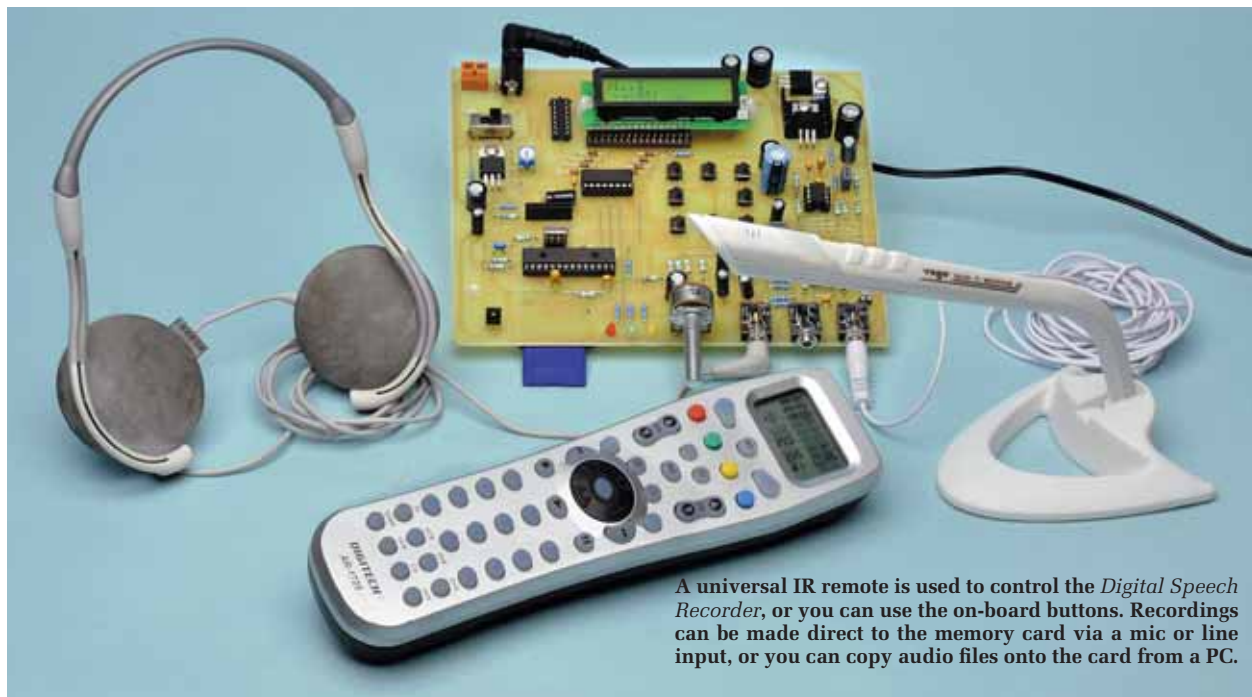This digital recorder stores WAV files on low-cost MMC/SD/SDHC cards. It can be used as a jukebox, a sound effects player or an expandable 'dictaphone'. You can use it as a free-standing recorder, or in conjunction with any Windows, Mac or Linux PC.



A universal IR remote is used to control the *Digital Speech Recorder*, or you can use the on-board buttons. Recordings can be made direct to the memory card via a mic or line input, or you can copy audio files onto the card from a PC.

IN the April 2011 issue of *EPE*, we published a very popular solid-state voice recorder project. The design was an improved version of older designs, employing the same voice recorder chip. These allowed you to record a number of short messages (up to about one minute of speech) and play them back at the touch of a button. The messages were stored in 'analogue EEPROM' cells in an analogue 8-bit format.

New level

This project takes the message recorder concept to a whole new level and employs a common SD memory card or MMC (multimedia card) for message storage. Depending on the size of the card, you can store and play back many hours of audio. We've also added infrared remote control and it can be used to play back any WAV file that you have downloaded or recorded on your PC.

We are presenting this project in a very simple module format; it is just a PC board with an SD card socket, a 2-line LCD panel and eight pushbutton switches to select the audio files and other features. If you want to build the unit into a case, you can take the LCD panel off the board and separately mount it and the same goes for the switches and sockets.

Compatible memory cards

The compatible cards to use with this project are MMC (MultiMedia Card), SD (Secure Digital) and SDHC (Secure Digital High Capacity) cards. SD cards come in capacities up to 2GB. Beyond that, you will find SDHC cards with capacities from 4GB to 32GB. The current version of the standard does not specify cards with capacities higher than 32GB, although these will become common in the future.

This project will work with most presently available cards. SD-type cards in particular have dropped in price dramatically and you can now pick up a 4GB SDHC card for under a fiver – see amazon.co.uk for example.

In operation, the unit can be run from either a 12V battery or a DC plugpack supply. It can drive stereo



The unit works with all commonly-available MMC, SD and SDHC memory cards. You can copy files from a PC onto these cards via an MMC/SD/SDHC card reader like the one shown at bottom right.

Parts List – Digital Audio Recorder/Player

1 PC board, code 815, available from the *EPE PCB Service*, size 164mm × 136mm
1 16 × 2 LCD module (DIL version, or SIL version) – see text
1 1k Ω horizontal-mount trimpot (VR1)
1 10k Ω log 16mm dual-gang pot (VR2)
8 SPST 6mm tactile switches (S1-S8)
1 DPDT PC-mount slide switch (S9) (Jaycar SS-0823)
1 2.5mm PC-mount male DC power connector (Jaycar PS-0520)
1 TO-220 mini heatsink (Jaycar HH-8502)
1 10MHz crystal (X1)
1 SD surface-mount card socket (Jaycar PS-0024) (CON1)
3 3.5mm PC-mount stereo jack sockets (Jaycar PS-0133)
1 infrared receiver module (IRD1) (Jaycar ZD-1952)
1 40-pin IC socket (to be cut)
1 28-pin IC socket (0.3-inch)
1 16-pin IC socket
2 8-pin IC sockets
12 M3 × 12mm nylon screws (some to be cut)
8 M3 × 9mm tapped nylon spacers
1 500mm 0.8mm-dia. length tinned copper (for links)
1 32-way machined pin socket strip
1 40-pin header strip
1 electret microphone insert (optional – see text)

Semiconductors

1 dsPIC33FJ64GP802-I/SP micro-controller (IC1) programmed for SIL version, or for DIL version – see text

1 74HC595 8-bit shift register (IC2)
2 LM833N dual op amps (IC3-IC4)
8 1N4148 signal diodes (D1-D8)
1 1N4004 silicon diode (D9)
1 7809 3-terminal regulator (REG1)
1 7805 3-terminal regulator (REG2)
1 LM317T variable regulator (REG3)
1 3mm red LED (LED1)
1 3mm green LED (LED2)
1 3mm yellow LED (LED3)

Capacitors

1 1000 μ F 16V electrolytic
2 470 μ F 25V electrolytic
3 470 μ F 16V electrolytic
1 220 μ F 16V electrolytic
5 100 μ F 16V electrolytic
3 10 μ F electrolytic
1 10 μ F tantalum
1 4.7 μ F electrolytic
2 220nF MKT polyester
2 150nF MKT polyester
3 100nF MKT polyester
5 100nF monolithic
2 18pF ceramic

Resistors (0.25W, 1%)

1 220k Ω	3 1k Ω
7 100k Ω	1 180 Ω (R2)
5 39k Ω	1 110 Ω (R1)
2 27k Ω	7 100 Ω
5 22k Ω	3 10 Ω
4 10k Ω	1 0 Ω (R3)
2 2.2k Ω	

(Note: 10 Ω and 160 Ω resistors may be required to adjust REG3).

Reproduced by arrangement
with SILICON CHIP
magazine 2011.
www.siliconchip.com.au

Firmware overview

The firmware is responsible for all the features of the *Digital Speech Recorder*. When you play a file, the firmware reads the WAV header that stores the sampling rate of the audio file. It then sets up an interrupt to push data into the DACs (digital-to-analogue converters) in the microprocessor at the requested sampling rate from the memory card.

When recording, data from the micro's ADC (analogue-to-digital converter) is written to a WAV file on the memory card using double buffering. The audio buffer stores up to 10KB of audio samples, and each sample is 16 bits.

FAT files

In this case, FAT does not stand for fat or obese. Instead, it stands for 'File Allocation Table' and is a file management system that's commonly used for hard disk drives and memory cards.

This Digital Speech Recorder recognises the FAT/FAT32 file system, meaning you should be able to read the cards using any Windows, Mac or Linux box coupled to a card reader or by using a laptop PC with an inbuilt card reader.

If you want more information on the FAT file system, refer to http://en.wikipedia.org/wiki/File_Allocation_Table or to a myriad of other internet sites.

If your memory card has a different file system on it, you will need to format the memory card first using a FAT/FAT32 system. Be sure to back up whatever was on the card *before* you do this, because the formatting process will erase anything that is on the card.

File sizes

Because this project does not decode compressed audio files, the size of the WAV files used is rather large compared to common MP3 files or similar audio formats. A WAV file can be up to 10 times larger than an equivalent MP3 file at the 44.1kHz sampling rate. Unlike MP3, uncompressed WAV is a lossless encoding format. Using lower sampling rates can reduce file sizes, but this will also reduce the audio quality and bandwidth.

Because we are using cheap and readily available SD or MMC cards, we are not too concerned about the size of

headphones or an external amplifier and loudspeakers.

WAV file format

The WAV file format from Microsoft can carry both compressed and uncompressed audio, but this speech recorder can *only* record and play back *uncompressed* WAV files. The samples are stored as 16-bit signed integers. The sampling rate of the encoded audio is stored in the WAV file header and is read by the recorder to vary the playback sampling speed.

Both stereo and mono files can be played. When playing mono files, both output channels (L and R) carry identical signals. A stereo WAV file contains information for the left and right channels interleaved, meaning every second sample is taken for each channel.

WAV files essentially store the PCM (pulse code modulation) samples of the audio waveform. The sampling frequency is twice the highest reproducible frequency in the audio stream. Note that WAV files have a '.wav' file extension.

Using Audacity To Convert MP3 Files To WAV Files



CONVERTING MP3 files (and other compressed audio formats) to WAV files suitable for the Speech Recorder is easy using a program called 'Audacity'. This freeware program allows you to convert at different sampling rates and can also be used as a basic sound editor.

Audacity can be downloaded from <http://audacity.sourceforge.net/download/>. There are versions for Windows, Mac and Linux. Follow the on-screen prompts after executing the downloaded installation program.

As indicated, Audacity can open MP3 (and other compressed) files. You can then export them to WAV format and copy them to an MMC/SD/SDHC card for use with this unit.

The first step in the conversion is to select the required sampling rate. This is a compromise between audio quality and the size of the file. The higher the sampling rate selected, the higher the audio quality but the bigger the file size.

Having selected the sampling rate, it's then just a matter of clicking 'File'

and then selecting the 'Export As WAV...' option.

There is no reason to choose a sampling rate higher than 44.1kHz, as this is high enough to encompass the whole of the audio spectrum (remember that the sampling rate will be double the highest reproducible frequency and that the audio spectrum reaches up to about 22kHz). Having converted the files to WAV files, it's then just a matter of copying them from the PC to the memory card via a card reader.

the files. Even at 40MB per 4-minute audio track, you can still store around 100 songs (or 400 minutes) of audio on a £5 4GB SDHC card.

Circuit description

Refer now to Fig.1 for the full circuit details of the Digital Speech Recorder. As shown, it's based around a powerful 16-bit DSP microcontroller from Microchip, the dsPIC33-FJ64GP802 (IC1).

The reasons for choosing this microcontroller are fourfold. First, it is one of the first microcontrollers from Microchip to have an integrated stereo DAC. Second, it is very fast, running at 40MIPS (millions of instructions per second). You need such speed when you are reading from a memory card in real time and dumping audio data onto the DACs.

Third, it has enough on-board RAM and program memory to implement the features of this project, and it comes in a through-hole package which is easier to install than an SMD. And finally, it runs from a 3.3V supply, which is

compatible with the supply requirements for a typical memory card.

IC1's system clock is derived from a 10MHz crystal (X1) via a PLL (phase-locked loop) stage to derive a 40MHz instruction clock. The two accompanying 18pF ceramic capacitors provide the correct loading for the crystal.

In operation, the microcontroller is responsible for implementing the hardware layer to read and write sectors to the MMC/SD/SDHC card. This low-level layer is called by higher layers that implement a FAT/FAT32 file system. The result is that we can read and write files.

The SPI (serial peripheral interface) outputs of the microcontroller connect to the SD card and to IC2, a 74HC595 8-bit shift register that's used to drive the LCD module. This shift register is used as a 'port expander' because there are simply not enough output pins on the microcontroller.

The output of the shift register is also used to scan the eight on-board tactile switches, S1 to S8. These are


connected via diodes D1 to D8, which effectively form a wired AND gate and they are active low. The microcontroller can detect a switch press by loading the shift register with the values 0xFE, 0xFD, 0xFB, 0xF7 and so on, up to 0x7F (one 0 bit).

Note that the E (enable) line to the LCD module is kept low during this scan, so as not to affect the contents of the display.

Remote control


The speech recorder and audio player can also be operated using a remote control. The infrared signals are amplified, filtered and demodulated by an infrared module (IRD1). Its supply is decoupled using a 10 Ω resistor and 10 μ F electrolytic capacitor. The data line passes through a voltage divider consisting of two 27k Ω resistors to pin 14 (RB5) of IC1.

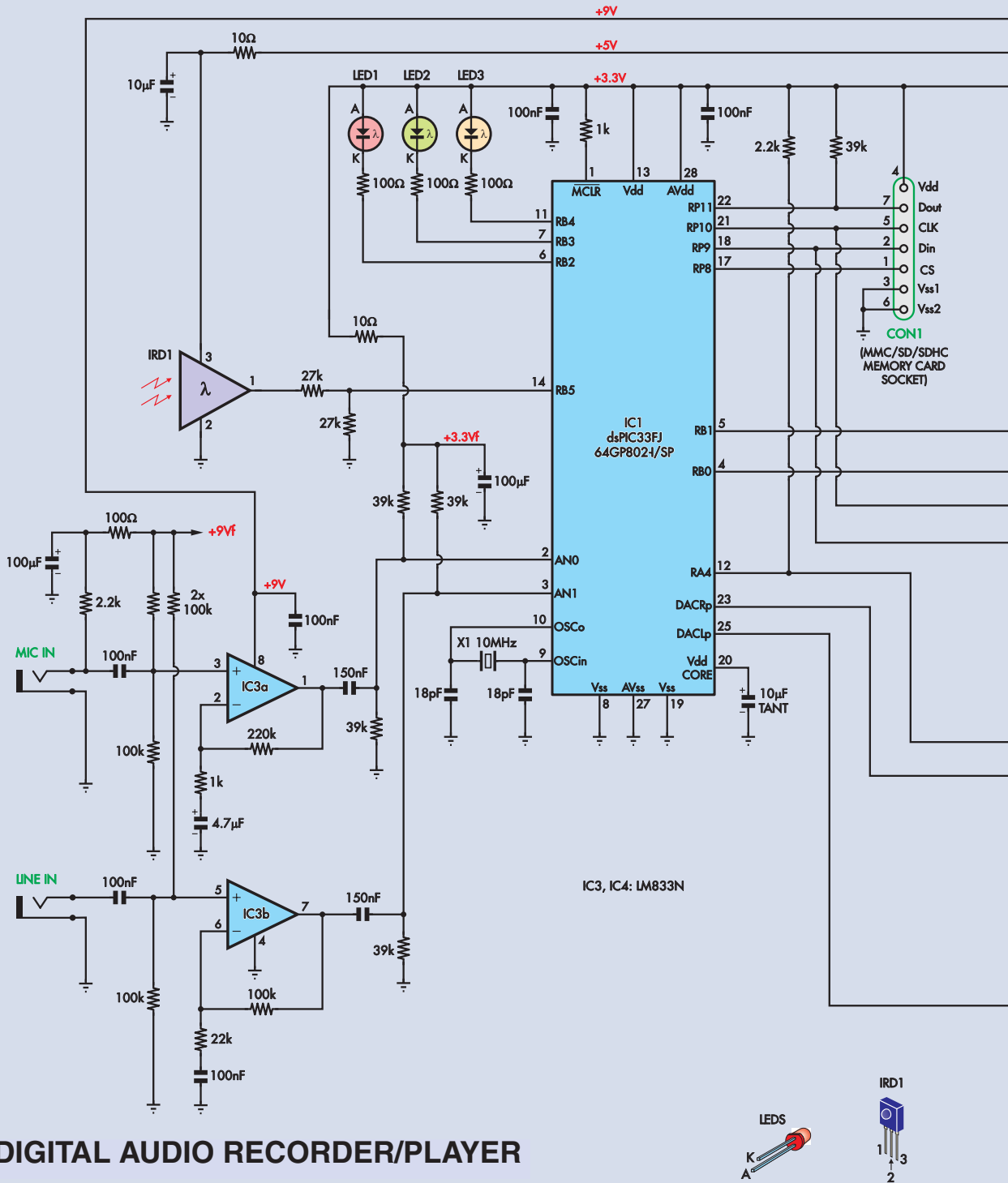Note that the infrared module works from a +5V rail, whereas the microcontroller decoding the signal runs from a 3.3V rail. The purpose of the voltage



DIGITAL AUDIO RECORDER/PLAYER

Fig.1: the circuit is based on a dsPIC33-FJ64GP802 microcontroller and a 16 × 2 LCD module. The micro scans the switch inputs via shift register IC2, drives the memory card, decodes the signals from the infrared receiver module (IRD1), writes to the LCD module and performs the ADC conversions on the analogue inputs.

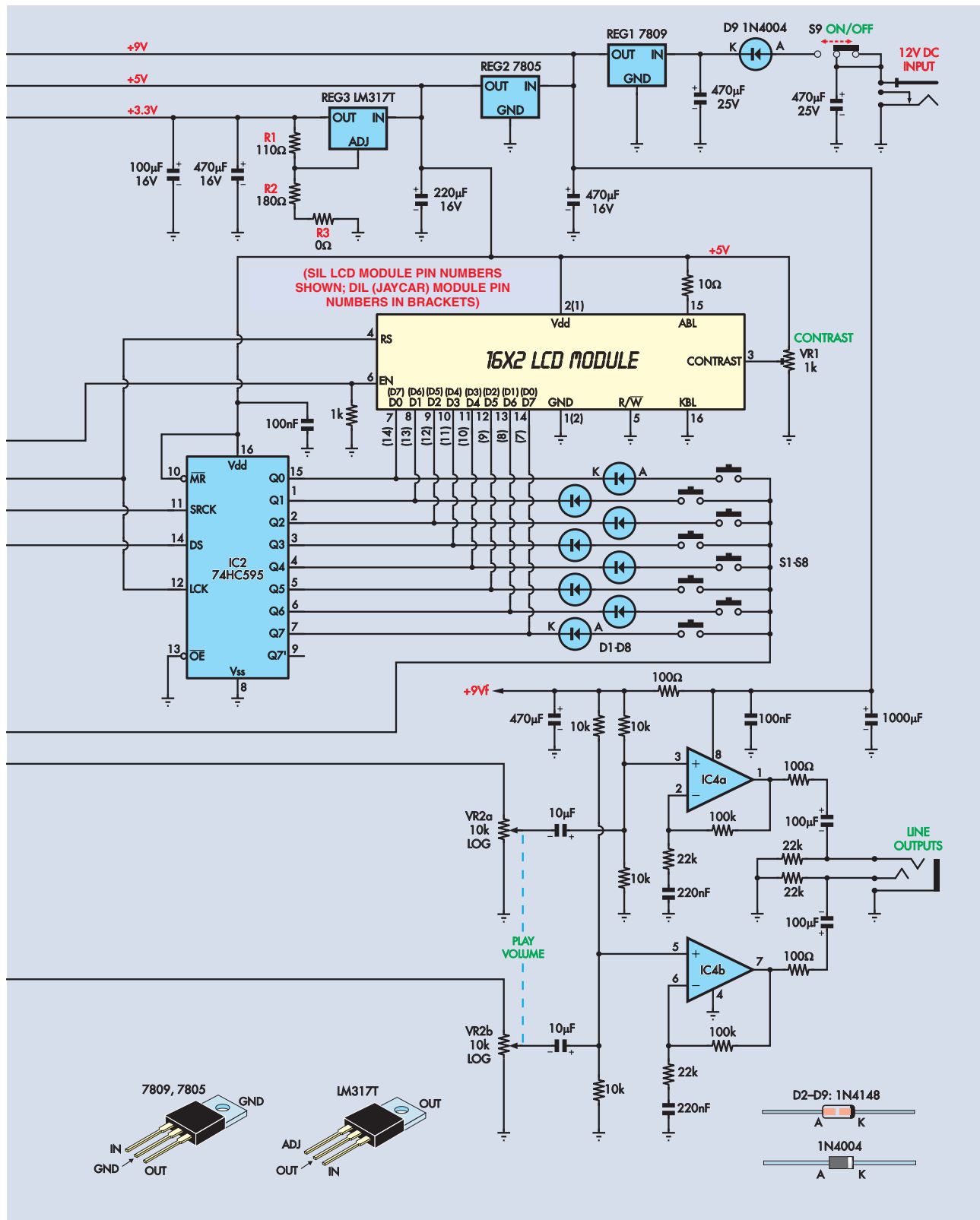

Main features and specifications

- Uses an MMC/SD/SDHC card to store audio files
- Stores mono recordings as Microsoft WAV files at 16kHz sampling rate
- Plays back Microsoft WAV files at up to 44.1kHz sampling rate
- Uses FAT/FAT32 file system (transfer files to any PC operating system)
- Has mono microphone and line inputs for recording
- Stereo socket for line output or headphone use
- 2-line LCD to display file names, show volume and other settings
- Can be controlled using on-board switches or any RC5 universal remote control
- Unit can learn remote control codes
- Signal-to-noise ratio: -70dB unweighted (22Hz to 22kHz) with respect to 1.6V RMS
- THD+N: 0.7% at 1kHz

divider is to roughly halve the signal level from the module so that it can be used with a 3.3V device.

SPI mode

As noted above, the SPI peripheral on the microcontroller is used to drive the LCD and scan the tactile switches. However, it's also used to read from and write to the MMC/SD/SDHC card.

This means that we are using the MMC/SD/SDHC card in SPI mode (MMC/SD/SDHC cards can be used in either native mode or in SPI mode). The advantage of SPI mode is that any off-the-shelf microcontroller that has an SPI peripheral can be used, making the hardware layer easy to implement.

The interface with SPI may be simple, but the penalty is slower transfer speeds. However, SPI speeds are adequate for real-time playing (and

recording) of audio. SPI also requires less interface pins and they are at a premium, as you can see.

Analogue stages

The outputs of the two internal DACs are fed via dual-gang potentiometer VR2 to an LM833N low-noise dual op amp (IC4a and IC4b). Both op amp stages are wired as AC-coupled non-inverting amplifiers with a gain of 5.5. The 220nF capacitor to ground from each feedback divider network rolls off the DC gain and sets the low-frequency response.

The outputs at pins 1 and 7 are each fed to the line output socket via a 100 Ω resistor and a 100 μ F capacitor, and can either drive stereo headphones or the line inputs of a stereo amplifier. Note that the LM833 is not really intended for driving low impedance loads, but it is a low-cost solution for a headphone output.

There are two analogue input channels, the microphone input and the line input, and they are provided by another LM833N low-noise dual op amp (IC3). IC3a is the microphone preamplifier. It is a non-inverting stage with a gain of 221 (+46dB), as set by the 220k Ω and 1k Ω feedback resistors connected to pin 2. The 4.7 μ F capacitor sets the low-frequency rolloff.

The microphone itself can be an on-board electret microphone insert or you can use a PC microphone (eg, Jaycar AM-4087) plugged into the 3.5mm stereo input jack – see photo. A 2.2k Ω resistor provides the biasing current for the electret microphone and its DC supply is decoupled from the +9Vf supply using a 100 Ω resistor and 100 μ F electrolytic capacitor.

IC3b is the line input preamplifier. It has a gain of 5.5 (+14.9dB), as set by the 100k Ω and 22k Ω feedback resistors connected to pin 6.

The outputs of both preamplifier stages are fed to the ADC inputs (AN0 and AN1) of IC1 via 150nF capacitors. Each ADC input is biased to half the +3.3V rail via voltage dividers, each consisting of two 39k Ω resistors.

Power supply

The circuit can be powered from either a 12V battery or a 12V DC plugpack supply. In operation, the 12V DC supply is fed in via on-off switch S9 and reverse polarity protection diode D9. Note that a 470 μ F 25V electrolytic capacitor is connected adjacent to the DC input socket, and is not protected from reverse polarity by D9 (this reduced the hum the most).

There are three 3-terminal regulators to provide the required supply rails. First, a 7809 9V regulator (REG1) provides the 9V rail for the analogue stages. It has 470 μ F and 1000 μ F capacitors across its output at different positions on the PC board. Further decoupling is provided by a 100 Ω resistor and 470 μ F capacitor to provide the +9Vf rail, which provides the biasing for the op amp stages.

The main +9V rail is also fed to REG2, a 7805 regulator, to derive the +5V rail. This is used to power the LCD module, shift register IC2 and the infrared receiver module (IRD1).

This +5V rail also feeds REG3, an LM317T adjustable voltage regulator. This produces the +3.3V rail that's

On-board control button functions

If you don't wish to use a remote control with this project, you can use the on-board buttons to control it. Their functions are as follows:

Functions while not playing or recording:

- S1: Random shuffle
- S2: Up
- S3: Record mic
- S4: Delete a file
- S5: Record line in
- S6: Down
- S7: N/A
- S8: Play

Functions while playing or recording:

- S1: Volume up
- S2: N/A
- S3: Choose display up
- S4: Stop
- S5: Choose display down
- S6: N/A
- S7: Volume down
- S8: Pause

MMC, SD and SDHC Memory Cards

Both MMC (MultiMedia Card) and SD (Secure Digital) cards are a type of non-volatile storage that uses FLASH memory technology. Similarly, SDHC (HC = high capacity) cards are a type of SD card with capacities between 4GB and 32GB.

All three types of cards can be used with this project. While they all look alike, MMC cards have only seven contacts, whereas SD cards have nine.

Note that miniSD and microSD cards can also be used as these are essentially SD cards with a smaller form factor. You will, however, need an external adaptor to convert them to standard size to connect to the Digital Speech Recorder.

MMC/SD/SDHC cards are commonly used in portable devices like mobile phones, computers, cameras and audio players, among others. They conveniently store a lot of data in a small form factor, consume little power and are light. Cards with increasingly larger storage capacity have been steadily appearing since their introduction in the late 1990s.

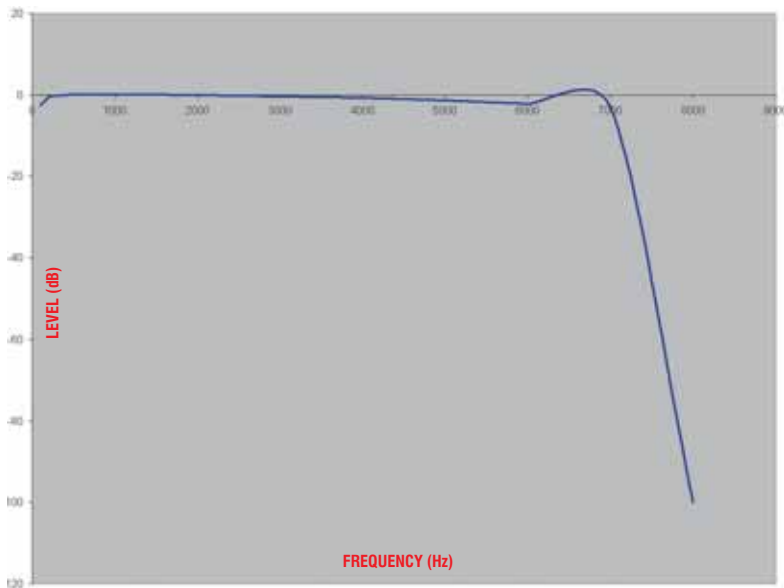


Fig.2: this graph shows the frequency response for recordings made on the Digital Speech Recorder. Note that the response is limited to half the sampling frequency, which is fixed at 16kHz for recording. The frequency response can be much wider for files recorded on a PC and transferred to the memory card.

used by the microcontroller and MMC/SD/SDHC card.

The accuracy of the +3.3V rail is important, because some MMC/SD/SDHC cards operate over quite a narrow voltage range. The firmware checks that the inserted card operates at 3.3V; so it is *crucial* that the supply rail be quite close to +3.3V.

The output voltage of REG3 is set by the divider network between its output terminal and its ADJ terminal to ground. The output is set at:

$$V_{OUT} = 1.25V \times (1 + (R2/R1))$$

With $R2 = 180\Omega$ and $R1 = 110\Omega$, we get a supply of 3.29V (close enough to 3.3V). However, the 1.25V reference in the regulator can vary between 1.2V and 1.3V.

For this reason, provision is made on the PC board for an additional resistor ($R3$) to allow you to adjust the 3.3V supply rail if necessary. We will touch on this point later in the setting-up procedure.

Software

According to which LCD module you use you will need to select the



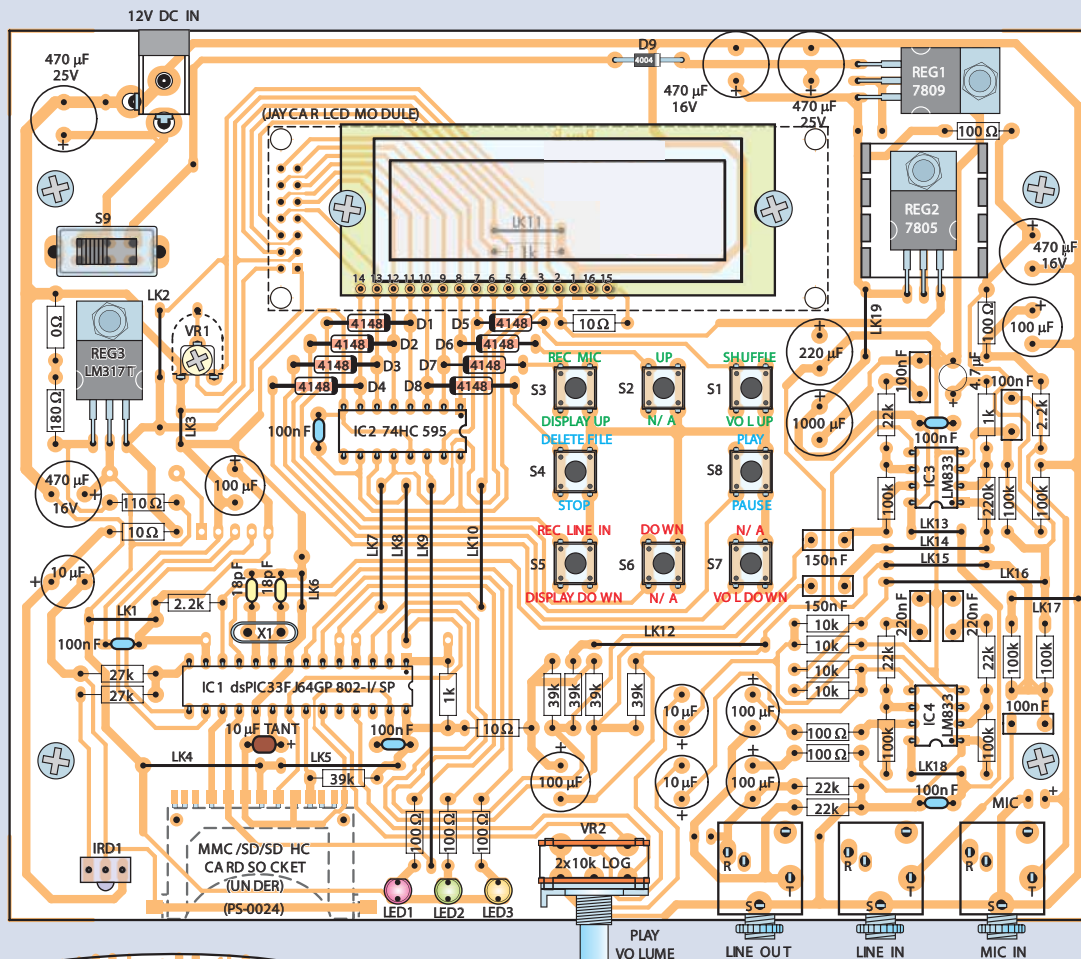


Fig.3 (above): install the parts on the PC board as shown on this component layout diagram. Take care to ensure that all polarised parts are correctly oriented and leave the ICs and the LCD module off the board until after the initial power supply checks have been completed.

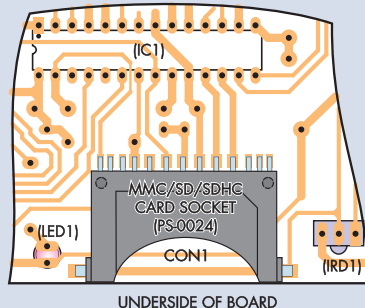


Fig.4 (left): the memory card socket (CON1) is a surface-mount device (SMD) and is installed on the underside of the PC board as shown here. Lightly solder tack one pin first, then check the socket's alignment before soldering the remaining pins.

correct code for a dual in-line (DIL) or single in-line (SIL) version of the 16-character 2-line LCD. See www.epemag.com for software.

Construction

All components are mounted on a single-sided PC board, coded 815, measuring 164mm × 136mm. This board is available from the *EPE PCB*

Service. Fig.3 shows the parts layout on the board.

The first thing to do is to carefully inspect the board for hairline cracks and for shorts between adjacent copper tracks. It's rare that you will find a fault, but it's easier to spot any problems at this stage than after the parts have been installed.


Begin the assembly by soldering in the 18 wire links. You can straighten

the link wire by clamping one end in a vice and then pulling on the other end with a pair of pliers to stretch it slightly. Don't forget link LK11 under the LCD module.

The resistors are next on the list, and again, one of these is under the LCD module. Table 1 shows the resistor colour codes, but you should also check each resistor using a DMM before

Table 2: Capacitor Codes

Value	μF Value	IEC Code	EIA Code
220nF	0.22 μF	220n	224
150nF	0.15 μF	150n	154
100nF	0.1 μF	100n	104
18pF	NA	18p	18

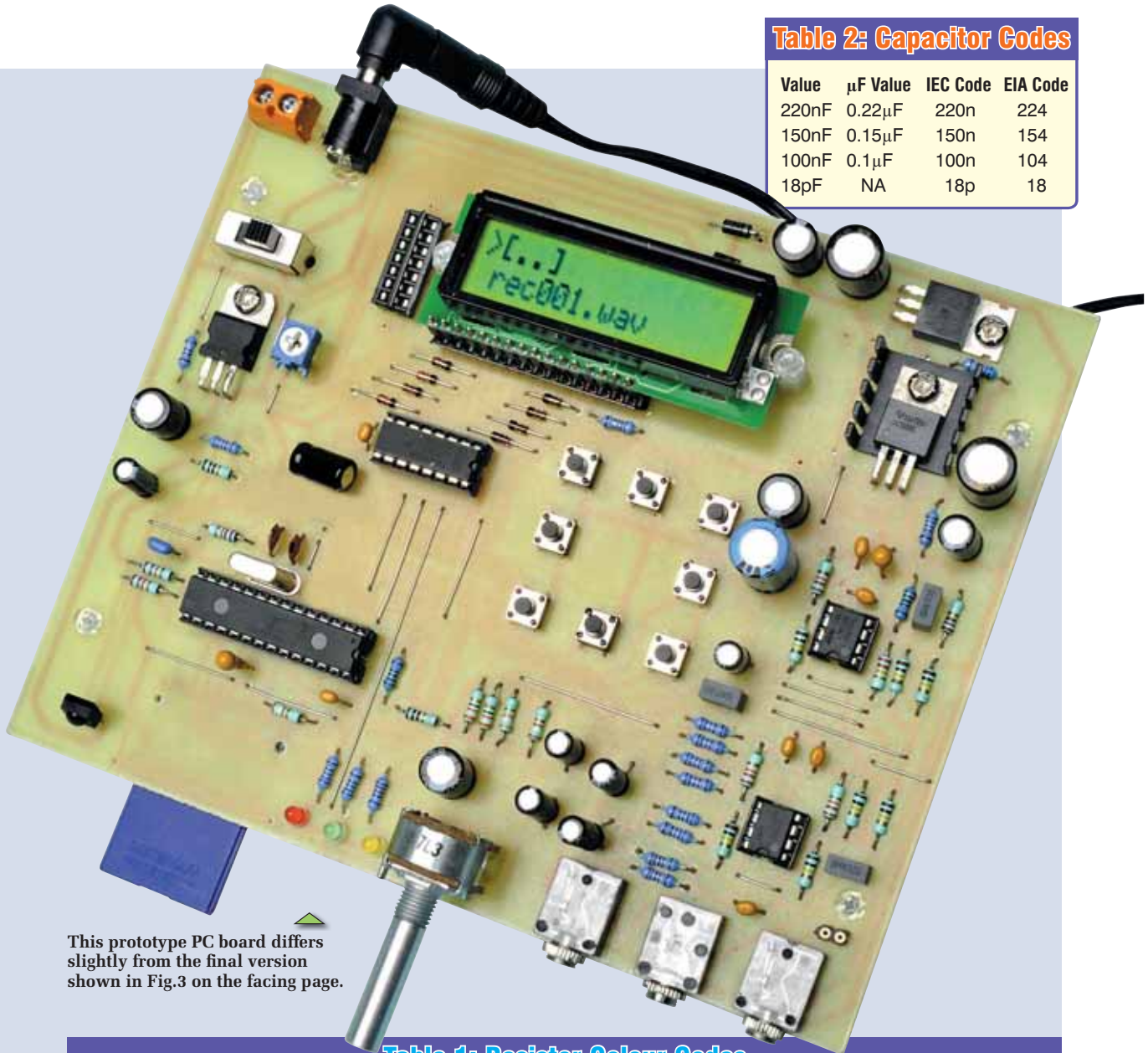

This prototype PC board differs slightly from the final version shown in Fig.3 on the facing page.

Table 1: Resistor Colour Codes

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
<input type="checkbox"/>	1	220k Ω	red red yellow brown	red red black orange brown
<input type="checkbox"/>	7	100k Ω	brown black yellow brown	brown black black orange brown
<input type="checkbox"/>	5	39k Ω	orange white orange brown	orange white black red brown
<input type="checkbox"/>	2	27k Ω	red violet orange brown	red violet black red brown
<input type="checkbox"/>	5	22k Ω	red red orange brown	red red black red brown
<input type="checkbox"/>	4	10k Ω	brown black orange brown	brown black black red brown
<input type="checkbox"/>	2	2.2k Ω	red red red brown	red red black brown brown
<input type="checkbox"/>	3	1k Ω	brown black red brown	brown black black brown brown
<input type="checkbox"/>	1	180 Ω	brown grey brown brown	brown grey black black brown
<input type="checkbox"/>	1	110 Ω	brown brown brown brown	brown brown black black brown
<input type="checkbox"/>	7	100 Ω	brown black brown brown	brown black black black brown
<input type="checkbox"/>	1	0 Ω	black	black

Transferring files and recording to the memory card

To transfer audio files from a PC to the memory card, you will need a low-cost SD/SDHC/MMC-card reader. The one shown in the accompanying photo is available from Jaycar for a few pounds (Cat No: XC-4756).

Note that before copying the files (eg, music tracks) to the MMC/SD/SDHC card, they must first be converted to WAV format. This can be done using a freeware sound editor program called 'Audacity' – see panel on page 13.

As indicated earlier, you can also directly record files to a memory card in the Digital Audio Recorder. Basically, you have two choices when making recordings: either use the microphone input or feed signals in via the recorder's line input.



When using the microphone input, you can use either an onboard electret microphone (see photo), or you can plug an electret microphone into the MIC In socket. Be sure to disconnect the on-board microphone if you are using an external one.

Note that the microphone and line inputs differ in the gain of their respective preamplifier stages, so be sure also to choose the correct input.

soldering it to the board. Resistor R3 can be either a 0Ω resistor or you can simply install a wire link (**note: this 0Ω resistor may have to be changed later – see section on trimming the 3.3V rail**).

Follow these parts with the diodes and the infrared receiver (IRD1). Note that D9 is a 1N4004 type, while the remaining eight diodes (D1-D8) are all 1N4148 signal types. These diodes must all be installed with the correct orientation (the striped end is the cathode (K)), while IRD1 must go in

with its domed lens facing outwards.

The three LEDs (LED1 to LED3) can be installed at this stage as well. Make sure that these are oriented correctly and match the colours shown on Fig.3.

Installing the regulators

The three TO-220 regulators (REG1 to REG3) can now go in. As shown, these are all mounted horizontally, with their leads bent down at right-angles about 6mm from their bodies. In addition, the 7805 regulator (REG2) must be fitted with a mini finned heatsink

Defining the remote control codes

If you wish to use a remote control with this unit, you will need an RC5-compatible remote. RC5 is an infrared communications protocol that was initially developed by Philips and is used by many Philips appliances.

This means that if you have a universal remote, there's a good chance it will work if you set it to control a Philips appliance. For example, we tested the project with the Jaycar AR-1726 remote and can confirm that it works.

Setting up the remote is straightforward. You start by pressing the S2 and S6 (UP and DOWN) buttons together

while booting the recorder, to enter the remote control programming menu. You are then prompted to press the key you want to define for that function.

For example, you may be prompted to 'Press Play' and you then simply press the relevant button on the remote which is to be assigned that function.

A recommended set-up using the AR-1726 Remote from Jaycar is shown in Table 3. It should be set to the VCR 917 code, which corresponds to the default programmed into the recorder's firmware.



This larger-than-life size view shows how the card reader is mounted on the copper side of the PC board.

before it is bolted down. Each regulator is secured using an M3 × 5mm machine screw and nut.

The next step is to install the four IC sockets. If you don't have a 28-pin 0.3-inch socket (or have a 0.6-inch socket instead), you can cut it down the middle and install the two strips for IC1. Place each socket so that its notch matches that shown on the overlay (Fig.3). This will make it easier when it comes to installing the ICs later on.

You will also need to cut down a 40-pin IC socket to make the connector for the LCD module. If you are using the DIL (Jaycar QP-5515) module, you will need two rows of seven pins and they must be installed with what were originally their outside edges touching in the middle, otherwise they won't fit in place.

Now move on to the capacitors. There are four different types: monolithic, ceramic, MKT and electrolytic. The first three types can go in either way around, but the electrolytic capacitors are polarised and each must be oriented as shown in Fig.3. The negative terminal is marked on the body of each capacitor.

The switches can go in next. The power switch (S9) is a DPDT slide type, while the rest (S1 to S8) are momentary pushbutton tactile types. Note that these tactile switches are not symmetrical in the horizontal and vertical directions, being slightly longer in the vertical direction.

It's just a matter of installing them with their terminals positioned as shown (they won't fit the wrong way).

Table 3: Recommended key assignments for Digitech AR-1726 remote control

Button	Function(s)	Recommended Key Definitions for the Digitech AR-1726 Remote
0	Unused	Press '0'
1	In Triggered mode, used to play file rec001.wav	Press '1'
2	In Triggered mode, used to play file rec002.wav	Press '2'
3	In Triggered mode, used to play file rec003.wav	Press '3'
4	In Triggered mode, used to play file rec004.wav	Press '4'
5	In Triggered mode, used to play file rec005.wav	Press '5'
6	In Triggered mode, used to play file rec006.wav	Press '6'
7	In Triggered mode, used to play file rec007.wav	Press '7'
8	In Triggered mode, used to play file rec008.wav	Press '8'
9	In Triggered mode, used to play file rec009.wav	Press '9'
VOL UP	In Normal mode, used to select a file to play. While playing, used to increase the volume	Press 'Vol Up'
VOL DOWN	In Normal mode, used to select a file to play. While playing, used to decrease the volume	Press 'Vol Down'
CH UP	While playing, used to select what is displayed in the second line on the LCD module	Press 'Ch Up'
CH DOWN	While playing, used to select what is displayed in the second line on the LCD module	Press 'Ch Down'
MENU	Used to delete the selected file; confirmation is requested	Press 'Menu'
STOP	Used to stop a playing file or a recording	Press 'Stop'
PLAY	Used to play the selected file	Press 'Play'
PAUSE	Used to pause a playing file or a recording	Press 'Pause'
FAST FWD	Used to start random shuffle	Press 'FF'
REWIND	Unused	Press 'Rewind'
RECORD	Used to initiate a recording from the microphone input	Press 'Rec'
OK	Unused	Press 'Ok'
EXIT	Unused	Press 'Exit'
LINE	Used to initiate a recording from the line input	Press '->'

The larger items can now be installed. These include trimpot VR1, dual-gang potentiometer VR2, the DC connector and the three 3.5mm stereo jack sockets. If you intend using an electret microphone, then you will also have to install a 2-pin socket strip to accept its connecting leads. Note that the electret microphone should *not* be connected while using an external microphone.

Installing the card socket

The memory card socket is mounted on the underside of the PC board – see Fig.4. This is an SMD, so you must carefully position it over its pads and solder one of the pins first to anchor it in position. Once that is done, you can solder the rest of the pins. Note that there are two mounting terminals on either side of the device that must

also be soldered to matching pads near the front edge of the board (see Fig.4 and photo).

The initial assembly can now be completed by fitting four M3 x 12mm nylon spacers to form the mounts for the PC board. **DO NOT fit the ICs or the LCD panel at this stage. These parts are installed only after the supply rails have been checked and that step comes next.**

Power supply checks

You will need a 12V DC 300mA (or higher) regulated plugpack with a 2.5mm connector to power this project.

Before applying power, make sure that the LCD is unplugged and that no ICs have been fitted. That done, apply power and move switch S9 to its ON position (ie, to the right). Now,

using a DMM, measure the voltage between the OUT and GND terminals of REG1 – you should get a reading of 9V. If not, switch off immediately and check for supply errors. If no voltage is present, then diode D9 may be reversed or the supply polarity could be incorrect.

Assuming all is OK, check the voltage on the OUT terminal of REG2. This time, you should get a reading of 5V.

Finally, check the voltage on the OUT terminal (ie, the centre terminal) of REG3. It should be close to 3.3V. If any of the above voltages is incorrect, disconnect power immediately and check your work.

Note: the OUT terminal of REG3 is the centre lead of the device. By contrast, the OUT terminal of both REG1 and REG2 is one of the outside leads – see Fig.1 for the pinouts.

Constructional Project



Play: 02:08
Vol.: 16

Screen grab showing the playing view. The time since the beginning of the track and the volume level are shown. Note that the time will blink on and off if track is paused.



>Radiohead.wav
The Beatles.wav

Screen grab showing file selection. You can scroll through the file system by using the Up and Down buttons and press Play when you are satisfied with your selection. The currently selected file is shown with '>'.
The previous directory is shown as '[..]'. You can press Play or Record to enter a directory. Note that directory names are enclosed in square brackets to differentiate them from normal files.



>[..]
soundEffect.wav

The previous directory is shown as '[..]'. You can press Play or Record to enter a directory. Note that directory names are enclosed in square brackets to differentiate them from normal files.



[..]
>[Sounds]

The playing view. The time since the beginning of the track, the sampling rate and whether the track is mono or stereo are shown. This view shows that the sampling rate is 44.1kHz and it is a stereo track that's being played.



Play: 00:10
S/R.: 44100 STER



Record: 01:50
Ch.: Mic

The recording view. The time since the beginning of the track, the sampling rate and whether the track is mono or stereo are shown. This view shows that the sampling rate is 16kHz and that it is a mono track that's being recorded.



Record: 01:50
S/R.: 16000 MONO



Record: 00:15
Ch.: Line

When playing a random selection through shuffle, this is the play screen shown. Notice the 'RND' indicator that's only shown in this mode.



Play: 01:30 RND
Vol.: 12



Size(MB): 995.3
Free(MB): 328.0

A screen readout showing the size of the inserted memory card and the remaining free space on it. This screen is displayed once on startup.

Fig.5: this diagram show some typical displays on the LCD, together with accompanying explanations. The unit shows file names, time elapsed while playing, the recording source, volume, sampling rate, card size, free space and other information.

Trimming the 3.3V rail

If the 3.3V rail is more than 3.4V or less than 3.2V, you will need to change one or both of the values for R2 and R3. For example, if the voltage from REG3 is 3.17V, you will need to install a 10Ω

resistor for R3 and this should bring it pretty close to 3.3V.

Alternatively, if the output voltage is 3.41V, you should change the value of R2 to 160Ω and R3 to 10Ω, giving a total value for R2 + R3 = 170Ω (or you

could use 150Ω for R2 and 22Ω for R3). Again, this should bring the voltage from REG3 pretty close to 3.3V.

If all three supply voltages are now close to their nominal values, you can disconnect power and insert the four ICs in their sockets. These ICs should all be oriented correctly of course.

Installing the LCD module

The LCD module can now be installed. The SIL module is secured to the board on two M3 × 9mm tapped nylon pillars, as shown in Fig.3, while the alternative DIL module is secured using four M3 × 9mm tapped nylon pillars, ie, one at each corner (all the necessary mounting holes are on the PC board).

Your Digital Speech Recorder and Audio Player is now completed and ready for use.

You should transfer the audio WAV files you wish to play to an MMC/SD/SDHC card using your PC or Mac, making sure the card is formatted with a FAT/FAT32 file system. Once the memory card has been inserted in its socket on the underside of the PC board, you can apply power. The firmware should display the version on the LCD panel and then compute the free size on the memory card. Your player is then fully operational.

Configuring the unit

The Digital Speech Recorder can be used in either of two modes: normal or triggered.

By default, the unit works in normal mode. However, if you wish to configure it for triggered operation, you simply create a file 'trigger.txt' and place it in the root folder of the memory card you are using. You can do this using a card reader and a PC. The file need not contain anything – it just needs to be there (as an empty file).

The microcontroller will look for this file on boot up and switch the mode of operation to triggered if it is present. On the other hand, if this file is absent, the recorder boots for normal operation.

The differences between these two modes of operation are explained below.

Normal mode

In Normal operation, you begin by using the UP and DOWN buttons (S2 and S6) or the VOL UP and VOL DOWN

Configuring the software to suit the LCD module

If you look closely at the PC board for this project, you will notice that the DIL and SIL LCD modules are wired with their data lines 'transposed'. Basically, the D0 line on the SIL module is connected to the D7 line of the DIL (Jaycar) module, while the D1 line on the SIL module is connected to the D6 line of the DIL module and so on. This was done to simplify the PC board layout.

It means, however, that the firmware must drive these two LCD modules differently. As a result, the microcontroller must either be programmed with a SIL version if you are using the SIL LCD module or with a DIL version if you are using the DIL LCD module.

You can also toggle either version to drive the alternative module. This is done by holding down buttons S4 and S8 together while applying power.

Note that this needs only to be done once, as the new setting is stored in non-volatile memory.

If nothing appears on the LCD at initial switch-on, try adjusting the contrast (VR1). If that doesn't work, you may have the wrong software for your particular LCD module, so switch off and reapply power while holding down S4 and S8.

If you buy a kit, then the default will be correct for that kit supplier's LCD module.

buttons on the remote control to scroll through the file system on the card.

When you've selected the correct file, you simply press PLAY (S8) to play it. A screen grab showing a typical view of the file system is shown in Fig.5 (second from top). Of course, only two files are ever shown at any one time. A directory is indicated by its name being enclosed in square brackets. Press PLAY to enter a directory. The previous directory is shown as '[..]' – see Fig.5.

The delay in playing a new file is very small, of the order of a fraction of a second. This makes this project perfect for playing sound effects on demand.

Pressing SHUFFLE (S1) or FAST FF on the remote enters random shuffle mode. In this mode, there is an 'RND' indicator on the display and a random selection of tracks (eg, songs) is continuously played from the root directory. You exit this random shuffle mode by pressing STOP (S4).

Pressing REC MIC (S3) or REC LINE-IN (S5) starts a recording from the microphone or line input respectively. Alternatively, you can press the Record or Line buttons on the remote.



This close-up view shows how an on-board electret microphone can be installed (it plugs into a 2-pin header near the external microphone socket – but watch the polarity). Do NOT install this if you intend using an external mic.

When recording a file, the filename will be of the form rec???.wav with ??? a string of three decimal digits. The filename recorded will be shown when the recording is ended using either the STOP button (S4) on the board or the STOP button on the remote.

In practice, it's more complicated 'in the telling' than 'in the doing'. A few minutes spent pressing buttons will quickly reveal how it works.

Triggered Mode

In Triggered mode, you simply press one of the eight buttons to play the file

'rec00?.wav' where '?' is a digit from 1 to 8. For example, pressing S3 will play the file 'rec003.wav'.

You can also press the corresponding digits on the remote control to play each of these eight files.

Basically, the Triggered mode is useful for quickly playing back one of eight tracks (or messages) once they have been recorded. After recording the messages (using Normal mode), it's just a matter of copying a file called 'trigger.txt' to the root folder of the card as detailed above and restarting the Digital Speech Recorder. **EPE**

**TO ADVERTISE IN
EVERYDAY PRACTICAL ELECTRONICS**

**PLEASE CONTACT
Stewart Kearn on**

01202 880299

or email

stewart.kearn@wimborne.co.uk

The coming revolution

TechnoTalk

Mark Nelson

You can't buy memristors (yet) but you might well wish to. Memristors offer greater memory storage than current semiconductor solutions, require less energy and occupy a smaller footprint. In time, they could also substitute for the billions of transistors found in a modern microprocessor. In fact, they're every designer's dream, as Mark now explains.

EVERY so often, fantastic futures are forecast for new electronic technologies. Some make it big time – like the transistor, CMOS and surface-mount components – while others don't.

If nuvistors, fetrons, tunnel diodes and fluidics don't ring a bell with you, it's really little wonder, since they failed to fulfil their expectations. But currently there's universal interest in memristors, so let's concentrate on them.

Missing link discovered

The memristor promises to create a semiconductor revolution as significant as the transistor did in the 1950s. Observers consider it to be the 'missing link' in electronics, the up-to-now uninvited complement to the resistors, capacitors and inductors used in well-nigh every electronic product.

In essence, the memristor is a resistor with memory; applying an electric voltage to it will alter the degree to which it impedes electric current. And there's a bonus: a memristor can 'remember' that factor, even after the power is turned off.

This makes it a prime contender for memory that requires minimal energy to store information, just like the non-volatile Flash memory used currently. Unlike Flash, however, the memristor will offer significantly greater memory storage, run ten times faster and require ten times less energy and space.

In principle, the memristor could also be used in logic circuits, substituting for the billions of transistors in a modern microprocessor, but this will come only after significant further development. Other uses will doubtless be found, for experience tells us that the most valuable applications will most likely come from a young student who learns about these devices and then has an inspiration for something totally new.

Simpler in operation

In a *BBC News* interview, Steve Furber, professor of computer engineering at the University of Manchester, stated: 'Memristors are much simpler in principle than transistors. Because they are formed as a film between two wires, they don't have to be implanted into the silicon surface – as do transistors, which form the storage locations in Flash – so they could be built in layers in 3D. Of course, the

devil is in the detail, and I don't think the manufacturing challenges have been fully exposed yet.'

This, of course, is true, and there's no way to compress the development time of a new technology. 'New' is a relative term, and the memristor model was first proposed by Leon Chua as long ago as 1971, when there was no method of achieving proof of concept of what he had already named the 'missing circuit element'.

The first actual memristor was demonstrated in April 2008 by electronics giant Hewlett Packard, but the real 'coming of age' occurred last year when HP and Korean memory manufacturer Hynix announced a joint effort to develop memristor memory chips. By 2013, the first products should be ready, known as resistive random access memory (ReRAM). This is designed to replace Flash memory and can also substitute for DRAM and hard drives, making it a new universal storage medium.

How does it actually work?

The Wikipedia definition explains that a memristor is a passive two-terminal electronic component whose resistance depends in some way on the amount of charge that has flowed through the circuit previously. When current flows in one direction through the device, the resistance increases; and when current is reversed, the resistance decreases, although never to zero or a negative level. The component retains its final resistance after the current ceases and when the flow of charge starts again, the resistance of the circuit will be the same as when it was last active.

It's these tiny read charges that provide access to a 'history' of the voltage applied previously. You might argue that batteries have memristance too, but they are not passive devices.

Machines that learn

In the longer term, memristors might enable computers to 'learn' what you want from them. HP scientist Jianhua Yang says, 'Any learning a computer displays today is the result of software. What we're talking about is the computer itself – the hardware – being able to learn.'

'This is not to say the computer would function like a human brain, but it could gain pattern-matching abilities, which

would let it adapt its user interface based on how you use it. These same abilities make it ideal for such artificial intelligence applications as recognising faces or understanding speech.'

The name says it all

The name memristor is short for 'memory resistor', so named because its resistance varies according to its 'memristance' function, providing access to a 'history' of previously applied voltage stored in minute read charges remaining in the device. The name, it has to be said, is more meaningful to the average person than 'transistor'.

Most people have a rather hazy idea of how and why the transistor got its name, so it's best to go to the man who named the device, John R Pierce of Bell Labs. He was the person who supervised the team which built the first transistor there.

Interviewed on the Public Broadcasting System in the USA, Pierce stated: 'The way I provided the name was to think of what the device did. And at that time it was supposed to be the dual of the vacuum tube. The vacuum tube had transconductance, so the transistor would have 'transresistance'. And the name should fit in with the names of other devices, such as varistor and thermistor. [So] I suggested the name *transistor*.'


Next step

Further development of memristors will rely in part on developing the best material implementation. HP is not alone in this quest, and IBM, HRL, Samsung and other research labs are also developing components based on a titanium dioxide substrate. However, manganite polymers and other substances are also being explored.

In 2009, Leon Chua, father of the memristor, wrote a paper with two co-authors that extended the notion of memristive systems to capacitive and inductive elements. It proposed the possibility of memcapacitors, and meminductors with memory properties dependant on the state and history of the system.

Whatever next?

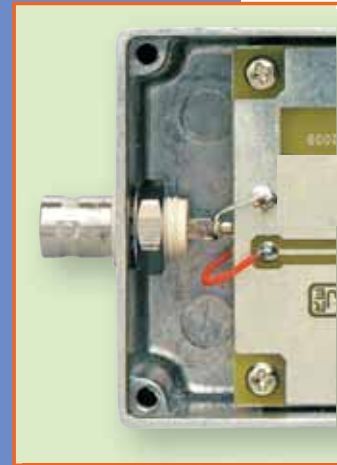The memristor has its own website at: www.memristor.org, while HP has produced a handy FAQ sheet that you can read at: www.hpl.hp.com/news/2008/apr-jun/memristor_faq.html.



By JIM ROWE

Input attenuator for the Digital Audio Millivoltmeter

If you'd like to be able to use our Digital Audio Millivoltmeter to measure AC voltages up to 140V RMS, this add-on project is the answer. It's a simple switched input divider that lets you add 40dB, 20dB or 0dB of attenuation ahead of the meter at the touch of a knob.

THE *Digital Audio Millivoltmeter* described in the March 2011 issue of *EPE* can measure signals over a 79dB range, from about $160\mu\text{V}$ (-76dBV) up to 1.41V RMS ($+3\text{dBV}$). This is fine for low-level measurements, but it does make the meter unsuitable for measuring higher level signals.

With the benefit of hindsight, we could have built a switched input divider right into the meter itself. However, this would have involved a tight squeeze to fit the additional switch and components into the PC board and box, and the front panel would have been very crowded as well.

To increase the measured voltage range, we have designed this little 'outboard' switched input attenuator.

It's designed to be connected ahead of the Digital Audio Millivoltmeter's unbalanced input via a short BNC cable.

There's no need for cable swapping to remove it when you are measuring small signals because it incorporates a 'straight through' (0dB) switch position. So, once it's built and connected to the input of the meter, its own input connector effectively becomes the meter's unbalanced input.



Simple circuit

There's very little in the attenuator, as you can see from the circuit schematic (Fig.1). A 2-pole switch is used to switch the input signal either straight through to the output (0dB) or via one of two taps on the resistive divider.

The upper tap gives a 10:1 division (-20dB), while the lower tap gives a 100:1 division (-40dB). As a result, the first position of the switch leaves the millivoltmeter's own ranges unchanged, while the next position effectively subtracts 20dB from the meter readings, and extends its 'full scale' reading to 14.1V RMS or $+23\text{dBV}$.

Similarly, the third switch position subtracts 40dB from the meter readings, and extends its measurement capability out to 141V RMS ($+43\text{dBV}$).

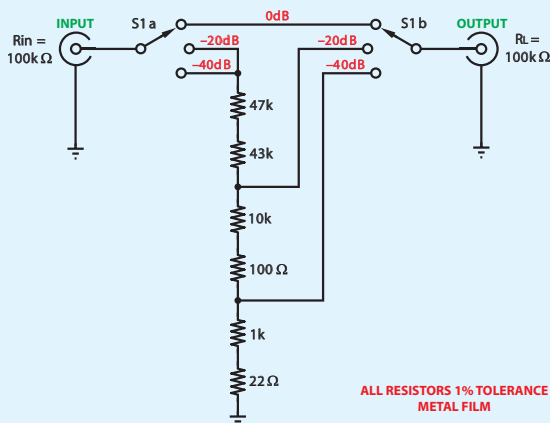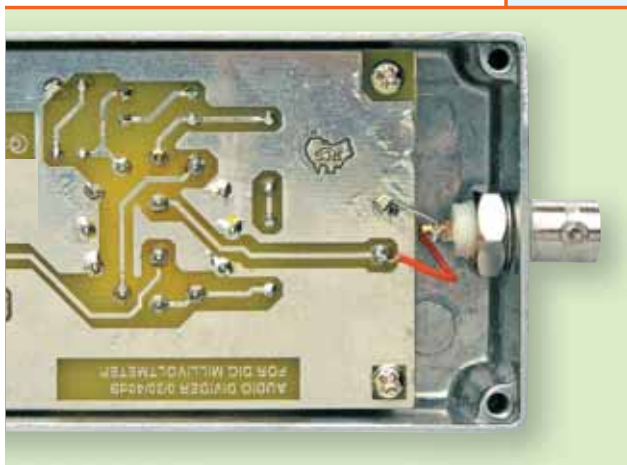Note that the meter readings don't take this added attenuation into account, because there's no way for the PIC micro inside the meter to know how much extra attenuation is being applied. So you have to add the 20dB



AUDIO INPUT DIVIDER 0/-20/-40dB

Fig.1: the circuit is simply a switched resistive attenuator network, with double-pole switch S1 selecting between the 0dB, -20dB (10:1 division) and -40dB (100:1 division) positions.

or 40dB to the readings yourself and/or multiply the millivolt readings by either 10 or 100 as appropriate. That doesn't involve a great deal of mental maths though.

Now, before you ask, we'll clear up a few points about the resistor values used in the divider. Do they make allowance for the shunting effect of the meter's own input resistance? Yes, they do.

If you care to work it out, you'll find that the division ratios of 10:1 and 100:1 are only correct when the output of the attenuator is loaded with 100kΩ (ie, the input resistance of the millivoltmeter). The ratios are then within 0.1% of their nominal 10:1 and 100:1 values – which is close enough considering we are using 1% tolerance resistors.

The input resistance of the input divider/millivoltmeter combination also remains very close to the

nominal 100kΩ figure for the meter itself. Clearly, it's exactly the same in the 0dB switch position, but even in the other two positions it is still within 2%.

Construction

Most of the parts are mounted on a small PC board measuring 76mm × 53.5mm and coded 811. This board is available from the *EPE PCB Service*. The board is designed to fit inside a standard small diecast aluminium box measuring 111mm × 59mm × 30mm. This box provides shielding and physical protection. It also matches the larger diecast box used for the millivoltmeter itself.

There's plenty of space inside the box for the BNC input and output connectors, which are both insulated single-hole mounting types. As shown in one of the photos, the board assembly itself mounts centrally in the bottom of the box and is secured via four M3 × 15mm tapped spacers. Note that metal spacers and screws must be used to secure the board, because one of the spacers is used to connect the box to the PC board earth copper.

Note, the other three spacers and screws must NOT make contact with the board's earth copper. This is done to prevent the formation of earth loops.

Fig.2 shows the parts layout on the PC board. There's just the six resistors


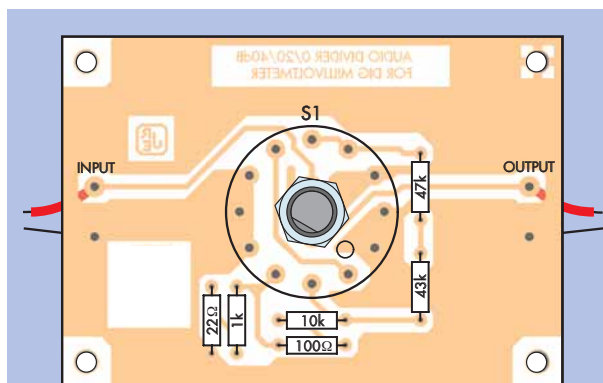
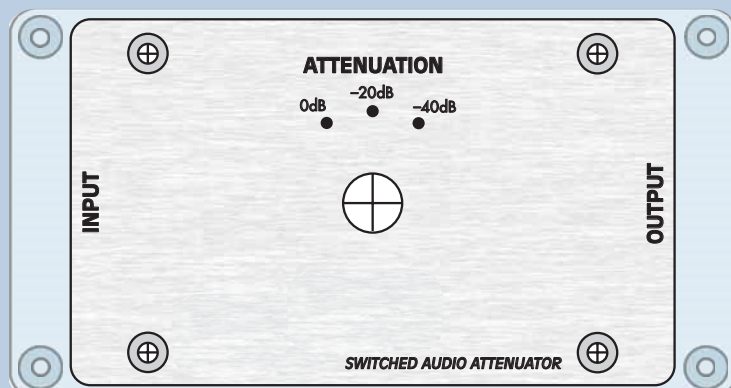


Fig.2 (left): position the parts on the PC board as shown here and install PC stakes on the copper side at the external wiring points. The completed board (right) – should only take a few minutes to assemble.

Constructional Project

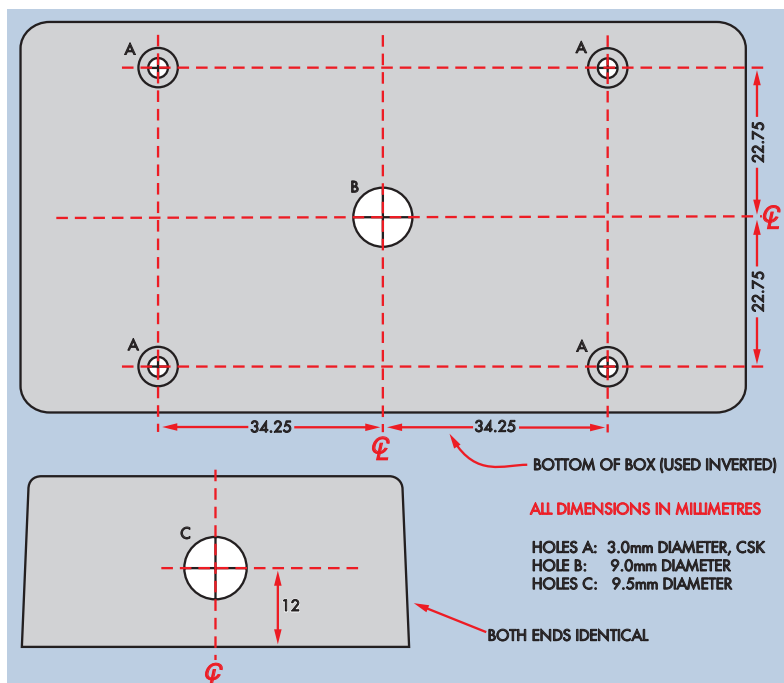

Parts List

- 1 PC board, code 811, available from the *EPE PCB Service*, size 76mm × 53.5mm
- 1 diecast aluminium box, size 111mm × 59mm × 30mm
- 1 2-pole 6-position rotary switch, with adjustable end-stop
- 1 small instrument knob
- 2 BNC connectors, insulated single hole mounting
- 4 M3 × 15mm tapped metal spacers
- 4 M3 × 6mm screws, pan head
- 4 M3 × 6mm screws, countersink head
- 4 1mm PC board terminal pins
- 4 stick-on rubber feet
- Light-duty hook-up wire

Resistors (0.25W 1%)

- 1 47kΩ
- 1 43kΩ
- 1 10kΩ
- 1 1kΩ
- 1 100Ω
- 1 22Ω

and the switch, so assembly will only take a few minutes to complete. Cut the switch shaft to a length to suit the knob before fitting it to the PC board.

The connections between the input and output BNC connectors and the PC board are made via short lengths of hookup wire. We fitted PC board pins to the board (from the copper side) to make these connections a little easier.


Wiring up the attenuator should be very easy – see Fig.2 and Fig.5. The whole job should take you no more than an hour or so, including the time to drill and ream the holes in the box.

Boxing up

The drilling details for the case is shown in Fig.3. **Note that the case is used inverted, so that the base becomes the front panel (do NOT drill the lid).** Use a small pilot drill to start

Table 1: Resistor Colour Codes

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
□	1	47kΩ	yellow violet orange brown	yellow violet black red brown
□	1	43kΩ	yellow orange orange brown	yellow orange black red brown
□	1	10kΩ	brown black orange brown	brown black black red brown
□	1	1kΩ	brown black red brown	brown black black brown brown
□	1	100Ω	brown black brown brown	brown black black black brown
□	1	22Ω	red red black brown	red red black gold brown

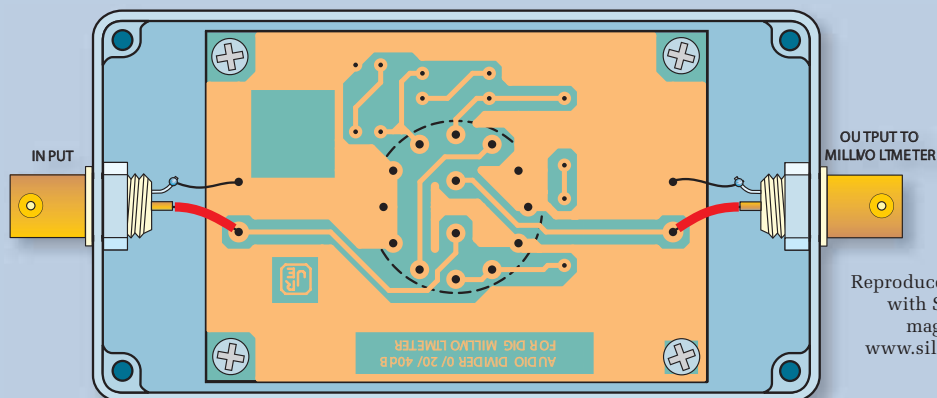

Reproduced by arrangement
with SILICON CHIP
magazine 2011.
www.siliconchip.com.au

Fig.5: the PC board is fitted with M3 × 15mm tapped spacers and mounted upside down in the base of the case. The BNC sockets are then wired by running leads to the PC stakes on the board.

the larger holes, then carefully enlarge them to the correct size using a tapered reamer.

Fig.4 shows a full-size artwork for the attenuator's front panel. It can be photocopied onto a piece of adhesive-backed label. This can then be covered with self-adhesive clear plastic film (to resist discolouration due to finger grease) and attached to the base (use a thin smear of silicone sealant to attach the label if it doesn't have an adhesive backing). Cut out the holes for the switch and the PC board mounting screws using a sharp hobby knife.

Next, move the end-stop washer on the rotary switch to the correct location for three switch positions. Do not initially refit the nut after doing this – just refit the lockwasher for the time being (the combined height of the switch and lockwasher above the PC board is very close to 15mm, so they match the four M3 × 15mm tapped mounting spacers).

Countersink-head M3 × 6mm screws should now be used to secure the four M3 × 15mm tapped spacers to the base. The PC board can then be fitted in position and secured using M3 ×

6mm pan-head screws. That done, fit the nut to the switch and attach the knob to the switch shaft.

Finally, secure the lid in position (this now becomes the base of the case). It's also a good idea to fit four small adhesive-backed plastic or rubber feet to the box lid, to prevent scratches to bench-tops or any other surface the device is placed on.

That's it. Once your add-on attenuator is finished, your Digital Millivoltmeter will be able to make measurements over a 96dB range: from 160µV to just over 140V RMS. **EPE**

EPE BINDERS

KEEP YOUR MAGAZINES SAFE – RING US NOW!

This ring binder uses a special system to allow the issues to be easily removed and re-inserted without any damage. A nylon strip slips over each issue and this passes over the four rings in the binder, thus holding the magazine in place.

The binders are finished in hard-wearing royal blue PVC. They will keep your issues neat and tidy but allow you to remove them for use easily.

The price is £7.95 plus £3.50 post and packing. If you order more than one binder add £1 postage for each binder after the initial £3.50 postage charge (overseas readers the postage is £6.00 each to everywhere except Australia and Papua New Guinea which costs £10.50 each).

Send your payment in £'s sterling cheque or PO (Overseas readers send £ sterling bank draft, or cheque drawn on a UK bank or pay by card), to:

Everyday Practical Electronics, Wimborne Publishing Ltd,
113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU
Tel: 01202 880299. Fax: 01202 843233
E-mail: editorial@wimborne.co.uk
Web site: <http://www.epemag.com>

We also accept card payments, Mastercard, Visa, or Maestro. Send your card number and card valid from and expiry date plus Maestro Issue No. and the security code on the back of the card with your order.



A Deluxe 3-channel UHF Rolling Code Remote Control

This high-security 3-button UHF transmitter and receiver can be used for keyless entry into homes and commercial premises, and for controlling garage doors and external lighting.

Three separate outputs on the receiver can be used to activate various electrical devices, such as a door strike, a motorised garage door and 230V AC lights. Up to 16 transmitters can be used with one receiver, so it's even suitable for a small business.

MAYBE you have been thinking of building a low-cost remote switching circuit, but have been put off the simpler ones because of concerns over security. If so, then this project is for you. It's a completely new design for applications where you want high security and the ability to control more than one device.

For example, you may want to control a garage door (one or two) and your house lights to illuminate the driveway or entry. Or maybe you want to control the garage door, the driveway lights and have keyless entry into your home.

After all, you already have keyless entry into your car; why should you have to fumble with keys to open your front door? In fact, there are already commercial keyless entry systems for homes. Why shouldn't you have it too; and at lower cost?

Or how about this scenario? Say you have a two-car garage, in which the cars are tightly parked with not enough room for the passenger to get in before you drive out.

So you turn on the lights in the garage and outside, reverse your car out, the passenger gets in and you then use the 3-button transmitter to close the garage door, turn off the lights and drive away. When you return, you can turn on all the lights, your passenger alights and you can drive into the garage; all very civilised and convenient. And then you could also have keyless entry into the house itself!

Rolling code for high security

As with any type of lock, it is important that no one can gain access without the correct key.

For UHF remote control systems, the 'key' is a specific code sent by the transmitter to the receiver. Usually, this code is a long sequence of on and off signals sent in a specific sequence and over a set period. The code must be correct in order for the receiver to allow access.

It's effective – but there's a problem. The coded signal is transmitted over a relatively wide area each time it is used to gain access. Intruders have, in the past, used a radio

receiver and recorder to intercept the signal as the transmitter sends it. The intercepted signal could then be retransmitted to gain access.

Another method they've used is to continuously generate access codes with a computer and send them one after the other to the receiver. Eventually, the code is broken and access is possible.

Neither of these tampering methods will work with a 'rolling code' or 'code-hopping' system. In a rolling code system, the code transmitted is altered after each transmission.

So intercepting the signal and resending the signal will not enable access because the door lock is now expecting a different code. The code is based on an algorithm (calculation) that both the transmitter and receiver have in common. This is such a good system that many cars now have rolling code keyless entry systems.

The code possibilities of a rolling code system usually run into the trillions. This renders any attempt to break the code totally unrealistic. The odds of picking a correct code at random for our rolling code transmitter, for example, is one in 2.8 trillion. Even then, the code needs to be sent correctly at the required data rate, with the correct start and stop bit codes and other transmission requirements. As we said, rolling code means high security!

Features

Our *UHF Rolling Code Security System* has two parts: a keyfob-style transmitter and a separate receiver.

The keyfob has three pushbutton switches and an acknowledgement LED that briefly lights up each time one of the switches is pressed. Up to 16 separate keyfob transmitters can be used with one receiver.

The receiver has three relays that can be switched independently using the three switches on the keyfob transmitter(s). Each relay can be set to toggle on or off, or remain energised for a set period. This can be adjusted from 0.26 seconds to 4.4 minutes.

Part 1

By
JOHN CLARKE

Features

Transmitter

- Three function buttons
- Coding randomisation
- Rolling code UHF transmission
- Registering ability
- 16 identifications encoding
- 12V remote control battery operation
- Keyfob case
- Acknowledge LED indication

Receiver

- 12V DC plugpack operation
- For use with up to 16 separate transmitters
- 3 independent 230V AC rated relay contact outputs
- Door strike driver output
- Momentary or toggle operations for each output
- Momentary outputs adjustable in duration from 0.26 seconds to 4.4 minutes
- Acknowledge, power and output LED indicators
- Look-ahead feature for 100 codes when transmitter code is ahead of receiver code
- Lockout available for any registered transmitter
- Local control of outputs available



Specifications

Transmitter

Battery:12V 55mAH (A23 type)

Battery life: >2.5 years expected with typical use

Standby current: Typically 2.5 μ A with switches open (drawing 22mAH/year from battery)

Code transmit current: 3mA average over 160ms (133nAH / transmission drawn from battery)

Register transmit current:.. 3mA average over 2.75s

Randomisation current: 3.3mA

'Stuck switch' current: 220 μ A (after transmission is ended if a switch is kept pressed)

Code transmission rate:..... 1.024ms/bit (1k baud)

Encoding: A high (or a 1 bit) is transmitted as a 512 μ s burst of 433MHz signal, followed by 512 μ s of no transmission. A low (or 0 bit) is transmitted by a 512 μ s period of no transmission, followed by a 512 μ s burst of 433MHz signal.

Rolling code: Sends four start bits, an 8-bit identifier, the 48-bit code plus four stop bits. The start bits include a 16.4ms gap between the second start bit and the third start bit. Code scramble value is altered on each transmission.

Register code:..... Sent as two blocks. Block 1 sends four start bits, the 8-bit identifier, a 32-bit seed code and four stop bits. Block 2 sends four start bits, a 24-bit multiplier, the 8-bit increment and 8-bit scramble values, and four stop bits. The start bits include a 16.4ms gap between the second start bit and the third start bit.

Code randomisation: Alters the multiplier values, the increment value, the scramble value and the seed code at a 40 μ s rate.

Transmission range: 40m minimum

Receiver

Power: 12VDC at 150mA. (If using an electric door strike up to 12V DC at 1A intermittent)

Standby current:14mA (168mW) with all relays off. 150mA (1.8W) with all 3-relays and indicator LEDs lit

Relay contact rating:10A @ 240V AC

Momentary period: When set to momentary operation, each output is adjustable from 0.26s to 2s in 0.26s steps, then in 1s steps to 10s and in 15s steps to 4.4 minutes. (See Table 2.)

The relay outputs can switch up to 10A and 230V AC. For use with an electric door strike, the third output on the receiver can provide switched power directly, rather than having to wire up through relay contacts and 12V power.

The facility to setup for momentary or toggle action for the three outputs is provided with three pushbutton switches, a small rotary switch and three trimpots.

Indicator LEDs are included for power indication, relay on or off, and receive acknowledgement. The three pushbutton switches can also double up to function as local controls to switch the relays instead of using the UHF remote control.

Security and registration

Each keyfob transmitter must be allocated an identity number from 0 (zero) through to 15. This is set by coding links on the PC board. Then the initial rolling code needs to be randomised and the algorithm parameters set so that they are unique for each transmitter.

Finally, each transmitter is registered, and this involves sending a synchronising code to the receiver from the

transmitter when the receiver is set in its registration mode. As we said before, this can be done for 16 transmitters, and each will operate independently with the receiver.

Also included is a facility to lock out a particular transmitter after it has been registered. This is useful if a transmitter has been lost and you do not wish it to be useable with the receiver. If the lost transmitter is found then it can be easily re-registered.

When the identity of the lost transmitter is not known, then all transmitters can be locked out and ones that are in use can be re-registered.

Another use for this lockout facility is where people hire a public hall for a function, are lent a keyfob transmitter to gain entry (via an electric lock) and turn off any alarm system. If the keyfob is not returned, it can be locked out to prevent future security breaches.

Transmitter circuit

The circuit diagram for the 3-channel UHF Rolling Code Keyfob Transmitter is shown in Fig.1. There is not a lot to



The keyfob transmitter, shown above about life size, has three buttons, each of which controls a relay in the receiver. At bottom left is an LED that briefly flashes when any button is pressed, telling you that the battery is still OK.

At right is an oversize view of the completed transmitter inside the open keyfob case. The green PC board is the 433MHz UHF transmitter module itself.



the circuit, with just a PIC16F88-I/P microcontroller (IC1), a 433MHz UHF transmitter module and a surface-mount 5V regulator (REG1) as the major parts.

IC1 is normally kept in sleep mode, with its internal oscillator stopped and most internal features switched off. In this state, it draws a typical standby current of $0.6\mu\text{A}$ from the 5V supply (which is derived from a miniature 12V battery).

Switches S1 to S3 and the jumper links LK1 and LK2 connect to the RB6, RB5, RB7, RB0 and RB4 inputs. Each input is normally held high by an internal pullup resistor to the 5V rail. A closed switch will bring the respective input low (0V). Similarly, when LK1 is closed, the RB0 input will be held low. RB4 is brought low only when LK2 is in and switch S3 is pressed. IC1 is programmed to wake up from its sleep condition when any one of the RB4 to RB7 inputs change in level, or the RB0 input goes to 0V.

When IC1 wakes up, it starts running its program. If RB0 is low, the routine to randomise the parameters is run. If RB4 is low, the registration codes are transmitted, and if RB5, RB6 or RB7 is low, as when one of the keyfob buttons is pressed, it sends the normal rolling code.

The rolling code and registration codes are sent via the 433MHz transmitter module. This module is powered via the paralleled RA3 and RA4 outputs of IC1, which go high to provide a nominal 5V to the V_{CC} input of the module. The code signal is applied to the data input of the module from the RA2 output of IC1.

LED1 is driven via the RB3 output and is modulated at the code transmission rate of about 1kHz. The LED acts as a transmit indicator.

Inputs RA1, RA0, RA7 and RA6 can be tied to 0V or to the 5V supply rail via links on the PC board. These select the identity of the transmitter. With all inputs connected to 0V, its identity is '0'. When all inputs are tied to 5V, the identity is '15'. Various combinations of high and low connections for these inputs select the other identities from 1 to 14.

When the selected software routine is completed, IC1 returns to sleep mode.

First, if UHF transmission was involved, supply to the UHF transmitter module is removed by taking the RA3 and RA4 outputs and the data line at RA2 to 0V. LED1 is switched off with a low at RB3.

So, IC1 returns to the sleep mode, when the RB0 and RB4 to RB7 inputs are high, with open links and switch connections.

Flea-power regulator


Putting the micro (IC1) to sleep for most of the time is useful for keeping battery drain to the minimum, but that still leaves the quiescent current of the regulator, because it needs to continuously provide 5V supply for IC1.

A standard low-power 78L05 regulator is out of the question, as it typically draws 3mA quiescent current. Better still is the micropower LP2950 voltage regulator, which has a $75\mu\text{A}$ quiescent current (typical).

But even with $75\mu\text{A}$ quiescent current, the battery will be flat after only 733 hours, or 30 days. The solution was to use Microchip Technology's MCP1703T-5002E/CB 3-terminal regulator, which draws a mere $2\mu\text{A}$. This regulator current, combined with the micro's quiescent current when it is asleep has the whole circuit drawing about $2.6\mu\text{A}$.

We measured the standby current draw of our prototype circuit and found that it consumed $2.5\mu\text{A}$ of current from a fresh 12V battery. Measuring this current was easy. A $1\text{k}\Omega$ resistor was temporarily placed in series with the battery supply and the voltage drop across this resistor was measured. As we measured 2.5mV, the current is then calculated as $2.5\text{mV}/1\text{k}\Omega$ or $2.5\mu\text{A}$.

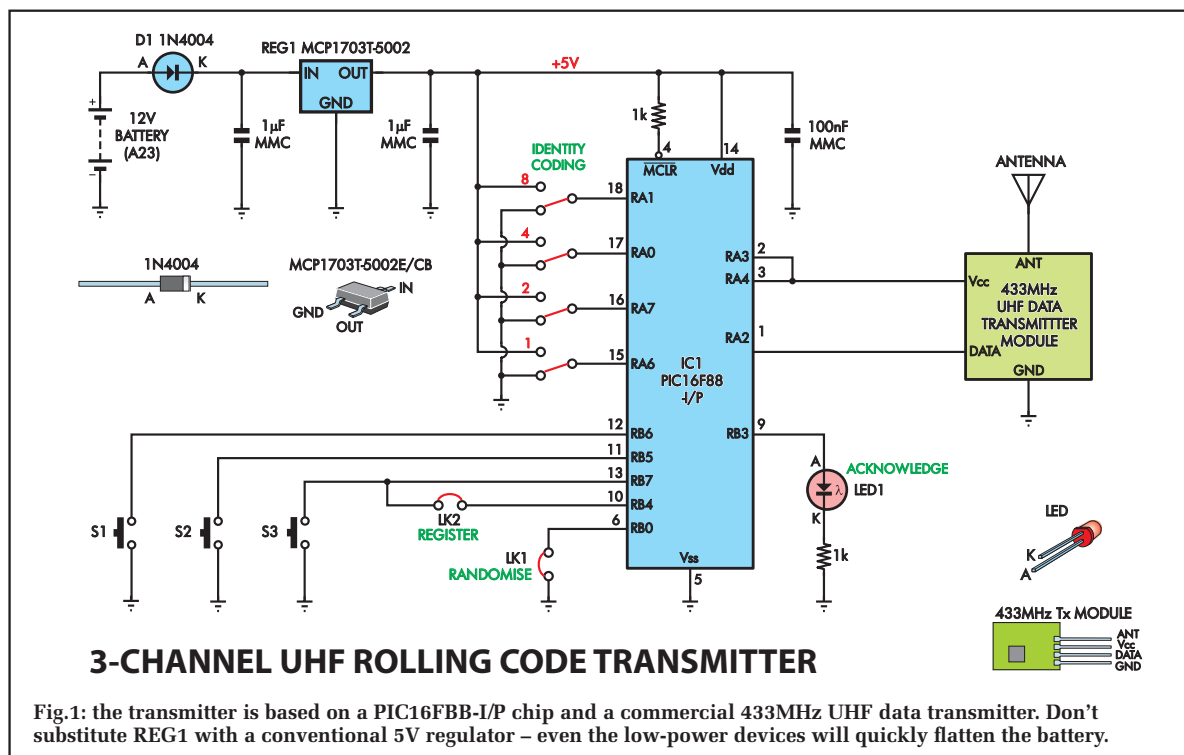During a transmission of a rolling code command, the current will briefly rise to about 3mA. If you hold one of the buttons down after the transmission is complete, the current will be about $220\mu\text{A}$. This is due to current flow in the switch pull-up resistor that connects from the 5V supply to 0V via the closed switch.



Battery life is expected to be more than 2.5 years, after which the 12V battery will have discharged down to 6V.

The transmitter circuit will continue to operate even at this low voltage – and this takes into account the nominal 600mV drop across reverse polarity protection diode D1. In fact, the regulator can operate down to 5.150V at its input and still maintain a 5V output. The input and output of REG1 are decoupled with $1\mu\text{F}$ monolithic ceramic capacitors. The regulator is designed to be stable with between $1\mu\text{F}$ and $22\mu\text{F}$ of capacitance on its output.

The effective series resistance (ESR) of the capacitor can range from 0 to 2Ω , so ceramic, tantalum or electrolytic capacitors can be used. IC1's supply is also decoupled with a 100nF monolithic ceramic capacitor.

Receiver circuit

The Receiver also uses a PIC16F88-I/P microcontroller (IC1) (see Fig.2). The UHF receiver module has a substantial on-board coiled wire antenna input to provide a very good reception range.

When no signal is present, the receiver's output signal is random noise that is caused by the module's automatic gain control (AGC) being set at maximum. Upon reception of a 433MHz signal, the receiver's gain is reduced for best reception without overload, and the coded signal from the data output of the module is applied to the RA2 input of IC1. LED4 indicates whenever a valid signal is received.

The RA4, RA6 and RA1 outputs of IC1 each drive a transistor and relay. When RA4 goes high, it turns on transistor Q1, which pulls in Relay1 and LED1 lights up. Diode D1 clips spike voltages at the collector (C) of Q1 when the relay

switches off. The relay contacts are rated at 10A and 240V AC, and can be used to control 230V AC lights if required.

Relay operation can be either momentary or toggle. Toggle operation means that the relay switches on with one press of switch S1 on the transmitter keyfob, and switches off when S1 is pressed again. Momentary operation has the relay switch on for a short preset period of time.

For Relay1, the momentary period is set using the trimpot VR1. The trimpot wiper (moving contact) can be adjusted from 0V through to 5V, and this voltage is monitored at the AN3 input of IC1 to give the actual period, which ranges from 0.26 seconds to 4 minutes 24 seconds.

The other two relays operate in a similar manner, with LED2 and LED3 indicating when they are on. Similarly, VR2 and VR3 set the momentary periods for Relay2 and Relay3.

Note that transistor Q3, used to switch Relay3 is a power Darlington. This allows it to drive an electric door strike (which may require 800mA or so) as well as the relay.

Dual function switches

Switches S1, S2 and S3 have different functions, depending on whether link LK1 is in or out of circuit. When LK1 is out of circuit, the RA5 input is held high via a 33k Ω resistor to the 5V supply, and switches S1, S2 and S3 can then be used to operate the relays directly. Hence, S1 operates Relay1, S2 operates Relay2 and so on.

Whether each relay operates in toggle or momentary mode depends on how it has been previously set.

When LK1 is placed in circuit, S1, S2 and S3 perform a different function. S1 does the lockout function, S2 sets toggle or momentary operation and S3 does keyfob registration.

BCD rotary switch

The on-board BCD rotary switch (S4) has 16 positions, labelled 0-9 and A-F. This switch is only applicable to the lockout and momentary/toggle selections; it plays no part in the keyfob transmitter registration.

The BCD switch has four outputs that connect to the RB3, RB1, RB2 and RB0 inputs of IC1. They are normally held high via internal pull-up resistors in IC1 unless an input is held low via a closed contact in the switch. When the BCD switch is set at 0, all four inputs are held high. Position 1 on the switch has the '1' output at RB3 pulled low. Position 16 (or F) sets all switch outputs at 0V.


Also in the settings mode with LK1 in circuit, pressing S3 places the program in IC1 ready to accept the registra-

tion signal from a transmitter. S1 provides the lockout function.

Pressing S1 will prevent the transmitter from operating the receiver. The transmitter to be locked out is identified by the number selected with BCD1. Similarly, for the momentary/toggle function, the position of BCD1 determines the output that will be changed from momentary to toggle, or toggle to momentary when S2 is pressed. BCD1 position 1 changes output 1, position 2 changes output 2 and position 3 changes output 3.

Power

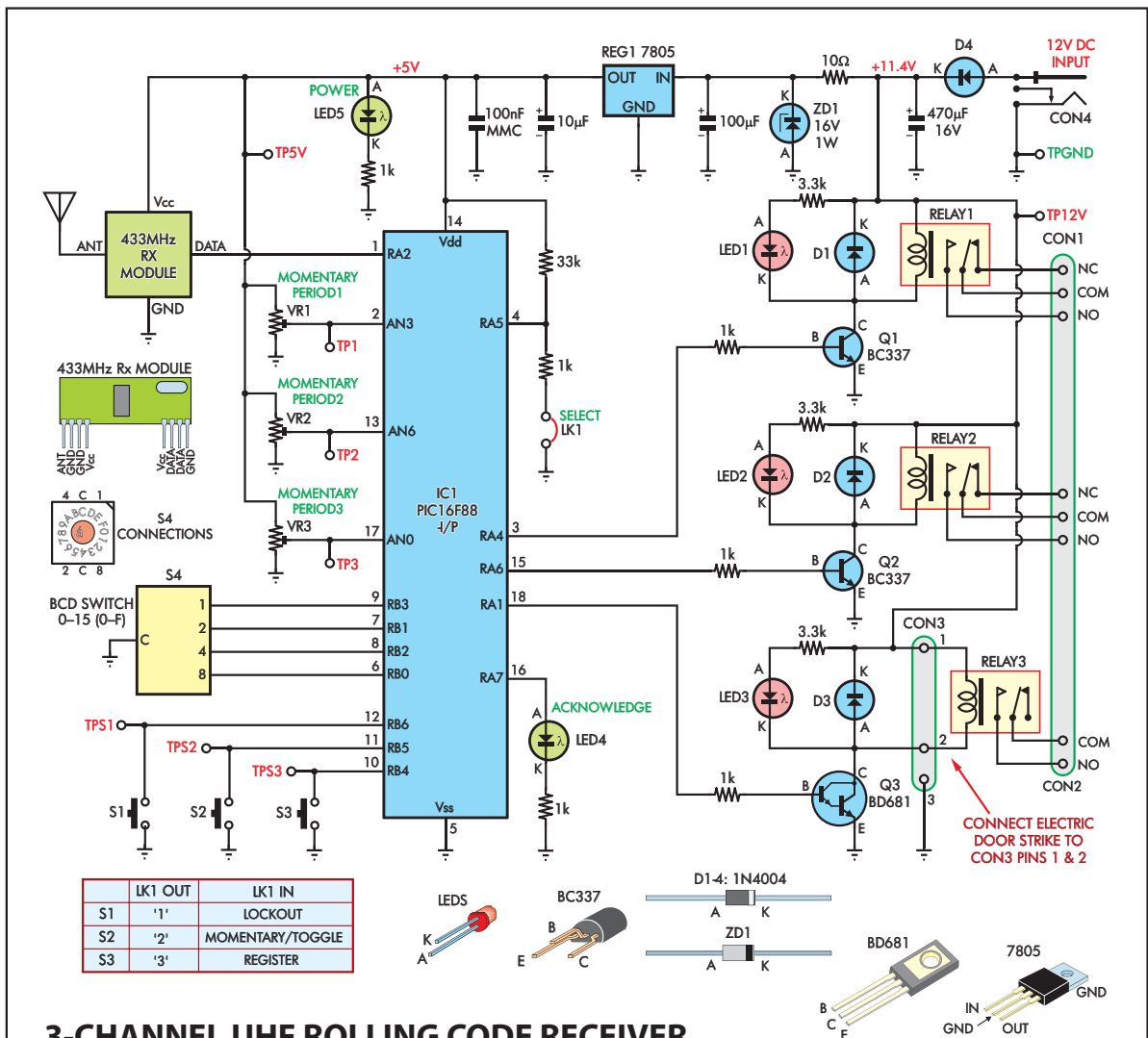The circuit is powered by a 12V DC plugpack. Reverse-polarity protection is provided by diode D4, while the



3-CHANNEL UHF ROLLING CODE RECEIVER

Fig.2: the receiver is not dissimilar to the transmitter, and is based on the same PIC. The main difference is in the coding arrangement (S4) and the relays, which can be used to switch just about anything, mains (up to 10A) or low voltage. If used to control a door strike, Relay 3 isn't required – it can be switched directly via the Darlington (Q3).

Constructional Project


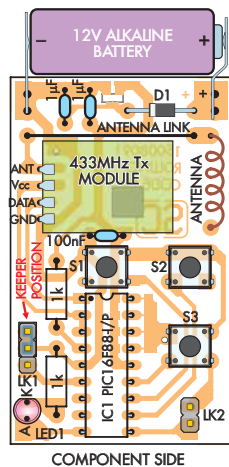


Fig.3 (left) shows the component side of the transmitter PC board. The UHF data module lies flat on the main PC board with its antenna, comprised of a short length of PC board track, a wire link and a wire coil.

Fig.4 (right) shows the under-side of the PC board, showing the identity coding links and the two locating holes. REG1, an SMD device, is also mounted on the copper side.

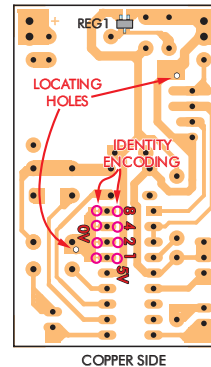

7805 3-terminal 5V regulator, REG1, is protected against excessive input voltage by Zener diode ZD1.

A nominal 12V rail supplies the three 12V relays. It is labelled as 11.4V on the circuit diagram (12V – 0.6V drop across D4), but the actual voltage could be higher, depending on the plugpack and power drawn from the plugpack. REG1 supplies IC1 and the UHF receiver module. A 100µF capacitor decouples the supply to REG1, while a 10µF capacitor bypasses the regulator output. LED5 indicates power is on.

Software

The software program files for the transmitter and receiver PICs are available from the *EPE* website at: www.epemag.com.

Construction

We'll begin construction with the keyfob transmitter. It is built using a 34mm × 56mm PC board, code 816. This board is available from the *EPE PCB Service* as a pair with the receiver board.

The assembled PC board is designed to fit into a Teco type-11 keyfob case with three buttons. The case is supplied with two battery contacts, a key ring loop, three switch caps and a case-securing screw.

Start by checking the PC board for correct sizing in the box. The edges of the PC board may need to be trimmed with a file if it has not been cut to the correct size. Note that the base of the case has a + and – polarity indicator for the battery terminals at its top end, while the PC board should fit neatly into the lower end of this case.

The case has two 1mm-diameter locating protrusions moulded into the base. These line up with the holes on the PC board when it is correctly fitted. Take care not to damage them – don't apply excessive force, or the pins will be bent or squashed.

Check the holes are correct with 1.25mm holes drilled for the battery terminals. Check

that the copper pattern is intact with no breaks in the copper tracks or hairline shorts between copper areas; repair if necessary.

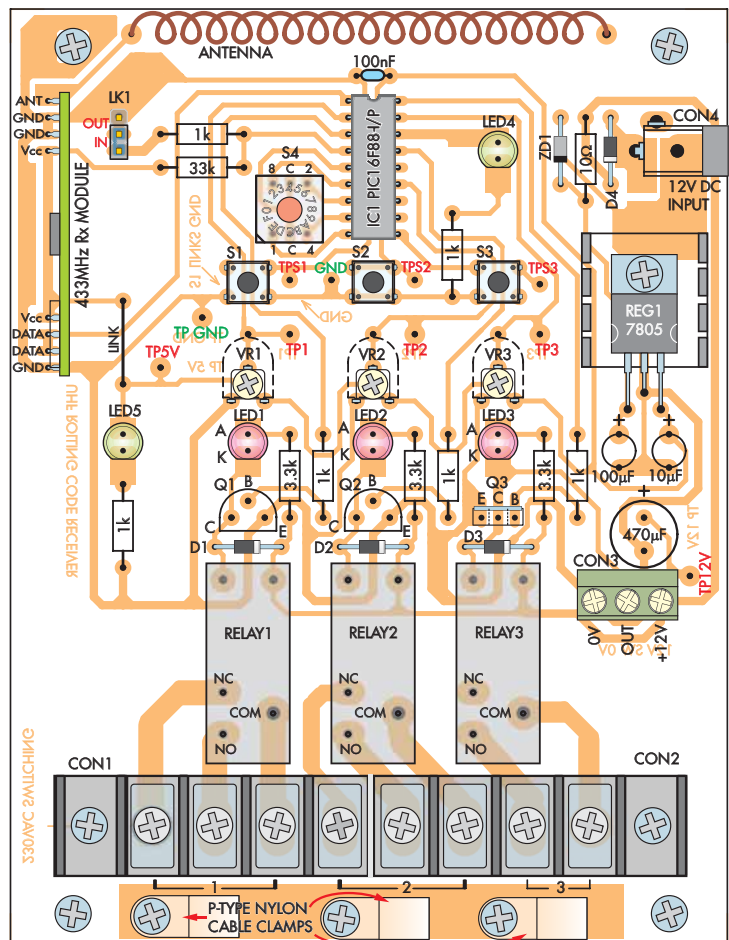


Fig.5: the receiver PC board. Everything is mounted on-board, with a similar coiled-wire antenna at the top of the board.

Identity coding

On the underside of the PC board are the identity encoding linking selections. The default setting is set for identity 0, where the '8', '4', '2' and '1' connections are tied to the 0V track with narrow PC tracks. If you are building just one transmitter there is no need to change these settings; it is only when more than one transmitter is required to work with the receiver that each transmitter requires a different identity. To set a different identity, use table 1 as a guide to setting the linking.

For example, to set identity 1, the '1' connection has to be tied to 5V with the '2', '4' and '8' connections left tied to 0V. To connect the '1' connection to the 5V rail, the narrow track connecting to the 0V rail has to be broken with a hobby knife or engraving tool, and a solder bridge applied between the terminal and the 5V rail track. Make sure the 0V and 5V supply are not shorted together by connecting both these supply rails to the one connection.

Identities available are from identity 0 to identity 15. Identities 10 to 15 are the letters A to F respectively. We mention the A to F values because the lockout switch on the receiver is labelled with these hexadecimal numbers instead of decimal – to lockout a transmitter identity on the receiver you must match the switch setting with the identity value.

It is a good idea to write the actual identity of each transmitter on the rear of the keyfob case. This will make



Con1 and Con2 are actually two 4-way barrier terminals, with one mounting hole cut off each end and the two halves glued together, as you can see here. Hot-melt glue holds them together while soldering and bolting in place (which takes most of the strain anyway). Note that these are actually panel-mounting types, which we made fit – the right ones, with PC pins instead of solder tags, which were out of stock at the time. You should use the *PC-mounting* type.


it easier to determine any lost transmitter identity so that it can be locked out.

Regulator REG1 mounts on the copper side of the PC board. This is a surface-mount device, but it only has three leads, so is quite easy to solder in place. Position the device over the copper lands as shown on the underside overlay diagram (Fig.4) and solder just one of the leads to the PC board. Check the device is still located correctly before soldering the remaining pins. If you need to realign the device, it is much easier when only one pin is soldered. Use solder wick to help remove it – don't try prising it off while heating the pins, as it is easy to damage either the pins or the copper lands underneath.

The topside of the PC board can now be assembled with the remaining components. Start with the wire link that acts as part of the UHF antenna. This is made from a 30mm length of 0.7mm tinned copper wire and is stretched as a straight wire between the two PC pads and soldered in position. We'll look at the remainder of the antenna (the coil) shortly.

Now insert the IC socket, taking care to place the notched end toward S1 as shown. Make sure the socket is fully seated onto the PC board before soldering the pins. Don't insert the IC just yet.

Switches S1, S2 and S3 are mounted fully seated onto the PC board. When soldering, be sure the locator hole near to S3 is not soldered, but is left clear of solder. Also, install the two 1k Ω resistors and diode D1 (which of course must be oriented correctly). Similarly, LED1 must go in the right way around – so that its anode, the round edge/longer lead, is oriented toward the lower edge of the PC board. The LED mounts right down on the PC board.

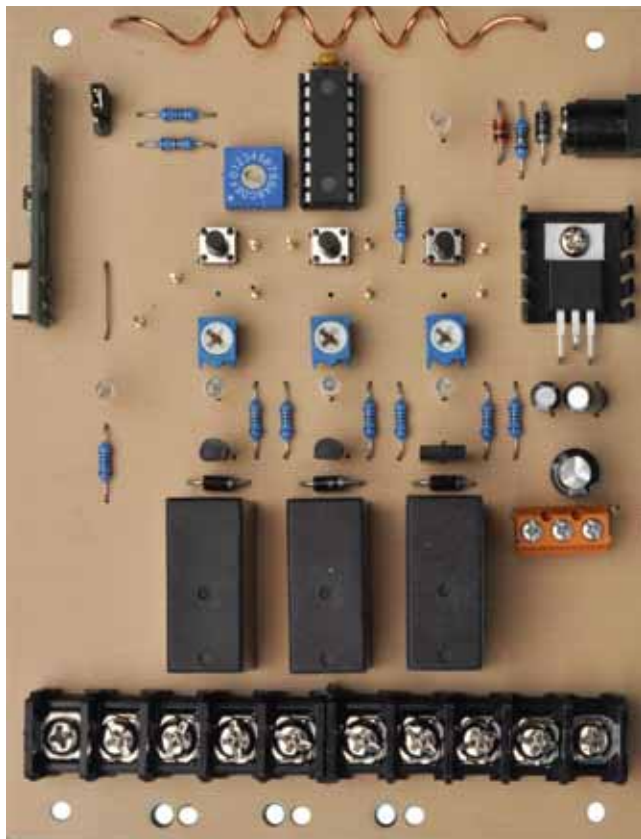

Here's a matching photo to help get everything where it should be. In the receiver, the UHF module mounts at right angles to the board...



... as shown in this close-up photo. Make sure it goes in the right way around.

Parts List – Deluxe Rolling-Code UHF Remote Control

Transmitter

- *1 PC board coded 816, size 34mm × 56mm
- 1 keyfob case with 3-buttons
(Teko type-11 No.11123.4) (supplied with battery contacts, key ring loop, 3-switch caps, LED diffuser and a securing screw)
- 1 433MHz UHF transmitter module
(Jaycar ZW-3100 or equivalent)
- 1 12V alkaline remote control battery
(Energizer A23 or equivalent)
- 1 DIP18 IC socket
- 3 SPST micro tactile switches, vertical mount with 3.5mm actuator (S1-S3)
(Jaycar SP-0602 or equivalent)
- 1 3-way 2.54mm spacing pin header
- 1 2-way 2.54mm spacing pin header
- 1 2.54mm jumper shunt
- 1 35mm length of 0.7mm tinned copper wire
- 1 138mm length of 0.63mm enamelled copper wire

Semiconductors

- 1 PIC16F88-I/P programmed microcontroller (IC1)
- 1 MCP1703T-5002E/CB 5V regulator (SOT-3 package) (REG1)
- 1 3mm green LED (LED1)
- 1 1N4004 1A diode (D1)

Capacitors

- 2 1 μ F monolithic ceramic
- 1 100nF monolithic ceramic

Resistors (0.25W 1%)

- 2 1k Ω

* Available as a pair from the *EPE PCB Service*

Receiver

- *1 PC board coded 817, size 110mm × 141mm
- 1 IP65 sealed polycarbonate box with clear lid, size 171mm × 121mm × 55mm
- 1 433MHz UHF receiver module
(Jaycar ZW-3102 or equivalent)
- 1 0-F BCD rotary switch (BCD1)
(Jaycar SR-1220, Altronics S 3000A or equivalent)
- 3 SPST micro tactile switches vertical mount with 6.0mm (or similar) actuator (S1-S3)
(Jaycar SP-0603 or equivalent)

- 3 12V SPDT relays with 10A 240V AC contacts (RLY1-3) (Jaycar SY-4050 or equivalent)
- 2 4-way PC mount terminal barriers with transparent cover and 9.5mm spacing (CON1)
(Jaycar HM-3162 or equivalent)
- 1 3-way screw terminals with 5.08mm pin spacing (CON3)
- 1 3-way pin header with 2.54mm pin spacing
- 1 2.54mm jumper shunt
- 1 30mm length of 0.7mm tinned copper wire
- 1 157mm length of 1mm enamelled copper wire
- 3 P clamps for 5mm cable
- 3 Cable glands (3-6.5mm diameter cable)
- 1 18-pin DIL IC socket
- 1 mini finned heatsink 19mm × 19mm × 9.5mm
- 1 2.5mm PC mount DC socket (CON2)
- 10 PC stakes
- 2 M4 × 15mm screws
- 3 M4 × 10mm screws
- 5 M4 nuts
- 1 M3 × 10mm screw
- 4 M3 × 6mm screws
- 1 M3 nut
- 3 M4 washers
- 2 M3 washers

Semiconductors

- 1 PIC16F88-I/P programmed microcontroller (IC1)
- 1 7805 5V regulator (REG1)
- 2 BC337 *NPN* transistors (Q1,Q2)
- 1 BD681 *NPN* Darlington transistor (Q3)
- 3 red 3mm LEDs (LED1-LED3)
- 2 green 3mm LEDs (LED4,LED5)
- 4 1N4004 1A diodes (D1-D4)
- 1 16V 1W Zener diode (ZD1)

Capacitors

- 1 470 μ F 16V PC electrolytic
- 1 100 μ F 16VW PC electrolytic
- 1 10 μ F 16VW PC electrolytic
- 1 100nF monolithic ceramic

Resistors (0.25W 1%)

- 1 33k Ω 3 3.3k Ω 6 1k Ω 1 10 Ω
- 3 10k Ω horizontal trim pots (coded 103) (VR1-VR3)

The 2-way and 3-way pin headers can be mounted and soldered in place. The jumper plug can be installed in the keeper position. This position is just to store the jumper plug so that it is not lost. When placed in the keeper position, it does not make a connection for LK1.

There are two 1 μ F monolithic capacitors, mounted near REG1. These will be marked as '105' or '1 μ ' on their body. The 100nF capacitor just above S1 will be marked as '104' or '100n'.

The 433MHz transmitter module mounts parallel with the PC board by bending the mounting pins down at right angles. Make sure the pins are bent in the correct direction, so when installed, the module has the antenna pin toward

the top edge of the PC board. The module sits about 3mm above the PC board.

Battery clips are mounted with the dimples pointing inward to face each other. The larger dimpled clip is for the + end and this mates well with a dint in the battery + terminal.

The antenna is made up using the straight wire link soldered in earlier and a spiral section, made using a 138mm length of 0.63mm enamelled copper wire. The insulation on each end is scraped clean for about 1mm to allow the ends to be soldered in position.

The wire is coiled by winding on about five turns on a 6.35mm (1/4-inch) former – a drill bit is ideal. The coil

winding should look something like our prototype (as shown in the photograph).

Before inserting the microcontroller, connect the battery and check that there is 5V between pins 5 and 14 on the IC1 socket. The voltage could range from 4.85V to 5.15V. Anything outside this means there is a problem. A 0V reading could mean the battery is in the wrong way, or there is a short circuit across the 5V supply rail.

If it is correct, remove the battery and insert IC1, the notch on the IC matching the notch on the socket.

The quiescent current can be measured if a 1k Ω resistor is placed in series with the battery to one of the clips. This is done by temporarily soldering one end of the resistor to the PC board at the + terminal. Connect your multimeter leads across the resistor and set the meter for reading millivolts. Then connect the ‘–’ end of the battery to the minus terminal on the PC board and hold the unsoldered end of the resistor to the plus battery terminal. The voltage should be around 2.5mV to 3mV, representing 2.5 μ A to 3 μ A. The voltage will rise when one of the switches is pressed to about 3V, but fall back to the quiescent value after the LED has flashed and the switch is released.

Receiver construction

The receiver is constructed on a PC board, code 817, measuring 110mm \times 141mm. This board is paired with the transmitter PCB and is available from the *EPE PCB Service*. It is housed in a 171mm \times 121mm \times 55mm IP65 sealed polycarbonate box with clear lid.

As you did with the transmitter, check the board fits neatly into its box. The corner mounting holes should be drilled out to accommodate M3 screws that are used to screw into the integral brass threads of the box. Holes for CON1 and CON2 are 2mm for the 4-way terminals and 4mm for the outside securing screws. The holes to secure the P-clamps are 4mm. Again, check the PC board for breaks in the copper tracks or for shorts between tracks, and repair any faults, if necessary.

Begin board assembly by installing the wire link and the resistors. It’s a good idea to verify each resistor value with a digital multimeter before soldering it in position. PC stakes can go in next.

Install diodes D1 to D4 and Zener ZD1, taking care to orient correctly. The IC socket may now be installed, again making sure the notched end is correctly positioned. Switches S1 to S3 can be installed now, as well as the 3-way pin header for LK1. Install BCD1, ensuring the switch is oriented correctly, along with trimpots VR1 to VR3.

Transistors Q1 and Q2 are mounted with the orientation shown. Darlington transistor Q3 is not so immediately obvious: it is installed with its metal face towards LED3. Next, install the four capacitors – the three electrolytic (polarised) types need to be oriented as shown. CON1, CON2, CON3 and CON4 can be installed.

Because barrier terminal strips only come in four and six-way (and we need eight-way!) we made our own by carefully cutting off the mounting holes from one end of two four-way types and gluing them together. Because they are soldered to the PC board and there is also a mounting point at each end, this should be more than adequate.

Before soldering in, the combined CON1 and CON2 block is secured to the PC board using two M4 \times 15mm screws

Table 1: Transmitter Identity Coding

IDENTITY	‘8’	‘4’	‘2’	‘1’
0	0V	0V	0V	0V
1	0V	0V	0V	5V
2	0V	0V	5V	0V
3	0V	0V	5V	5V
4	0V	5V	0V	0V
5	0V	5V	0V	5V
6	0V	5V	5V	0V
7	0V	5V	5V	5V
8	5V	0V	0V	0V
9	5V	0V	0V	5V
10 (or A)	5V	0V	5V	0V
11 (or B)	5V	0V	5V	5V
12 (or C)	5V	5V	0V	0V
13 (or D)	5V	5V	0V	5V
14 (or E)	5V	5V	5V	0V
15 (or F)	5V	5V	5V	5V

The default setting is Identity 0, as set by narrow PC tracks that connect the ‘8, 4, 2 and 1’ inputs to 0V. Other Identities are set by breaking the appropriate track that connects an input to 0V and soldering a bridge from the input to the 5V rail. For example, to set Identity 1, break the 0V connection to the ‘1’ terminal and solder to the 5V rail. For Identity 5, the ‘4’ input would need to be tied to 5V, as well as the ‘1’ input.

placed through the two outside holes and with two M4 nuts on the underside of the PC board.

We ended up using only one of the clear protective coverings – it adequately covers the eight live terminals, while leaving the two mounting screws uncovered.

LED1 to LED5 are mounted about 15mm above the PC board, with red LEDs used for LEDs 1 to 3, while LED4 to LED5 are green. Be sure to orient each correctly. The UHF receiver module can be installed next; again take great care to position it correctly. The pin connections for the module are printed adjacent to each pin.

The three relays can be mounted now, followed by the 5V regulator. It mounts horizontal to the PC board on a small finned heatsink. The leads are bent down 90° to protrude through the holes in the PC board. Fasten the regulator and heatsink to the PC board (with an M3 \times 10mm screw and nut), before soldering the leads in place underneath.

The antenna is made using 157mm of 1mm enamelled copper wire. The ends are stripped of enamel insulation for about 1mm using a sharp hobby knife to scrape it clean. Again, the wire is wound into a coil over a 6.35mm (1/4-inch) former such as a drill bit. The coil is stretched out to reach the two connection points and soldered in position.

That completes the construction of the boards themselves. Next month, we’ll look at testing and setting them up to ‘talk’ to each other and complete the project. We’ll also look at some FAQs (frequently asked questions) about rolling code and code scrambling – stay tuned!

STORE YOUR BACK ISSUES ON CD-ROMS

**FIVE YEAR
DVD/CD-ROMS
NOW AVAILABLE**

**ONLY
£16.45
(£29.95 FOR 5 YEAR)
each including VAT and p&p**

VOL 1: BACK ISSUES – January 1999 to June 1999
Plus some bonus material from Nov and Dec 1998

VOL 2: BACK ISSUES – July 1999 to December 1999

VOL 3: BACK ISSUES – January 2000 to June 2000

VOL 4: BACK ISSUES – July 2000 to December 2000

VOL 5: BACK ISSUES – January 2001 to June 2001

VOL 6: BACK ISSUES – July 2001 to December 2001

VOL 7: BACK ISSUES – January 2002 to June 2002

VOL 8: BACK ISSUES – July 2002 to December 2002

VOL 9: BACK ISSUES – January 2003 to June 2003

VOL 10: BACK ISSUES – July 2003 to December 2003

VOL 11: BACK ISSUES – January 2004 to June 2004

VOL 12: BACK ISSUES – July 2004 to December 2004

VOL 13: BACK ISSUES – January 2005 to June 2005

VOL 14: BACK ISSUES – July 2005 to December 2005

VOL 15: BACK ISSUES – January 2006 to June 2006

VOL 16: BACK ISSUES – July 2006 to December 2006

VOL 17: BACK ISSUES – January 2007 to June 2007

VOL 18: BACK ISSUES – July 2007 to December 2007

VOL 19: BACK ISSUES – January 2008 to June 2008

VOL 20: BACK ISSUES – July 2008 to December 2008

VOL 21: BACK ISSUES – January 2009 to June 2009

VOL 22: BACK ISSUES – July 2009 to December 2009

**FIVE YEAR CD-ROM No.1 – Jan '03 to
Dec '07**

**FIVE YEAR CD-ROM No.2 – Jan '04 to
Dec '08**

**FIVE YEAR DVD-ROM No.3 – Jan '05 to
Dec '09**

NOTE: These DVD/CD-ROMs are suitable for use on any PC with a DVD/CD-ROM drive. They require Adobe Acrobat Reader (available free from the Internet – www.adobe.com/acrobat)

WHAT IS INCLUDED

All volumes include the *EPE Online* editorial content of every listed issue, plus links to all the available **PIC Project Codes** for the PIC projects published in those issues. **Please note that we are unable to answer technical queries or provide data on articles that are more than five years old.** Please also ensure that all components are still available before commencing construction of a project from a back issue.

A great way to buy *EPE* Back Issues – our DVD/CD-ROMs contain back issues from our *EPE Online* website plus bonus articles, all the relevant PIC software links and web links. **Note: no free gifts are included.**

Order on-line from
www.epemag.com (go to the UK store or US store)
or by phone, fax, email or post

BACK ISSUES DVD/CD-ROM ORDER FORM

Please send me the following Back Issue DVD/CD-ROMs.

Volume Numbers:

Price £16.45 each, £29.95 for Five Year DVD/CD-ROMs – includes postage to anywhere in the world.

Name

Address

Post Code

☐ I enclose cheque/P.O./bank draft to the value of £

☐ please charge my Visa/Mastercard/Maestro £

Card No.

Card Security Code (The last 3 digits on or just under the signature strip)

Valid From. Expiry Date

Maestro Issue No.



SEND TO: **Everyday Practical Electronics,**
Wimborne Publishing Ltd., 113 Lynwood Drive, Merley,
Wimborne, Dorset BH21 1UU.

Tel: 01202 880299. Fax: 01202 843233.

E-mail: orders@epemag.wimborne.co.uk

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally posted within seven days of receipt of order.

**EPE
EXCLUSIVE**

Win a Microchip MPLAB Starter Kit For PIC24H MCUs

EVERYDAY PRACTICAL ELECTRONICS is offering readers the chance to win the new **Microchip** MPLAB Starter Kit for the PIC24H, which includes everything needed to develop and evaluate Human-Machine Interfaces (HMIs) and intelligent sensor processing for embedded designs.

The MPLAB Starter Kit for PIC24H MCUs allows developers to run the included accelerometer-based sample programs, and check out the interaction of the accelerometer and the switches with the MCU on the visual display, while listening to speech playback. Users can connect their own analogue sensors for signal processing, and can download and test their own applications.

Additional key features of the MPLAB Starter Kit for PIC24H MCUs include: integrated debugger/programmer; USB powered; 128×64 OLED display and onboard speaker; low-cost speech playback via G.711 compression; two switches for application utility; separate analogue, conditioning circuitry to plug in a wide range of sensors for sensor signal processing. Plus a CD with Microchip's MPLAB Integrated Development Environment, including a full editor, programmer and debugger; MPLAB C compiler; code examples and user's guide.

HOW TO ENTER

For your chance to win a Microchip MPLAB Starter Kit for PIC24H, visit: www.microchip-comps.com/epe-pic24h and enter your details in the online entry form.



CLOSING DATE


The closing date for this offer is 30 September 2011

TEACH-IN 2011

A BROAD-BASED INTRODUCTION TO ELECTRONICS

Part 10: Electronic circuit construction and testing

By Mike and Richard Tooley

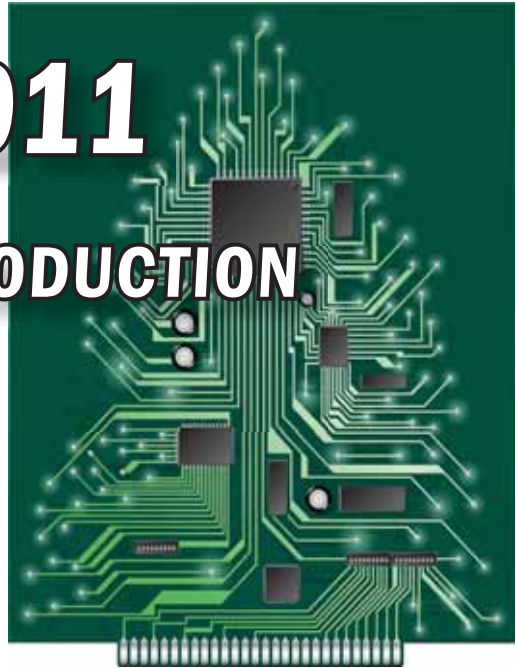

Our Teach-In series aims to provide you with a broad-based introduction to electronics. We have attempted to provide coverage of three of the most important electronics units that are currently studied in many schools and colleges in the UK. These include Edexcel BTEC Level 2 awards as well as electronics units of the new Diploma in Engineering (also at Level 2). The series will also provide the more experienced reader with an opportunity to “brush up” on specific topics with which he or she may be less familiar.

Each part of our Teach-In series is organised under five main headings; Learn, Check, Build, Investigate and Amaze. Learn will teach you the theory, Check will help you to check your understanding, and Build will give you an opportunity to build and test simple electronic circuits. Investigate will provide you with a challenge which will allow you to further extend your learning and finally Amaze will show you the ‘wow factor’!

THIS month, we look at the practical aspects of electronic circuit construction and testing.

In **Learn** we introduce you to two of the most common and versatile items of test equipment, the *multimeter* and *oscilloscope*. **Build** looks at techniques that can be used to design, construct and test printed circuit boards (PCB) within Circuit Wizard.

Investigate involves taking measurements and fault finding on a simple voltage regulator circuit. Finally, **Amaze** looks at the reliability of electronic components.

Learn

At BTEC Level 1 and Level 2 you need to be able to make measurements on simple DC and AC circuits including:

- Measuring *voltage*, *current* and *resistance* using a multi-range meter (or *multimeter*)
- Displaying waveforms and making measurements of voltage (peak and peak-to-peak) and time using an *oscilloscope*.



Fig.10.1. Multimeters can be either analogue (left) or digital (right)

In all cases, you will need to ensure that you work safely and observe correct procedures (for example, switching off and disconnecting the power supply *before* connecting test leads). We begin this month's **Learn** by introducing the test instruments that you will be using.

Multimeters

One of the most common, versatile and easy-to-use instruments is the multi-range meter, or multimeter. This instrument combines the functions of a voltmeter, ammeter and ohmmeter into a single instrument. Many multimeters also have additional ranges, for example to check continuity, measure capacitance or to check diodes and transistors.

Most multimeters operate from internal batteries, and are thus independent of the mains supply. This allows you to easily carry them around and make measurements on electronic equipment when you are away from the laboratory or workshop.

There are two main types of multimeter: *analogue* and *digital* (see Fig.10.1). Analogue multimeters employ conventional moving coil movements; the display takes the form of a pointer moving across a calibrated scale.

This arrangement is not so convenient to use as that employed in digital instruments because the position of the pointer is rarely exact and may require interpolation. Analogue instruments do, however, offer some advantages, not least, is that it's very easy to make adjustments to a circuit, while observing the relative direction of the pointer; a movement in one direction representing an increase and in the other a decrease.

Despite this, the main disadvantage of analogue meters is the rather cramped and sometimes confusing scale calibration. To determine the exact reading requires first an

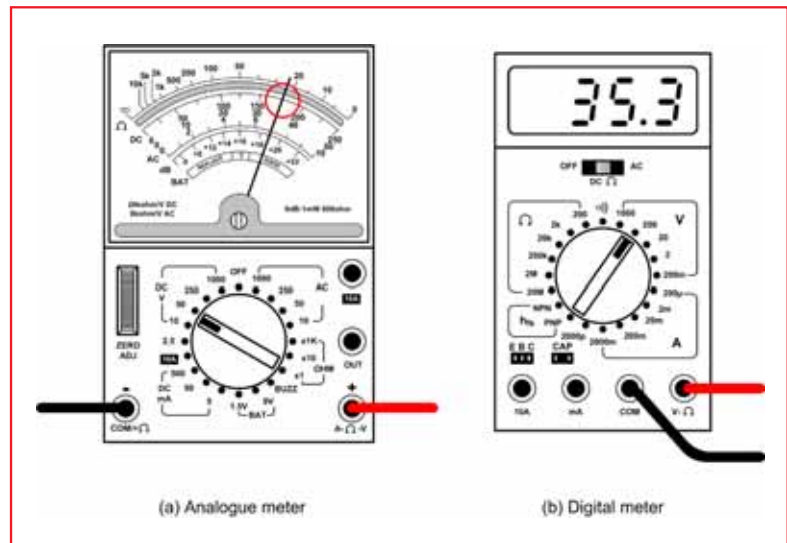


Fig.10.2. A comparison of the displays provided on analogue and digital multimeters. Both meters indicate the same value.

estimation of the pointer's position, and then the application of some mental arithmetic based on the range switch setting (see Fig.10.2)

Unlike their analogue counterparts, digital multimeters are usually extremely easy to read and have displays that are clear, unambiguous, and capable of providing a very high resolution. It is also possible to distinguish between

readings that are very close. This is just not possible with an analogue instrument.

Digital multimeters offer a number of significant advantages; when compared with their analogue counterparts. The display fitted to a digital multimeter usually consists of a 3½-digit seven-segment display—the ½ simply indicates that the first digit is either blank (zero) or 1.

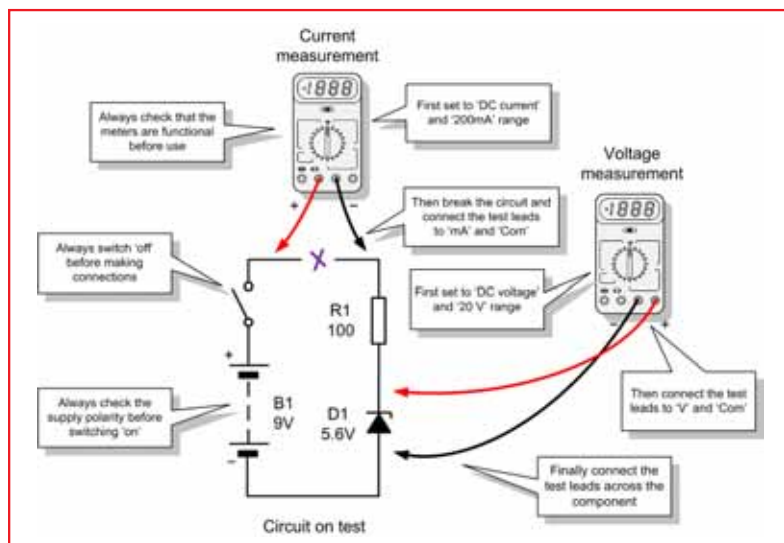


Fig.10.3. The procedure for making current and voltage measurements using a digital multimeter

Consequently, the maximum indication on the 2V range will be 1.999V. This suggests that the instrument is capable of offering a resolution of 1mV on the 2V range (in other words, the smallest increment in voltage that can be measured is 1mV).

Depending on the size and calibration markings on the instrument's scale, the resolution obtained from a comparable analogue meter would typically be about 50mV, and so the digital instrument provides us with a resolution that is many times greater than its analogue counterpart.

Multimeter measurements

The procedure for making current and voltage measurements using a digital multimeter, is shown in Fig.10.3. We've chosen this type of instrument for our example because you will probably be using a modern digital instrument rather than an older analogue type.

Note how it is necessary to break the circuit and insert the meter when making a current measurement. Notice also how the voltmeter is connected in parallel with the circuit at the point at which you are making a measurement.

It is *essential* that you get these two connections right and that you select the correct ranges on the multimeter. Failure to observe these two simple precautions can result in damage to the meter and/or the circuit under test!

In Fig. 10.3, one of the meters is used to measure the supply current (note that the circuit must be broken and the meter inserted into it), while the second instrument is being used to measure the potential difference (voltage drop) across diode D1.

The initial range settings (200mA for the current measurement, and 20V for the voltage measurement) are chosen so that they are both greater than those that we would expect to find in the circuit. For example, we

would calculate the current flowing in the circuit to be $(9 - 5.6)/100$ amps or 34mA.

Similarly, we could assume that the voltage that we would measure should be 5.6V (the same as the Zener voltage), but in no event would we expect it to be greater than the supply voltage (9V). We have, therefore, left quite a margin for safety with the two ranges that we've selected!

Please note!

It is *essential* to switch off and disconnect the power supply *before* attempting to connect test leads. When the meter ranges have been set and the connections made, the supply can be reinstated and switched back on, so that measurements can be made.

Please note!

In your school/college course you will only be working with equipment that uses safe low voltage supplies. Even so, it is essential to observe Health and Safety precautions whenever you are working on live electrical and electronic circuits.

When in doubt, you should always refer to your tutor!

Please note!

When the circuit on test uses large value capacitors it may be necessary to wait a few minutes in order to allow them to discharge safely before making connections to the circuit.

Please note!

Make sure that you only use properly *insulated* test leads to make connections to a circuit on test. The leads should be fitted with clips and probes to make connections to a circuit.

Never use bare wires and test prods

as these can cause short-circuits to adjacent connections!

Oscilloscopes

Oscilloscopes can be used in a variety of measuring applications, the most important of which is the display of time related voltage waveforms.

Older oscilloscopes (Fig.10.4) used cathode ray tubes (CRT) for their displays. In order to make accurate measurements, the face of the CRT was fitted with a *graticule* that was either integral with the tube or took the form of a separate translucent sheet. Modern oscilloscopes use flat LCD displays, either colour or monochrome, which incorporate an electronically generated measuring scale. Accurate voltage and time measurements are made with reference to the scale or graticule, applying a scale factor derived from the appropriate range switch.

The use of the graticule is illustrated by the following example. An oscilloscope screen is depicted in Fig.10.5. This diagram is reproduced at a reduced size. If shown full-size, the graticular markings would be spaced at 1cm and the fine graticule markings would be every 2mm along the central vertical and horizontal axes.

The oscilloscope is operated with all relevant controls in the 'CAL' position. The timebase (horizontal deflection) is switched to the 1ms/cm



Fig.10.4. A typical two-channel general purpose oscilloscope that uses a CRT display

range and the vertical attenuator (vertical deflection) is switched to the 1V/cm range.

The overall height of the trace is 4cm, and thus the peak-to-peak voltage is $4 \times 1\text{V} = 4\text{V}$. Similarly, the time for one complete cycle (period) is $2.5 \times 1\text{ms} = 2.5\text{ms}$.

One further important piece of information is the shape of the waveform that, in this case, is sinusoidal. The function of some of the more common controls and adjustments for a general purpose oscilloscope are listed in Table 10.1.

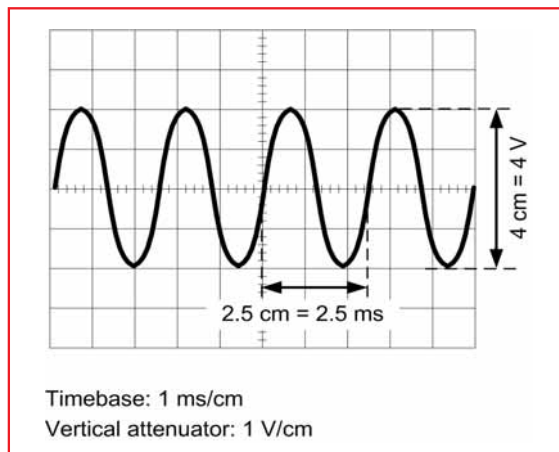


Fig.10.5. Using an oscilloscope scale

Please note!

Before taking meaningful measurements from a CRT screen it is absolutely essential to ensure that the front panel variable controls are set in the *calibrate* (CAL) position. Results will almost certainly be inaccurate if this is not the case!

Oscilloscope measurements

A typical oscilloscope measurement is shown in Fig.10.6. In this application the oscilloscope is being used to display the waveforms in a simple half-wave rectifier power supply.

As with the multimeter measurements that we met earlier it is essential to make initial adjustments to the oscilloscope BEFORE connecting the oscilloscope to the circuit and switching on the supply. Once again, when in doubt, you should refer to your tutor!

Virtual instruments

In recent years, a new type of electronic measuring instrument has

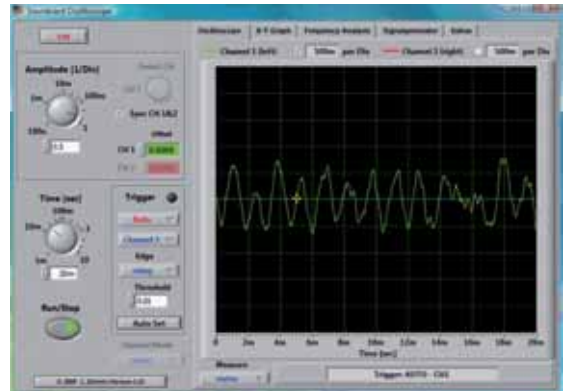


Fig.10.7. A typical display produced by a PC-based virtual oscilloscope

become available. Rather than using conventional analogue, digital or CRT displays, these *virtual instruments* use plug-in adapters or USB-connected interfaces, together with a PC (either desktop or laptop). The interface circuit captures a digital sample of the analogue input, which can then be stored in memory and recalled for later display.

Virtual instruments offer a number of advantages when compared with conventional test instruments, including the ability to display waveform parameters (such as time, voltage, frequency and phase) as well as being able to store, recall and print waveform data. A typical virtual soundcard oscilloscope display is shown in Fig.10.7.

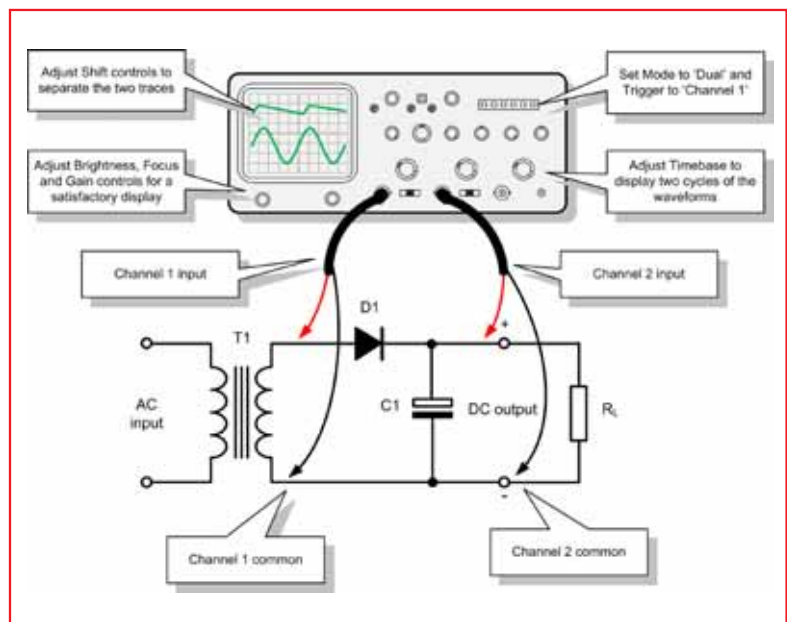


Fig.10.6. Oscilloscope measurements on a simple half-wave rectifier power supply

Table 10.1. Oscilloscope controls and adjustments

Control	Adjustment
Focus	Provides a correctly focused display on the screen
Intensity	Adjusts the brightness of the display
Astigmatism	Provides a uniformly defined display over the entire screen area and in both x and y directions. The control is normally used in conjunction with the focus and intensity controls
Trace rotation	Permits accurate alignment of the display with respect to the graticule (CRT displays only)
Scale illumination	Controls the brightness of the graticule or scale
<i>Horizontal deflection system</i>	
Timebase (time/cm)	Adjusts the timebase range and sets the horizontal time scale. Usually this control takes the form of a multi-position rotary switch and an additional continuously variable control is often provided. The 'CAL' position is usually at one, or other, extreme setting of this control
Stability	Adjusts the timebase so that a stable waveform display is obtained
Trigger level	Selects the particular level on the triggering signal at which the timebase sweep commences
Trigger slope	This usually takes the form of a switch that determines whether triggering occurs on the positive or negative going edge of the triggering signal
Trigger source	This switch allows selection of one of several waveforms for use as the timebase trigger. The options usually include an internal signal derived from the vertical amplifier, a 50Hz signal derived from the supply mains, and a signal which may be applied to an External Trigger input
Horizontal position	Positions the display along the horizontal axis (CRT displays only)
<i>Vertical deflection system</i>	
Vertical attenuator (V/cm)	Adjusts the magnitude of the signal attenuator (V/cm) and sets the vertical voltage scale. This control is invariably a multi-position rotary switch; however, an additional variable gain control is sometimes also provided. Often this control is concentric with the main control and the 'CAL' position is usually at one, or other, extreme setting of the control
Vertical position	Positions the display along the vertical axis of the display
AC-DC-ground	Normally an oscilloscope employs DC coupling throughout the vertical amplifier; hence a shift along the vertical axis will occur whenever a direct voltage is present at the input. When investigating waveforms in a circuit, one often encounters AC superimposed on DC levels; the latter may be removed by inserting a capacitor in series with the signal. With the AC-DC-ground switch in the AC position, a capacitor is inserted in the input lead, whereas in the DC position the capacitor is shorted. If ground is selected, the vertical input is taken to common (0V) and the oscilloscope input is left floating. This last facility is useful in allowing the accurate positioning of the vertical position control along the central axis. The switch may then be set to DC and the magnitude of any DC level present at the input may be easily measured by examining the shift along the vertical axis.
Chopped-alternate	This control, which is only used in dual-beam CRT oscilloscopes, provides selection of the beam splitting mode. In the chopped position, the trace displays a small portion of one vertical channel waveform followed by an equally small portion of the other. The traces are, in effect, sampled at a relatively fast rate, the result being two apparently continuous displays. In the alternate position, a complete horizontal sweep is devoted to each channel alternately.

Check – How do you think you are doing?

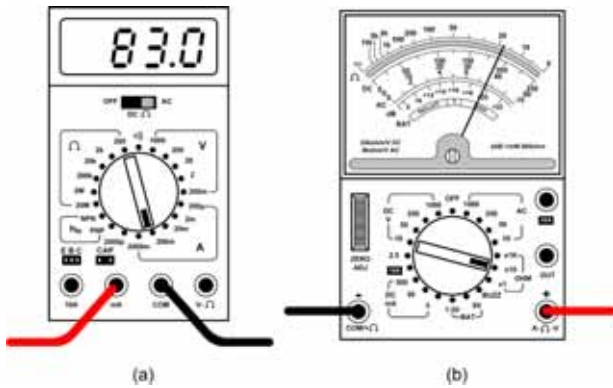


Fig.10.8. See Question 10.2

10.1. Briefly explain the difference between analogue and digital multimeters. Which type of instrument offers the greatest resolution? Why is this?

10.2. What indications are displayed on the analogue and digital multimeters shown in Fig.10.8?


10.3. What information (eg, amplitude, period) can be obtained from the oscilloscope displays shown in Fig.10.9?

10.4. Explain the function of each of the following oscilloscope controls:
(a) Brightness


- (b) Focus
- (c) Stability
- (d) Trigger source
- (e) Vertical attenuator.

10.5. Explain why it is important to ensure that the variable controls of an oscilloscope are placed in the 'CAL' position before attempting to make an accurate measurement.

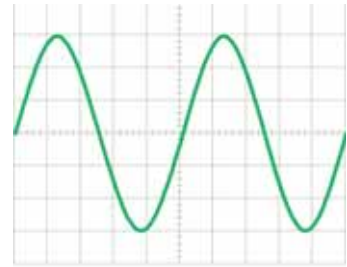10.6. What adjustment should be made to an oscilloscope when it is to be used to display a small AC voltage superimposed on a much large DC voltage? Explain why this adjustment is necessary.



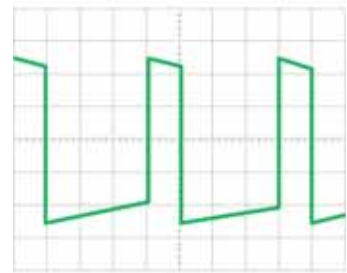(a) Timebase: 1 ms/cm
Y-attenuator: 1 V/cm



(b) Timebase: 2 ms/cm
Y-attenuator: 500 mV/cm

Fig.10.9. See Question 10.3

For more information,
links and other resources
please check out our
Teach-In website at:
[www.tooley.co.uk/
teach-in](http://www.tooley.co.uk/teach-in)


CIRCUIT WIZARD

Circuit Wizard is a revolutionary new software system that combines circuit design, PCB design, simulation and CAD/CAM manufacture in one complete package. Two versions are available, Standard and Professional.

By integrating the entire design process, Circuit Wizard provides you with all the tools necessary to produce an electronics project from start to finish – even including on-screen testing of the PCB prior to construction!

- * Circuit diagram design with component library (500 components Standard, 1500 components Professional)
- * Virtual instruments (4 Standard, 7 Professional)
- * On-screen animation
- * PCB Layout
- * Interactive PCB layout simulation
- * Automatic PCB routing
- * Gerber export

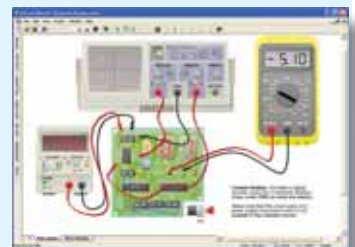This is the software used in our Teach-In 2011 series. Standard £61.25 inc. VAT Professional £91.90 inc. VAT. See Direct Book Service – pages 75-77 in this issue



Build – The Circuit Wizard way

A soft touch

IN previous instalments of *Build*, we've been using Circuit Wizard to simulate and test various circuits in order to demonstrate electronic theory. However, in this edition, we are going to look at the process of taking an electronic circuit and converting it to a printed circuit board (PCB) design that can be produced for real.

This is one of the real gems of the Circuit Wizard software as you'll see later on. We will try out some of the software's automatic conversion tools, as well as investigating some of the more advanced functionality. Once you've completed this tutorial you should be ready to enter, test and convert your own circuits to a PCB design.

The electronics industry is heavily reliant on software throughout the *product design cycle*. An example design cycle for an electronic circuit is shown in Fig.10.10.

A designer might use various tools and calculators to design the initial circuit. The circuit would then be drawn in an electronic format in a process known as *schematic capture*.

The circuit may then be simulated and analysed using a Simulation Program with Integrated Circuit Emphasis (SPICE). SPICE software runs thousands of calculations on each junction point or node of a circuit, taking into account all of the components.

There are various types of analysis that can be carried out: information can be displayed in real time (as in Circuit Wizard) to show a virtual simulation, or gathered and presented in reports or graphs/charts to show how a circuit functions over time and/or with varying characteristics.

In this way a designer can be pretty sure that a circuit will operate

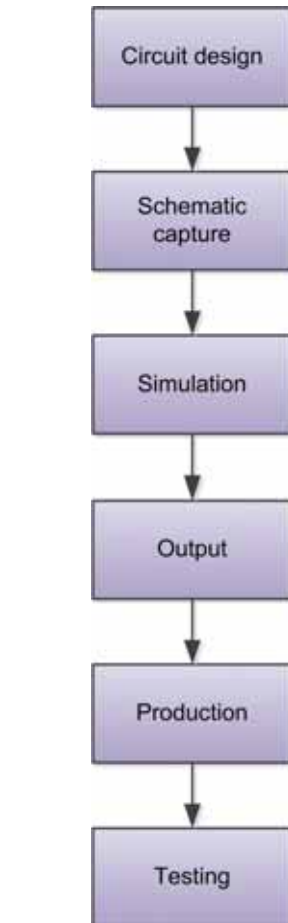


Fig.10.10. A typical design flow for an electronic circuit

correctly before spending time and money producing the physical board. Once the operation is confirmed, the information from the circuit is then used to generate a PCB design ready for production and testing of the circuit.

On the board

So, let's get to work and see Circuit Wizard in action generating a PCB! Start off by entering the circuit shown in Fig.10.11; a basic potential divider-based automatic light circuit. Ensure that you

get all of the component values and connections correct.

Once you've entered the circuit, run a quick simulation to make sure that it functions correctly. Press the 'Run' button on the toolbar and raise/lower the light level on the LDR (R2) to ensure that the LED (D1) lights under low light conditions).

Now we're ready to begin the conversion process. Click on the 'Convert to PCB Layout' button on the toolbar (Fig.10.12), or alternatively use the menu to navigate through 'Project', 'Circuit Symbols' then 'Convert to PCB Layout...'. This will start a short wizard to guide you through the conversion process.

Click 'Next' to continue to the next screen, where you will be asked to select a board type (single or double-sided) and a track size. For most home/school low voltage DC projects, with a relatively low component count and where space and component density is not a premium, we would suggest normal tracks on a single-sided board.

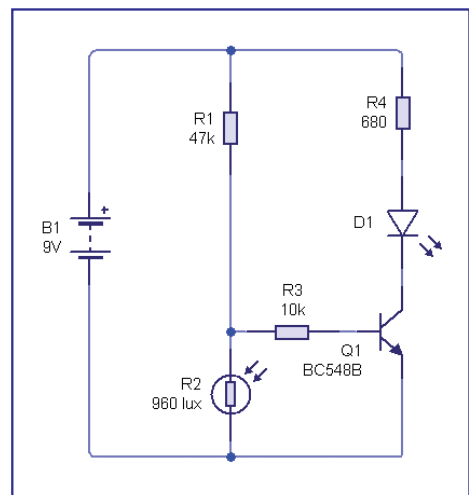


Fig.10.11. A simple light-operated switch circuit ready for conversion to a PCB layout

Therefore, select 'Single-Sided; Normal Tracks' and then click on 'Next'. The next screen allows us to change the size and shape of the board. In this case, we'll leave these as the default and click on 'Next'.

Last, on the final page, select 'Convert' and keep your fingers crossed! As Circuit Wizard carries out the conversion of your circuit to a PCB, it will animate the placing of the components, followed by the calculation of the optimum track layout. If all goes well, after

from yours. It should be noted that the automatic routing functionality of Circuit Wizard is a little limited, and it does struggle to route much more than the simplest circuits without a little help. However, we'll be looking at tactics for creating more complex PCBs later in this article.

Now that we have created our PCB layout, there are a number of exciting things that we can do with it. A superb feature of Circuit Wizard is that as well as simulating the circuit



Fig.10.13. Automatic routing confirmation

Fig.10.12 (above left). The 'Convert to PCB layout' toolbar button

a short period of time you should receive a completion message detailing the success of your conversion (Fig.10.13). Closing this should reveal your new PCB layout!

Fig.10.14 shows our example PCB layout; this may vary slightly

schematic, you can also simulate a virtual copy of your PCB design.

As with a real circuit, we must first attach a suitable power supply. Drag and drop across a PP3 9V battery from the Off-board Components in the Component Gallery (Fig.10.15).

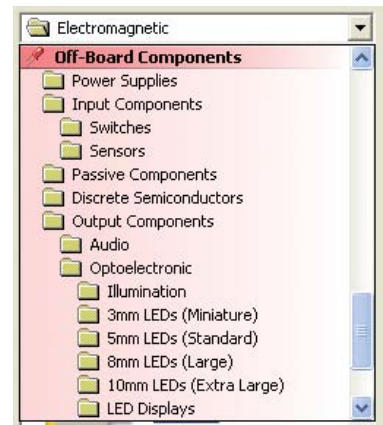


Fig.10.15. Off-board Components in the Component Gallery

Make sure that you select the Off-board Component variant, *not* a PCB Component. Wire the PP3 battery's positive and negative connections to the two-pin screw terminal block by dragging from the ends of the battery connector wires (Fig.10.14).

Virtual test

You are now ready to virtually test your PCB; start the simulation using the 'Run' button on the toolbar, as you would for a standard circuit, and try out the function of the circuit by changing the light level on the LDR. On the left-hand side of the screen you may select various different views of the PCB. The default is 'Real World', which shows a full colour representation of what the board will actually look like when constructed. 'Normal' is a more traditional PCB design view. As with schematic simulation, the PCB may also be simulated in a 'Current Flow' and 'Logic Level' view.

In 'Current Flow' view, the tracks are colour coded depending on the instantaneous voltage and 'marching ants' demonstrate the rate of flow of current (Fig. 10.16). This is particularly useful for understanding the operation of the circuit, as well

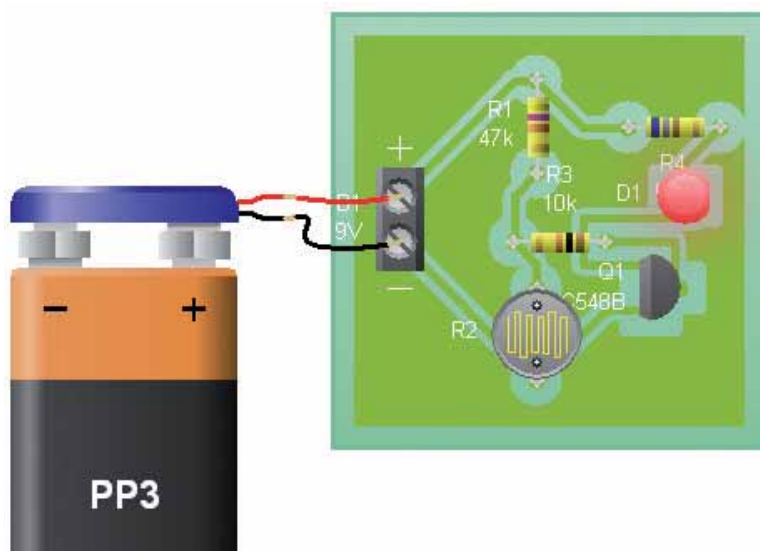


Fig.10.14. Example PCB layout for the simple light-operated switch circuit in Fig.10.11, and wiring the PP3 9V battery to the PCB

Build – The Circuit Wizard way

as providing a comparison for fault finding/testing of the completed circuit. Try simulating the circuit in this mode.

The 'Logic Level' view is excellent when dealing with digital circuits, as it highlights the logic state of pins and tracks. 'Artwork' shows the output PCB mask and 'Unpopulated' shows the physical board along with the silk screen layer, which can be very useful as a constructional aid.

Design output

How you now output your design ready for production will depend on your chosen circuit board production method. The print menu (Fig.10.17) allows you to print various artwork, including top and bottom copper layers, silk screen as well as mirrored and inverted designs.

For those using standard UV photo-resist board and a traditional etching technique, 'Solder Side (Bottom) Artwork' would be printed using a laser printer on to acetate ready for UV exposure. If you use isolation gap routing or sending

your data away to a third party for production, then the CAD/CAM menu (Fig.10.18) permits you to output the PCB data in DXF, NC and Gerber formats. Schools with Techsoft CAM equipment may copy the PCB data and paste it into Techsoft 2D PCB ready for CNC routing and drilling.

More complex circuits

As you've seen, Circuit Wizard does a nice job of automatically converting a

simple circuit into PCB with no help from the user. However, with a more complex circuit you may need to make a few tweaks and get a bit more involved in the generation process. To demonstrate this, we will convert a slightly more complex circuit; this time a 555 astable mode LED flasher circuit. Enter the circuit shown in Fig.10.19, and verify its operation through simulation.

Follow through the PCB conversion process as you did for the first

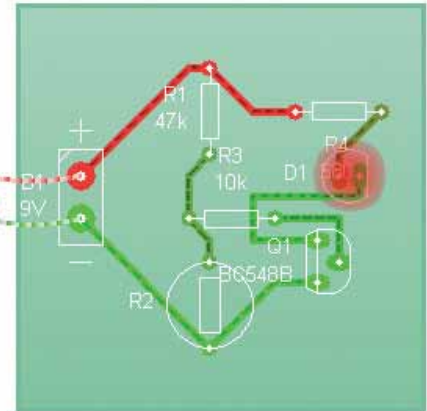


Fig.10.16. Current Flow view of the PCB

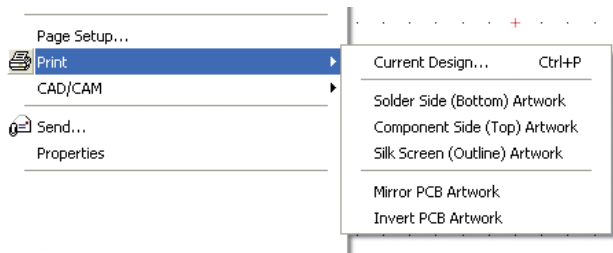


Fig.10.17. The Circuit Wizard PCB print menu



Fig.10.18. Circuit Wizard's CAD/CAM menu

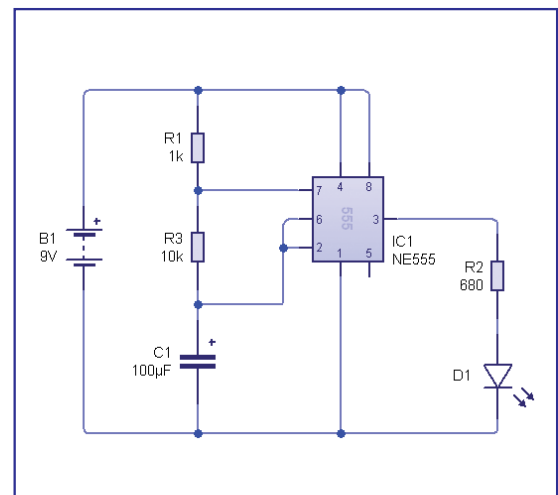


Fig.10.19. 555 astable mode LED flasher

circuit. Once complete, you may find that you receive a routing message similar to that shown in Fig.10.20, explaining that the software was unable to completely convert your circuit automatically.

In our example, you can see that only 92% of the connections could be made. It is important to note that you may be more or less successful than our example circuit, depending on how you have drawn your circuit and your software setup.

The description here is indicative of how to deal with a PCB that fails to completely route using the automatic routing feature. Inspecting the generated design (Fig.10.21), you can see that the software inserted a jumper and one connection could not be made at all (shown by a thin green line).

Note, this does not mean to say that it is impossible to wire the circuit, just that the software was unable to do so automatically and/or using the current configuration. Fortunately, we can step in here to make the job of the software a little easier.

Rats nest

Return to your circuit diagram and repeat the conversion process.

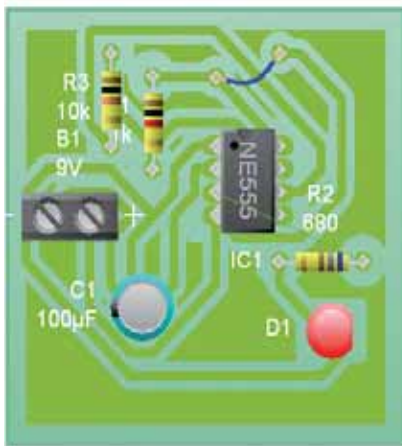


Fig.10.21. The generated PCB layout showing incomplete routing

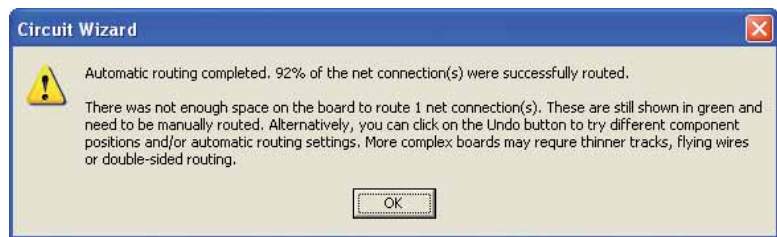


Fig.10.20. Automatic routing message for the circuit of Fig.10.19

However, this time select 'Rats Nest; No Placement or Routing' on the second screen of the wizard. You should then be presented with a blank PCB board and a set of the required components, as shown in Fig.10.22.

The pins of the components are linked by green lines showing where the connections are required. This mass of criss-crossing wires is often referred to as a 'rats nest'.

We now have to place the components on to the PCB. Rather than simply placing components at random, what we are looking to do here

is to place the components so that they can be routed with tracks in the easiest and most efficient manner. We might also require components in specific locations; for example an off-board connector at the side of the PCB, or the fixed location of an LED so that it locates in the right place on a finished product.

To achieve the former, it is essentially a case of placing the components so that there are as few cross-overs of green lines as possible. Hence, this will make the job of routing the tracks as easy as possible and avoid the requirement of jumpers/

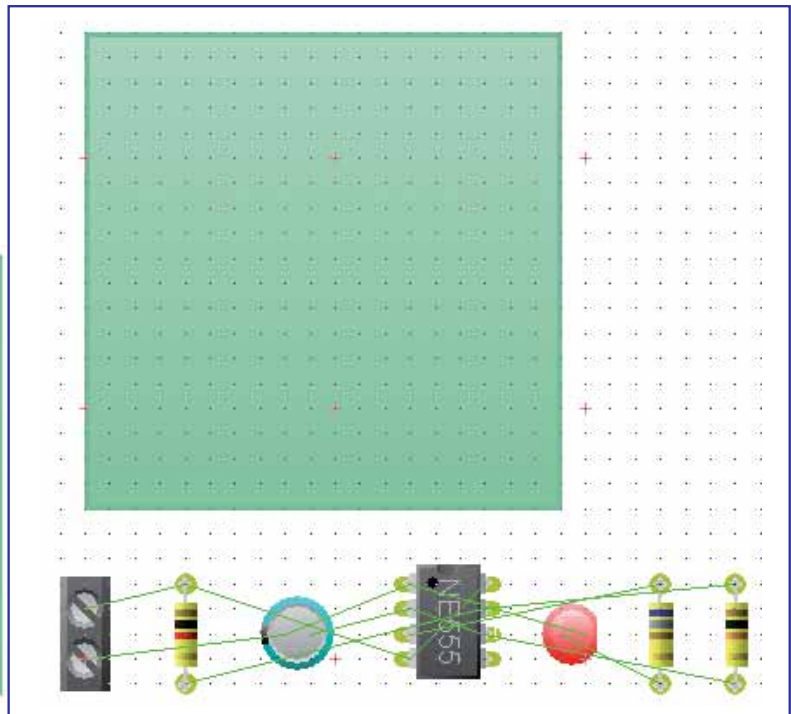


Fig.10.22. Starting point for the 'rats nest' PCB layout

Build – The Circuit Wizard way



Fig.10.23. Improved layout using 'rats nest' technique

links. As well as component position, their orientation may be altered by rotation (keyboard shortcut CTRL+R).

Notice that as you move components to a new location, the green lines will update to the nearest common point for that net. This allows you to significantly simplify the rats nest prior to routing the tracks. Fig.10.23 shows an example layout which places the battery connector at the edge of the board and attempts to leave the rats nest as clean as possible.

On track

At this point we can either start to draw our tracks manually in-line with the green nets, or instruct Circuit Wizard to attempt to automatically route the board now that we have prepared the component layout more efficiently. The author's personal preference is to have the software route the tracks automatically, then go in and modify the results as required to achieve a nice neat job. However, it's up to the individual user to experiment and decide upon their favoured approach.

To initiate automatic routing, click on the 'PCB Layout Tools' icon from the toolbar and select 'Auto Route...' (Fig.10.24). Our completed auto

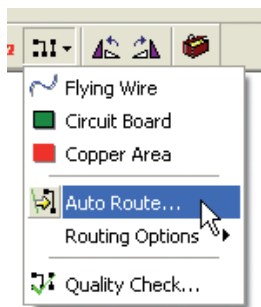


Fig.10.24. Selecting automatic routing from the PCB Layout Tools menu

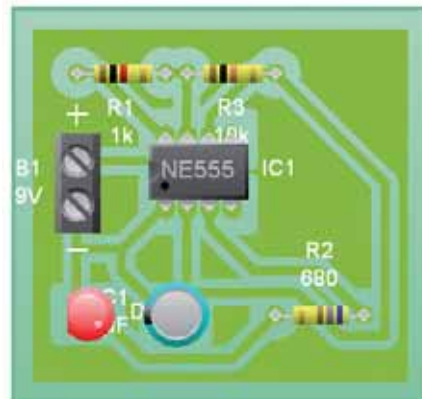


Fig.10.25. The completed auto-routed layout

Previous users of PCB drafting software will find the track drawing process familiar, whereas first-time users may find it takes a little practice for it to become intuitive. You may find it easier to use 'Normal' view for manual track drawing. Fig.10.27 shows a track manually added to the 555 circuit.

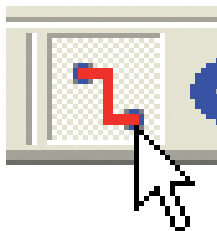


Fig.10.26. The track button

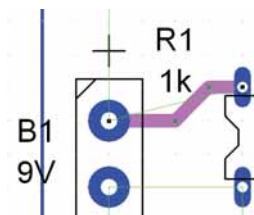


Fig.10.27. A manually added PCB track

routed layout looks as shown in Fig. 10.25. The layout is now complete and ready for virtual simulation and output for production.

If you prefer to draw the tracks manually (or indeed if Circuit Wizard fails to route your circuit automatically) select the track button from the toolbar (Fig.10.26). Tracks are started by left-clicking with additional segments added by further left-clicking and are finished by right-clicking.

Configuration options

A number of additional PCB conversion configuration options are available through the PCB wizard. On the second screen, tick 'Allow me to customise the PCB layout conversion'. You will then be provided with many additional options as you proceed through the conversion process.

One of these additional configurations is the ability to alter the physical component mappings. When converting to a PCB, Circuit Wizard selects the most appropriate PCB component footprint based on the component variant and values selected.

However, there may be times when you wish to specify a different model from that chosen by default. The screen shown in Fig.10.28 will be included in the wizard when the tick box is checked as described earlier, allowing you to alter the package

used for each component (in this case showing the package selection window for the battery, B1).

On the subsequent wizard screen you are given a number of component placement options. An interesting option is 'Take into account component positions'. When Circuit Wizard converts to a PCB it tries to order the components as you have set them out on your schematic.

This may be convenient for keeping component numbering sequential. However, in practice this is not always the best way to place components for efficient routing.

If you find your circuits are not automatically routing and/or the components are being placed in a

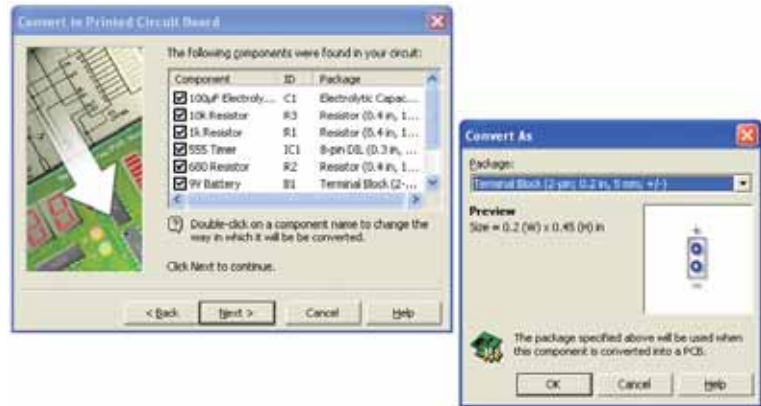


Fig.10.28. Specifying different component models

poor manner, try unticking this option. This can have a dramatic effect on the results.

Finally, one really useful tool is Quality Check. This may be accessed from the PCB Layout Tools icon on the toolbar, or by selecting 'Project', 'PCB Components' then 'Quality Check' from the menu.

This will analyse the PCB layout in comparison to your circuit diagram, to ensure that all of the connections have been made correctly, as well as various other checks. This is particularly useful when routing manually to check the connectivity of your design. Fig.10.29 shows an example Quality Check Report.

We've really only scratched the surface of the PCB conversion and drafting tools within Circuit Wizard. As with any

software tool, the best way to learn more is to get 'hands on' and use the software.

In the next edition of **Build** we'll be giving you the opportunity to do just that with a range of project circuits for you to enter, test, convert and build using all of the skills you've learnt throughout the series.

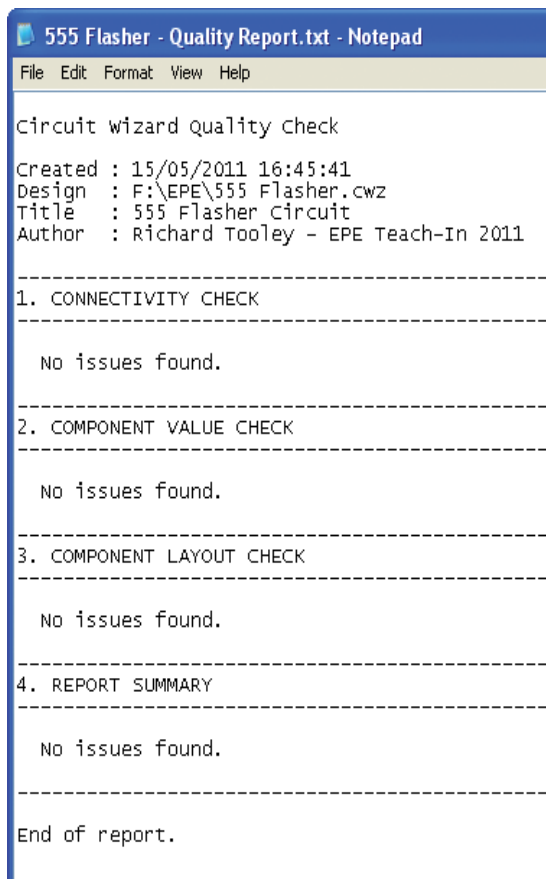


Fig.10.29. An example of a Quality Check Report

Answers to Check questions

10.1 See page 43 and page 44

10.2 (a) 83.0mA AC
(b) 180Ω

10.3 (a) Sine wave; 5ms period (frequency = 200Hz); amplitude 6V pk-pk
(b) Pulse wave; 8ms period (p.r.f. = 125Hz; high time = 2ms, low time 6ms; 25% duty cycle (mark-to-space ratio = 1:3; (amplitude 2.5V pk-to-pk

10.4 See page 46 and Table 10.1

10.5 See page 45 and Table 10.1

10.6 See page 46 and Table 10.1

Investigate

Fig. 10.30 shows a simple regulated power supply and three common items of test equipment.

1. Photocopy the diagram and add connecting wires to the diagram in order to show:

(a) How the collector current of transistor TR1 is measured

(b) How the base-emitter voltage of TR1 is measured.

2. For (a) and (b) above, list the initial adjustments that should be made to the test equipment.

3. If the output voltage of the circuit is measured at 0V and the input voltage as 15.1V, what measurements would you make, and in what order, to locate the fault? Explain your answer.

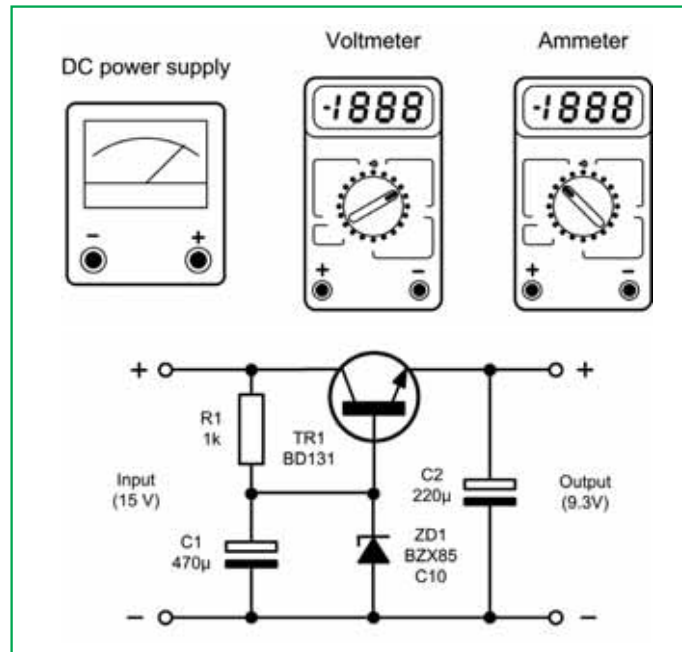


Fig.10.30. See Investigate

Amaze

In our everyday lives we are increasingly reliant on highly complex electronic systems that involve large numbers of individual component parts. However, because each individual part can be prone to failure, we need to ensure that each component has a very high reliability in order to ensure that the equipment as a whole remains free from failure. Reliability (ie, the ability to operate without failure) is thus a paramount consideration for those involved with the design of electronic equipment.

To put this into context: suppose that we know that one out of every 100000 of a particular component type is likely to break down every hour. This implies that an item of equipment that makes use of 100 of these components would break down at an average interval of 1000 hours or less than 42 days operation. In many cases this would be woefully inadequate!

The requirement for a very high degree of reliability is crucial in many applications. In satellite communications, the electronics is often expected to operate for at least 20 years without failure, simply because it would be impossible to recover and repair the satellite without spending far more than the satellite was actually worth. Added to this, there would be considerable loss of revenue while the satellite was out of service: in many cases this might amount to millions of pounds or dollars.

The failure rate of individual components depends on the situation and environment in which they are used. A satellite experiences extreme forces and temperatures during launch and manoeuvre into final orbit.

In consequence, the environment in which a satellite operates is considered severe when compared with that in which most consumer electronic equipment finds itself. For this

reason, we need to ensure that only the most reliable types of electronic component are used in satellites.

But just how reliable are the electronic components used in the circuits that you construct? A single low-cost metal oxide resistor operated within its rating and in a benign environment can be expected to have a working life of more than 1000 years. The same item fitted into a satellite would need to have a reliability that is at least ten times and preferably more than 100 times greater than this!

Next month!

In next month's *Teach-In 2011* we round up the series with a brief look back at previous parts. We shall also be including some fun revision activities as well as essential reference information. Our series concludes with a selection of electronic projects that you can build and test using Circuit Wizard.

EQUATION is SOLVED

PIC
+ PIC24
+ dsPIC30/33
+ PIC32
+ AVR
+ 8051
+ ARM (DECEMBER 2011)

= MIKROC,
MIKROBASIC or
MIKROPASCAL

everywhere

Whatever project you decide to go for, you don't ever have to change your favorite compiler. The same comfortable and intuitive IDE will always be with you across different microcontroller architectures. We have been carefully planning backward compatibility for over 500 of our library functions, so you will be able to literally copy-paste your existing codes and build them with just a few adjustments.

PIC n' Mix

Mike Hibbett

Our periodic column for PIC programming enlightenment

MPLAB-X

THIS month, we take a break from our Internet Computer series to look at a major new development from Microchip, the MPLAB-X Integrated Development Environment, or IDE.

The MPLAB IDE (and IDEs in general) provides a framework for an editor, compiler, programmer, debugger and other tools to work together. Build your project with the compiler in one window, and when it reports an error you can click on the message to be taken to the source file and offending line of code. It helps make software development a faster, more pleasant activity. While not everyone likes the integrated approach (preferring instead separate command windows, and batch file-based build scripts) it is undeniably a more efficient method for software development for the majority of users.

IDEs consist of a logical 'framework', into which various tools such as editors, compilers and debuggers can fix and then interact with each other. The term IDE could refer

to the framework alone or with a combination of several other tools. From now on, we will use the acronym 'IDE' to refer to the combination of the Integrated Development Environment, the debugger, compiler and any other third party plug-ins.

MPLAB-8

Provided for free, the existing MPLAB has been very popular. Although introduced in 1992, and now a very mature product, Microchip are still seeing over 120,000 downloads *per month*, and have sold more than one million development tools over the last year. This is not surprising, as the tools are essential for developing products using Microchip processors, but it does give an indication of the number of customers using these tools. We hobbyist are not in a small community of developers!

New releases of the software have been frequent, as Microchip release new processors and also to provide enhanced development features to help entice customers away from other chip manufacturers.

A survey of embedded software engineers taken earlier this year (see Fig.1) shows just how important an IDE is to engineers, as it appears in the top four list of important tools. Although we would have placed coffee in that group too!

MPLAB-X

So what is new about MPLAB-X? What differentiates it from any other upgrade to MPLAB?

Two things: MPLAB-X is a complete rewrite of the IDE, and now provides cross-platform support. That second point is the big one, as MPLAB is now supported on Mac and Linux systems, natively. Not just the editor, but all the tools and hardware drivers.

This cross-platform support has been achieved by porting the compiler, debugger and simulator software to Mac and Linux and by discarding the basic MPLAB-8 framework, replacing it with an existing, Open Source multi-platform IDE called NetBeans.

NetBeans is an Open Source IDE written in Java, tailored to provide an environment for developing mobile, desktop and web software in a range of languages. Why did Microchip choose NetBeans? They evaluated several Open Source and proprietary IDEs, and found NetBeans not only provided the advanced features they wanted, but also that the NetBeans development community was very responsive to the changes and additions that Microchip needed to make.

This is typical of Open Source development; if you are an organisation wanting to participate, it's important to build and be able to build good working relationships with the other developers in the group. Being an Open Source project also means that there are hundreds of developers working on it, providing new features and bug fixes. Your software engineers are often in the minority.

NetBeans is sponsored by Oracle, which, in this case, means Oracle allow some of their engineers to work on NetBeans as part of their main job. This is not unusual, and companies as large as Oracle and even IBM provide significant support to select Open Source projects, which they then use within their organisation (or even sell onto customers). It's a very positive symbiosis, and is a subject worth its own article (or book – there are already several on the subject).

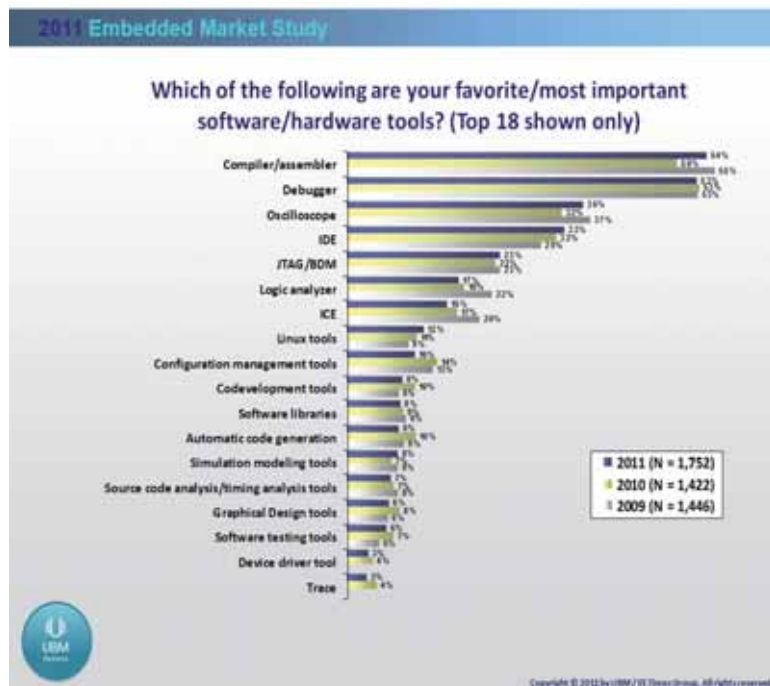


Fig.1. Survey of most important tools

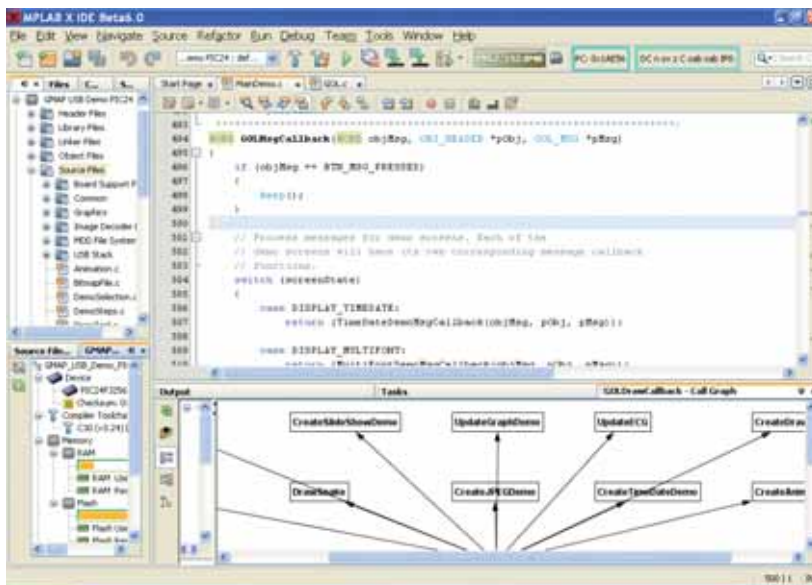


Fig.2. MPLAB-X under Windows XP

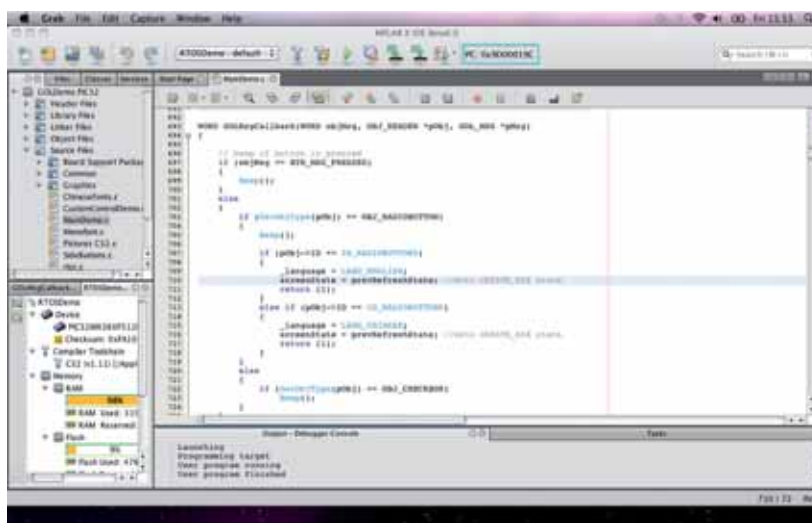


Fig. 3 MPLAB-X under Mac

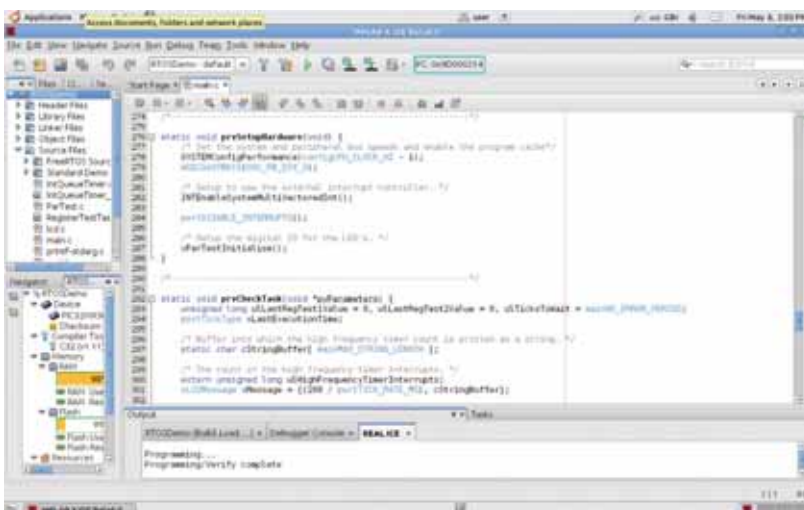


Fig. 4 MPLAB-X under Linux

As the features and supported languages have grown, so has the need for an ever increasingly powerful IDE, providing wider debug tool support and more efficient code editing facilities. The way customers use Microchip products has an effect too as they create increasingly complex products – sometimes with multiple processors requiring simultaneous debugging. The time is right for a major refresh of the supporting software tools, and the IDE in particular.

Look and feel

NetBeans does bring a new look and feel to the user interface, but Microchip have made a considerable effort to make the transition from MPLAB-8 as easy as possible. There is also a very similar look between the three different platforms, as can be seen in Fig.2, Fig.3 and Fig.4.

There will be a transition period for users who are currently committed to MPLAB-8 and do not wish to interrupt their current project's progress. Expect this to last for one to two years, but note that the future is clear, and it's going to be MPLAB-X.

MPLAB-X has been in 'Beta development' for the last 18 months, initially to a number of customers, and then to the community at large. It is currently only available for download on a special forum Microchip have set up for MPLAB-X (emphasising the 'Beta' nature of the release). The link is provided at the end of this article.

Microchip have over 800 microcontroller products available, and MPLAB-X already supports them all. There are a few 'corners' where this isn't quite true yet, such as UART support in the simulator, but Microchip are working hard to supply these. It's a massive task when you think about it, and they are doing well at the moment to improve the support.

New features

There is excellent support for integration with third-party version control software, including the major free products such as Subversion. For those not familiar with version control, this is the way that changes to source code files can be stored in a special database, allowing you to view and compare earlier versions of code, and to add comments to each version to identify the reason for the change. For professional engineers, this is an essential tool, and having it integrated into the IDE is a major bonus.

An unusual addition – one we haven't seen elsewhere – is a built-in version 'history'

feature which acts like a lightweight version control system. By clicking on a 'History' menu button you can see the contents of any file as it has been saved in the past.

A side-by-side viewer allows you to see each change to the file, and provides a simple way to revert sections of code back to an earlier version. This is an excellent feature for hobbyists who have not yet seen the value of a version control system. (Everyone should use a version control system, unless you enjoy pain!)

One of the most interesting new features is the ability to debug multiple processors simultaneously. While not a common setup, having two or more processors on your board can be difficult to debug, if you are tracing one processor while it is talking to another. Now you can debug both within the same IDE, making complex projects easier to work on.

Another good feature is that sections of source code contained within `#ifdef` or `#if` statements will be commented out if they evaluate to false. For the more complex projects (including those using the Microchip Application Library) this will be a major benefit, making it obvious what code will actually be compiled.

Import tool

Moving from MPLAB-8 to MPLAB-X is very simple. MPLAB-X has an import tool, and once a project has been imported MPLAB-X creates a new sub-directory where it holds the new, MPLAB-X specific data. None of your original files are affected, so if you try out MPLAB-X and don't think you are ready for it you can revert back to MPLAB-8 with no extra effort.

Projects created in MPLAB-X cannot be migrated back quite so simply, and, as an aside, it is for that reason that *PIC n' Mix* software projects will continue to be issued under MPLAB-8 (while MPLAB-8 is supported). You are, of course, free to import our project files into MPLAB-X.

Three versions

The IDE is released as three versions – one for the Mac, one for Linux and one for Windows. They all provide identical features. The Windows version runs under XP or later, Mac v10.5 and 10.6. Linux is supported across multiple distributions, with our review conducted on the latest release of Ubuntu.

Why support multiple platforms? Microchip have acknowledged the increasing use of Mac and Desktop Linux (Ubuntu in particular), a strong desire for Open Source tools within academia and the increase in professional acceptance of Open Source development tools generally.

As it is based on NetBeans, the IDE software is released under an Open Source licence – meaning you can get the source code and make your own modifications, at no cost. The Microchip and commercial plug-ins to NetBeans, however, are proprietary

and closed, as they have been in the past. Microchip do, however, intend to open up the interface (the Application Programming Interface, or API) to their own tools, which means you will be able to write plug-ins that can talk to, say, the Microchip debugger or compiler and display or utilise that data as you wish. This is a very exciting change, and should result in some very interesting projects to develop new plug-ins.

There are over 670 NetBeans plug-ins already that provide generic IDE-related features (such as spell checkers), and a much smaller set of plug-ins designed to integrate specifically with Microchip features. The area of 'plug-ins' is an uncharted territory. To date, only a few existing ones have been tested with MPLAB-X. For the others, some may be found to be really useful; some may not work 'out of the box', but could be modified to do so. And of course, the opportunity to create new tools previously impossible to make is now available. Interesting times ahead!

Third party plug-ins

We expect there will be an increase in the number and type of third party plug-ins available for MPLAB-X as people find out just how (relatively) easy it is to develop NetBean plug-ins. There is a wealth of examples, experience and support out there on the Internet because the NetBeans IDE is itself so widely used and popular. We look forward to seeing some novel tools in the future. (If anyone is interested, how about a code coverage tool working with the debugger?).

Microchip have set up a dedicated web forum to handle the feedback from users as they ready the IDE for formal release, which must give them quite a headache with all the questions, requests for help and new features coming in. All this across three PC platforms, not just Windows!

As this is a more powerful IDE than MPLAB, one has to ask if those of us with older PCs are going to suffer with slower user interface interaction, or longer build times. The minimum PC specifications are good, at an 800MHz processor and 512MB RAM, and our experience with it was that it is not noticeably slower. Rather surprising given that the IDE is written in Java, but perhaps the developers of NetBeans have given careful thought to the efficiency of their code for us cheapskates.

Comparing the build time of a large project under MPLAB-X on Windows and Linux did show something rather surprising – building under Linux (or Mac, we were told) is *significantly* faster. Even more reason to move away from Windows!

References

MPLAB-X download: <http://devupdates.microchip.com/mplab/>

MIACTM

Now you are in control



The MIAC rugged PICmicro microcontroller is an industrial grade controller which can be used to control a wide range of different electronic systems: for mains switching, motor control, sensor monitoring and much more.

Free Flowcode 3 with every MIAC



- ▶ Rugged PIC 18F4455
- ▶ Programmable from USB - download software provided
- ▶ Compatible with third party PICmicro, BASIC and C compilers
- ▶ Includes free Flowcode 3 graphical programming software (no upgrade rights)
- ▶ 8 digital or analogue inputs
- ▶ 4 relay outputs - 8A
- ▶ 4 motor outputs with speed control - 12V, 500mA
- ▶ 4 line 16 character display
- ▶ Control keypad
- ▶ Fully networkable via built in CAN bus
- ▶ Lab View and Visual Basic compatible - DLL supplied
- ▶ In-Circuit Debug over USB with FlowKit

MATRIX

www.matrixmultimedia.com

What's all this noise about?

CHAT ZONE contributor **alec_t** posted the following question about simulating noise in LTSpice.

LTSpice provides a noise analysis option, but as far as I can see it does not have a component which can be easily parameterised to simulate a controllable noise source. The only workaround I've managed is to set the Value property of a voltage source equal to 'wavefile=.\\mynoisefile.wav', where the wav file is a recording of white noise or similar.

That seems a bit of a kludge. Does anyone know of a simpler method?

A typical random noise signal is shown in Fig.1. Fig.2 shows a sinewave suffering from a significant amount of random noise. These were generated using LTSpice and are what we assume alec_t may be after, although it is not clear exactly what he wants in terms of the parameterisation and controllability

of the noise source. Another possible interpretation of 'controllable noise source' is a signal source which will contribute a specified amount of noise to an LTSpice noise analysis.

Before discussing LTSpice though, we will take a look at some of the basic concepts relating to noise in electronic circuits.

Noise floor

The fact that the components in any electronic circuit or system generate random noise means that there is always a certain level of noise, even with no signal present. The circuit's noise floor relates to noise *within the circuit*, this is different from noise *within the input signal*. If the properties of the required signal are known there are techniques which can extract signals that are smaller than noise present within the signal, for example, due to interference.

There are a variety of types of random noise generated within electronic

circuitry, these include: thermal noise, shot noise, flicker noise, and avalanche noise. This noise generated is fundamentally due to the discrete nature of electricity at the atomic level – electric charge in circuits is carried in packets of fixed size on electrons.

Random noise may be classed according to the frequency, or range of frequencies, present. White noise has the same power throughout the frequency (f) spectrum, whereas 1/f noise (or pink noise) decreases in proportion to frequency. For 1/f noise, there is the same amount noise power in the bandwidth of say 100Hz to 1kHz as there is in 1kHz to 10kHz, whereas for white noise there would be 10 times as much power in the bandwidth 1kHz to 10kHz as 100 to 1kHz, because it is 10 times larger.

The difference between the signal and the noise is often of great importance. It is expressed as the signal-to-noise ratio (SNR), usually in decibels (dB) and based on the ratio of noise *power* (hence the v^2 terms in the equation):

$$SNR = 10 \log_{10} \left(\frac{v_s^2}{v_n^2} \right)$$

Where v_s is the rms signal voltage and v_n is the rms noise voltage. When using or quoting SNR values, the bandwidth (range of signal and noise frequencies considered) should be quoted because noise power is frequency dependent and noise may be present well outside the range of signal frequencies of interest.

Thermal noise

Thermal noise (also known as Johnson noise) is a fundamental property of resistors (including the internal resistances of sensors and semiconductor devices), which results in a white-noise voltage across the terminals of any resistor, even when it is not connected in a circuit. This is a fundamental property of any resistor, so whatever we do we cannot get lower noise than the thermal noise. Thermal noise cannot be reduced by improved component manufacture, however, as it is temperature-dependent, reducing the temperature will reduce the noise.

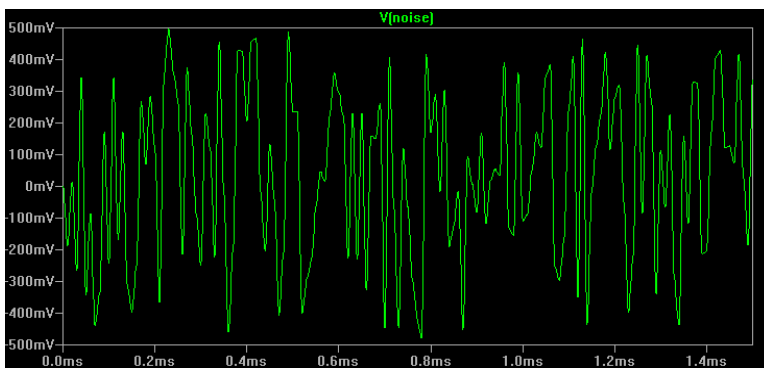


Fig.1. Random signal generated using LTSpice

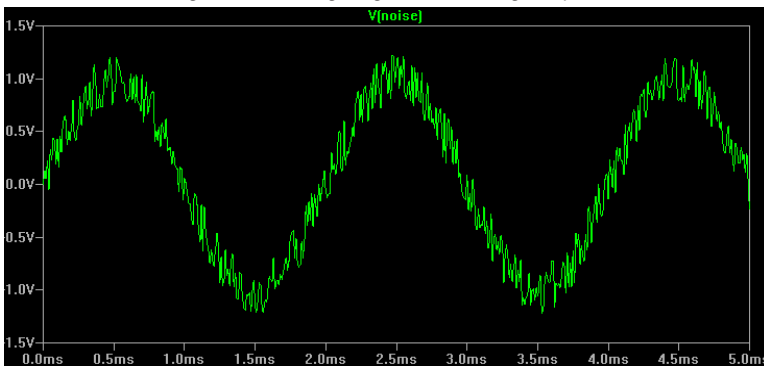


Fig.2. A noisy sinewave generated using LTSpice

The thermal noise rms voltage across a resistor is given by:

$$v_{N,rms} = \sqrt{4kTR\Delta f}$$

Where k is a physical constant known as Boltzmann's constant ($1.38 \times 10^{-23} \text{ J/K}$), T is the temperature in kelvin (K), R is the resistance in ohms (Ω), and Δf is the bandwidth of interest in hertz (Hz) (ie, the range of frequencies over which you are measuring the noise). Δf is pronounced 'delta f', the delta symbol means 'change in' and so Δf represents a range of frequencies.

The fact that a bandwidth has to be specified in order to get a noise voltage means that noise figures are often expressed in 'volts per bandwidth unit' form rather than simply as voltages (have a look on datasheets for ICs such as op amps and you will see noise figures expressed this way). This value is known as noise density. If we divide both sides of the above equation by the square root of the bandwidth ($\sqrt{\Delta f}$) we get:

$$\frac{v_{N,rms}}{\sqrt{\Delta f}} = \sqrt{4kTR}$$

The value $\sqrt{4kTR}$ has units 'volts per root hertz' often written as $\text{V}/\text{Hz}^{1/2}$ or V/Hz . So, for example, the noise from a $1\text{k}\Omega$ resistor at 27°C (300K) is:

$$\sqrt{4 \times 1.38 \times 10^{-23} \times 300 \times 1 \times 10^3} \\ = 4.07 \text{ nV}/\text{Hz}^{1/2}$$

If we were interested in a bandwidth of say 20kHz , the thermal noise voltage from this resistor would be:

$$4.07 \text{ nV} \times \sqrt{20 \times 10^3} = 576 \text{ nV}$$

Statistical analysis of the properties of thermal noise shows that the instantaneous peak noise voltage will be less than five times the rms (average) value for 99% of the time.

Shot noise

When current flows through a resistance (in a resistor or active device) it will generate additional white noise above the thermal noise due to the quantum nature of electric current at the atomic level (electric current is the flow of discrete charge carriers – eg, electrons), rather than a 'continuous' flow. This noise is known as 'shot noise' and, like thermal noise, is due to fundamental physics and cannot be reduced. For an applied current of I in amps (A) the shot noise is given by:

$$I_{N,rms} = \sqrt{2eI\Delta f}$$

where e is the electronic charge (charge on one electron = $1.6 \times 10^{-19} \text{ C}$

(coulombs)) and Δf is the bandwidth as before. For a current of $1\mu\text{A}$, this is $0.57 \text{ pA}/\text{Hz}^{1/2}$, which is about 80 pA over a 20kHz bandwidth. Shot noise is an important source of noise in semiconductor devices such as diodes and transistors.

Flicker noise

In addition to thermal noise and shot noise, resistors and active devices produce yet more noise for various and often complex reasons. This noise is called 'flicker noise' and takes the form of $1/f$ noise, typically having a $1/f$, or similar, relationship with frequency.

Unlike thermal and shot noise, the flicker noise in resistors (and other devices) depends on the component type and manufacture, and can even vary quite widely for components of the same type. For a decade bandwidth (frequency range of 1 to 10 times), the flicker noise for typical resistors varies from tens of nanovolts to a few microvolts, depending on type and quality. Carbon composition resistors produce the highest flicker noise and wirewound resistors the lowest.

Avalanche noise

Avalanche noise is produced by Zener diodes (or other diode junctions undergoing Zener or avalanche reverse breakdown). Avalanche noise is much larger than shot noise and so Zener diodes can introduce a lot of noise into a circuit. For this reason, they should be avoided in low noise circuits, even though they are a temptingly easy way to produce a stable voltage reference. On the other hand, this may be useful if what you need is a source of noise.

Noise is not necessarily modelled in a very detailed way in Spice simulators, for example resistor noise models may only include thermal noise.

Input or output reformed

The noise (density) produced by a circuit can be input referred, or output referred. This is illustrated in Fig.3. The total noise produced by a circuit (Fig.3a) can be seen as equivalent to replacing the circuit with a noise-free version and accounting for the noise by adding a noise voltage source to the input or output to represent all the noise the circuit (Fig.3b and Fig.c).

The value of the input and output noise are related by the circuit's gain with respect to the input noise source. In a similar way, the contribution of any individual component in the circuit can also be represented by an input-referred or output referred value.

The LTSpice analogue simulator to which `alec.t` refers can be downloaded free in its full form from the Linear Technology website, www.linear.com/designtools/software/. The 'Spice' part of the name refers to the acronym of 'Simulation Program with Integrated Circuit Emphasis' – a *de facto* industrial standard for computer-aided electronic

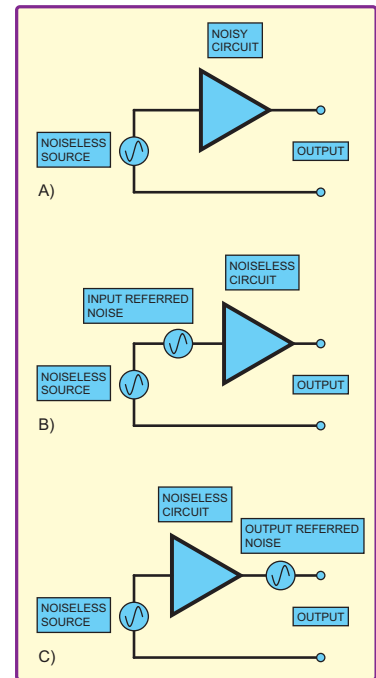


Fig.3. Representing noise. (a) A noisy circuit is driven by a noiseless signal source. (b) The circuit noise represented by an input referred noise source driving a noiseless version of the circuit (c) similarly, output referred noise

circuit analysis with many commercial versions. It was originally developed in the early 1970s at the University of California, Berkeley.

As `alec.t` indicates, LTSpice, in common with most other SPICE simulators, has a noise analysis capability. Spice noise analysis works out the noise produced by each component using formulae such as that for the resistor discussed earlier. We will start by looking at this, before showing how we can generate a random signal like that in Fig.1, and discuss how this differs from noise analysis.

The circuit in Fig.4 can be used to demonstrate noise analysis. The voltage source is noise free (it is an ideal voltage source as far as the noise analysis is concerned), so the noise contributions to the output (at node *pd*) will be due to the two resistors. Using the value from the calculation we did earlier, each resistor will

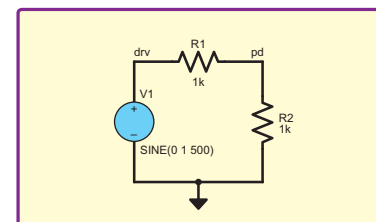


Fig.4. A simple circuit to illustrate noise analysis in LTSpice

produce a noise density of $4.07\text{nV}/\text{Hz}^{1/2}$ at a temperature of 27°C , which is the default simulation temperature for LTSpice.

Circuit gain

Noise calculations have to take account of the effective circuit gain from each component to the output. For the circuit in Fig.4, the gain with respect to the noise from each resistor is 0.5, due to the potential divider effect of the two equal resistors. Thus, each resistor contributes $0.5 \times 4.07\text{nV}/\text{Hz}^{1/2} = 2.035\text{nV}/\text{Hz}^{1/2}$ of noise to the output signal at node *pd*.

LTSpice calculates the individual noise contribution of each component and is able to plot these against frequency. These are output-referred values, but they can be divided by the input-to-output gain of the circuit to find the input-referred noise contribution.

LTSpice will calculate the total noise density due to all components in the circuit. To do this, the square of the noise density is multiplied by the square of the gain relevant to each component, and these values are totalled (squares because this is a power-based calculation). This gives the square of the output-referred total noise density – taking the square root gives the noise density. As with individual components, dividing the output referred noise density by the input-to-output gain of the circuit gives the input-referred value.

As resistor noise is equal at all frequencies, and the gain from both R1 and R2 to the output is 0.5, the total output noise density for the circuit in Fig.4 due to the two resistors contributions of $4.07\text{nV}/\text{Hz}^{1/2}$ will be:

$$\sqrt{(0.5)^2(4.07 \times 10^{-9})^2 + (0.5)^2(4.07 \times 10^{-9})^2}$$

which is $2.88\text{nV}/\text{Hz}^{1/2}$ at all frequencies (output referred). The input to output gain (from node *drv* to node *pd* in

Fig.4) is 0.5, so the input referred noise is $2.88/0.5 = 5.76\text{nV}/\text{Hz}^{1/2}$ at all frequencies. In more complex circuits we would have to take account of the frequency dependence of noise from active devices, and the gain calculations would be more difficult and frequency dependent, but LTSpice will do that work for you.

Noise analysis

To run a noise analysis, select Edit Simulation Command from the Simulation menu while in the schematic editor. In the Edit Simulation Command window, select the Noise tab and fill in the parameters as required (see Fig.5).

The Output parameter is written as V(x) where x is the node in the circuit which will be regarded as the output for noise analysis (*pd* in this example). The Input parameter identifies a voltage or current source, which is the input to the circuit, and to which input referred noise will relate.

The remaining parameters determine the range of frequencies over which the noise analysis will take place, and the frequency points at which LTSpice will make noise analysis calculations. Click OK, and then on the schematic, to complete setting up the command.

Running the noise analysis will cause a blank waveform window to open. Right click this and select Add Traces. For the example circuit in Fig.4 you will be able select the following noise values to display:

V(inoise)	Input referred total noise
V(onoise)	Output referred total noise
V(r1)	Output referred noise contribution from R1
V(r2)	Output referred noise contribution from R2
gain	Gain of the circuit from input to output

The 'input' and 'output' are as specified in the noise analysis

command set up in the window shown in Fig.5. Results from the analysis of the circuit in Fig.4 are shown in Fig.6. The values agree with our calculations above. Note that the noise density scale is on the left and the gain scale is on the right.

AC analysis

The noise analysis we have been discussing does not involve waveforms which we can 'see', as we would when looking at a noisy signal on an oscilloscope (like Fig.1 and Fig.2). The noise analysis performed by Spice is related to AC Analysis, which is typically used to plot circuit gain and phase shift against frequency. To perform a time-based simulation of a noise signal we have to address a couple of potential problems, first that noise has infinite bandwidth and second that it is random.

The problem with the large bandwidth of noise is that the noise voltage changes will occur much more rapidly than in the signal of interest. This is clear in Fig.2 – the noise has a much higher apparent frequency than the sinewave. From a simulation point of view, this implies we need much longer run times for (say) a sinewave plus noise, than for just the sinewave. We have to make sure the simulator uses a sufficiently small time step in its calculations; otherwise it will miss the detail in the noise. If you want to simulate noisy signals in the time domain you need to take account of this.

Random numbers

The second issue is that noise is random, so to simulate a noisy signal we have to generate random numbers. There are a number of computer algorithms which will do this; actually they produce pseudorandom numbers – sequences of values which have statistical properties close to true random values, but which are

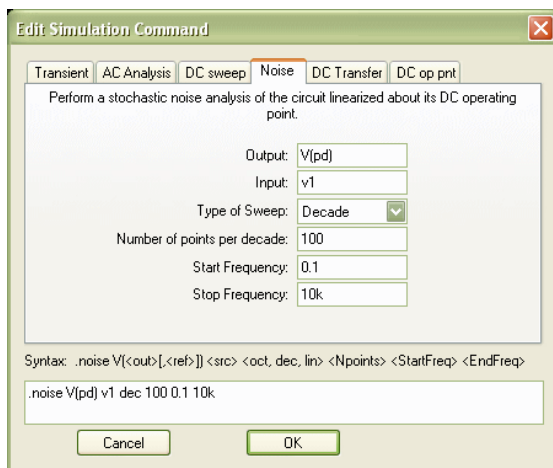


Fig.5. Setting up a noise analysis in LTSpice (for the circuit in Fig.4)

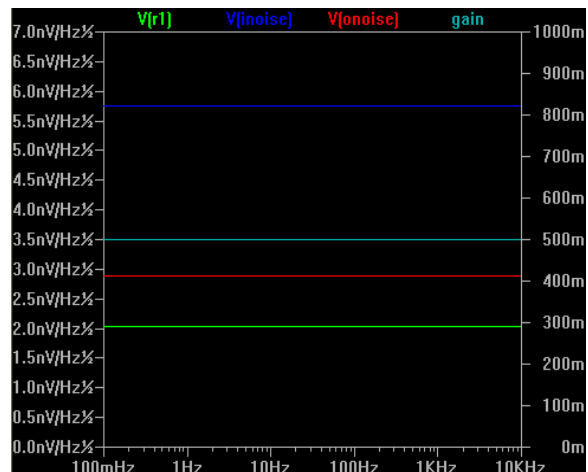


Fig.6. LTSpice noise analysis results for the circuit in Fig.4

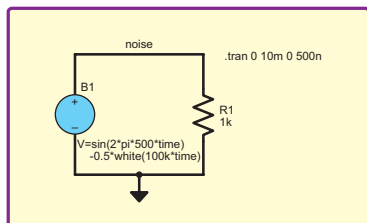


Fig.7. LTSpice schematic for generating a sine-plus-random waveform. The source will not contribute to a Spice noise analysis

in fact fully predictable. Fortunately, we do not have to work this out from scratch to simulate noise because LTSpice provides random number generation for us.

The usual voltage and current sources (V and I components) which we use for power supplies and signal sources in our simulation can provide DC, sinewaves, pulse trains, exponentials, decaying sinewaves, frequency-modulated sinewaves and arbitrary waveforms using piecewise linear (PWL) or .wav file based definitions. The latter, as `alec_t` points out, can be used for a random signal, but is inconvenient if you do not have a suitable file available.

The V and I components do not have a built-in random signal capability, however, they are not the only signal sources provided by LTSpice. On the basic component list you will also find BV and BI. These are arbitrary behavioural voltage or current sources.

The term behavioural refers to the approach to modelling circuits in terms of their behaviour rather than by drawing a schematic of their actual physical implementation. This approach is useful for modelling electronic systems before a fully detailed design is performed, to check that the concept of the design is valid. Such models are also useful for manufactures of ICs, such as op amps.

Mathematical expressions

The arbitrary behavioural voltage or current sources in LTSpice allow the voltage to be set using a mathematical expression. These expressions can use node voltages, node voltage differences, circuit element currents, *time* (the current time in the simulation) and the constant π . The expressions can be built using a set of mathematical functions such as $+$, $-$, $\sin(x)$, $\max(x,y)$, \sqrt{x} and $\log(x)$ – like those you would expect to find on a scientific calculator. For the full list consult the LTSpice help on BV and BI.

The available mathematical expressions include random number generators `rand(x)`, `random(x)` and `white(x)`. These all produce a random number depending on the integer value of x (imagine a look-up table of random values, indexed by

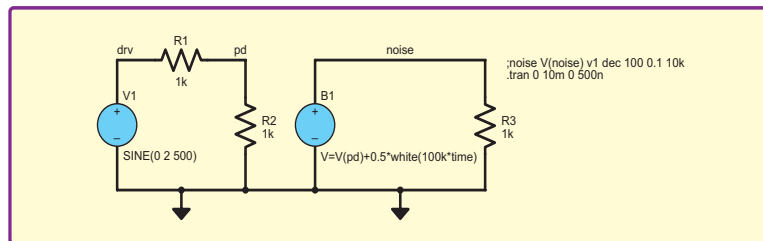


Fig.8. LTSpice schematic for adding a random waveform to a copy of an existing signal. This signal will also inherit noise analysis contributions from the original

x). `rand(x)` and `random(x)` produce numbers in the range 0 to 1, whereas for `white(x)` the range is -0.5 to 0.5 . The functions also vary in terms of the smoothness of transition of one value to the next, with `white(x)` being the smoothest.

If we make x equal to *time*, these functions will produce a random value which varies with simulation time – in other words, a ‘noise’ waveform. However, because the numbers are pseudorandom, the same random waveform will be produced each time a simulation is rerun.

Random valves

To set up a random voltage source add a BV element to your schematic and edit the value attribute, which defaults to $V=F(\dots)$, to something like $V=\text{rand}(\text{time})$. This will give you a random waveform varying between 0 and 1V. Modify the expression to create the voltage levels required. For example $V=1+2*\text{rand}(\text{time})$ will give you a 2V peak-to-peak random signal on top of 1V DC.

The function `rand(x)` produces a different random value for each integer x , so $V=\text{rand}(\text{time})$ will cause the voltage to change every second. We will probably need it to change faster than this, which is easily achieved by multiplying time by an appropriate value. For example, to get a new voltage every $10\mu\text{s}$, multiply time by 100,000 (1 divided by the required update interval), writing the value attribute as $V=\text{rand}(100k*\text{time})$.

To create a signal with randomness added to it we can use the other mathematical functions available with the BV source to define the signal, for example, for a 1V, 500Hz sinewave, with 0.5 peak-to-peak random signal superimposed use:

$V=\sin(2*\pi*500*\text{time})+0.5\text{white}(100k*\text{time})$

This is the signal shown in Fig.2. The LTSpice schematic is shown in Fig.7. The signal produced by B1 will not contribute to a noise analysis, we will return to this fact shortly.

The mathematical expression for the BV source can also refer to other node voltages, so we can take an existing signal and add the

random waveform to a copy of it. For example, Fig.8 shows the circuit we used earlier with a 0.5V peak-to-peak random signal added:

$V=V(\text{pd})+0.5*\text{rand}(100k*\text{time})$

This will also produce a 1V sinewave the random signal added, as in Fig.2.

If you run a noise analysis of the circuit in Fig.8, with V1 as the input and `v(noise)` as the output, the figures will be the same as those for Fig.5. The random signal will not contribute to the noise analysis because all voltage sources are noise-free as far as the LTSpice noise analysis is concerned, whatever signal they are producing. This also applies to Fig.7, as we noted earlier. Resistor R3 does not contribute noise in this case because the noise node is driven directly by the ideal voltage source B1.

If you would like the noise analysis to be at least approximately compatible with your random signal, then the circuit in Fig.8 may be useful. By contriving suitable resistor values, and/or multiplying the signal at the node *pd* by a suitable factor in the expression for the BV source, the noise node can have any noise contribution you like. We can make the original sinewave very small (eg, microvolts) so that it gets scaled up to the right level by the same factor which is boosting the noise contribution. For example, by setting:

V1 to $V=\text{SINE}(0\ 2u\ 500)$

B1 to $V=1e6*V(\text{pd})+0.5*\text{white}(100k*\text{time})$

we get the same sine-plus-random waveform as before and $2.88\text{mV}/\text{Hz}^{1/2}$ of noise analysis contribution from B1 (rather than the nanovolt levels at node *pd*). This value is not meant to be equal to that of the random signal; this just illustrates the possibility of controlling the noise analysis contribution.

Alec_t asked for a parameterised and controllable noise source in LTSpice, but we are uncertain about exactly what his requirements are. Hopefully, the discussion here will have provided some inspiration for achieving what he wants.

INTERFACE

Long-lived converters

IN THE world of computing and electronics, it tends to be taken for granted that things will be forever changing, and that the latest gizmos of today will be obsolete by tomorrow. However, there are some electronic gadgets, components, or whatever, that do 'buck the trend' and remain available and in use for many years.

When it comes to electronic components, I suppose that there are few examples of semiconductors that have managed to stay in production from one decade to the next. Most of those that have managed this feat are simple devices such as transistors and diodes. Some of these must be approaching their golden jubilees!

There are very few integrated circuits that manage to remain current for many years, but there are some. These are mostly the devices that became the 'industry standards' of their day, and for many applications have not been replaced by anything better.

Standard A/D

Many of the analogue-to-digital (A/D) and digital-to-analogue (D/A) converters featured in *Interface* articles over the years have disappeared from the marketplace. By contrast, the National Semiconductors ADC0800 and DAC0800 series of chips (Fig.1) are early devices, but have remained in production while many of their competitors have become obsolete. They still represent an attractive option for many applications, as they offer excellent performance but are now relatively cheap. Another advantage is that they can still be obtained in easy-to-use DIL packages, although



Fig.1. Unlike many computer related chips these days, the DAC0800 and ADC0804 are available in standard DIL plastic packages. They are also available in other forms, it is devices with an 'LCN' suffix that have a DIL package

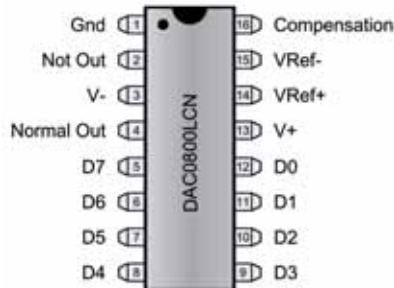


Fig.2. The pinout diagram for the DAC0800LCN. Unusually for a computer interface chip, it operates from dual balanced supplies, but the digital inputs still operate at standard 5V logic levels

surface-mount types are also available if you should need them.

The DAC0800 is the digital-to-analogue converter, and it is an 8-bit type that has parallel inputs that operate at standard CMOS or TTL logic levels. The pinout diagram for the DAC0800LCN, which is the standard 16-pin DIL version, is shown in Fig.2.

Many D/A converters operate from a single +5V supply and provide an output voltage range that is typically from 0 to 2.5V. Signal processing is then

used to provide the required output voltage range.

The approach taken with the DAC0800LCN is different, and it operates from dual balanced supplies, rather like an operational amplifier (op amp). No +5V supply is required. It can provide a large output voltage range without the need for any amplification, although in most applications it is necessary to at least use some buffering at the output.

There are actually two outputs terminals, which are the Normal and Not types. The Not output is at zero volts with an input value of 128, with higher values raising the output voltage in the positive direction. Lower values send the output negative.

An opposite action is obtained at the Normal output, with high input values producing negative output potentials, and lower values giving positive output voltages. An output voltage range of something like -12V to +12V is easily achieved without using any external amplification.

Current sinks

The voltage changes at the two outputs might seem slightly illogical, with the two outputs operating with the opposite sense to what one might

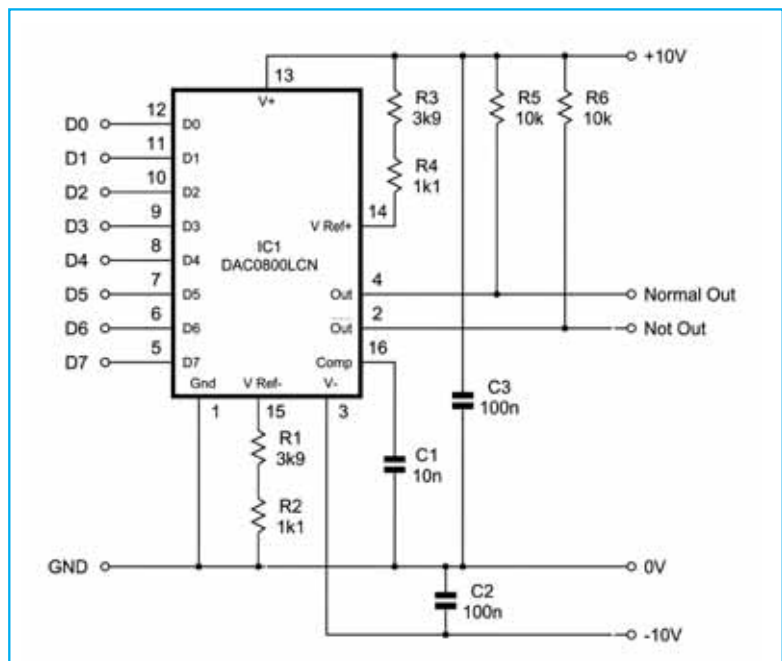


Fig.3. The basic DAC0800LCN digital-to-analogue converter circuit. The +10V supply also acts as a reference voltage

reasonably expect. The reason for this is that the outputs are actually current sinks, and the input values are converted to corresponding output currents.

Using load resistors at the output produces a simple voltage to current conversion, but the higher the output current, the greater the voltage developed across the load resistors, and the lower the output voltage. Hence higher values result in the voltage at the Normal output heading in a negative direction.

This ability to produce positive and negative output voltages, together with the anti-phase outputs, is clearly a bit 'over the top' for many applications. However, in the right applications it can greatly simplify matters. For example, with a computer controlled power supply that must provide dual balanced outputs there is no need for any circuits to generate an accurately balanced negative voltage from the positive output signal from the converter. The DAC0800LCN can provide suitable negative and positive output potentials.

The resolution is only seven bits for each polarity, but this gives 127 different output levels for each one, which is perfectly adequate for many purposes. Actually, the output is slightly lopsided in that there are 128 positive output voltages from the Normal output, but only 127 negative ones. The missing negative output voltage is sacrificed to provide the central 0V output level. There are other operating modes available, including unipolar types, but there are probably better alternatives available unless bipolar operation is needed.

Basic DAC0800LCN circuit

The basic converter circuit for a DAC0800LCN is shown in Fig.3. This chip does not have built-in data latches, and the 8-bit input bus (D0 to D7) must therefore be fed from a latching output port. C1 is a compensation capacitor that is needed to prevent instability, as are supply decoupling capacitors C2 and C3. R5 and R6 are the load resistors at the Normal and Not outputs respectively. These must be high quality components, having low tolerance figures and good thermal performance, since errors in their accuracy will cause corresponding errors in the output voltages.

In this circuit, they are fed from the main +10V supply rail, which must be highly accurate and stable as it is also acting as a reference level. It is not essential to use the positive supply rail as the reference voltage, and it is perfectly acceptable to power the circuit from something like dual 12V supplies while using a separate reference source for R5 and R6.

Resistors R1 and R2 provide reference currents to the V Ref- input, and the equivalent function is provided by R3 and R4 at the V Ref+. If a separate positive reference level is used,

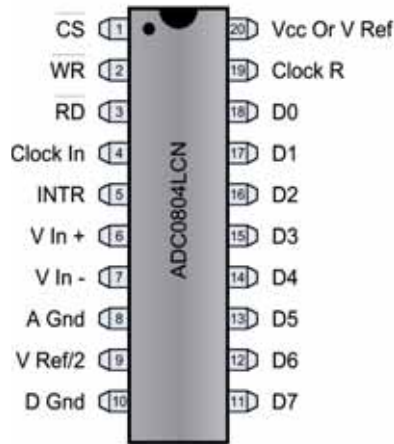


Fig.4. Pinout details for the ADC0804LCN. It is designed to interface to the buses of an 8080 microprocessor, but it can also be used in stand-alone applications with the aid of some control logic

R3 and R4 should be fed from this instead of the positive supply rail. For optimum accuracy, R2 and R4 can be replaced by high quality 2.2kΩ preset resistors (potentiometers). These are then adjusted for 0V at their respective outputs with an input value of 128.

ADC0804LCN

The fact that the ADC080x range of analogue-to-digital converters were designed to interface easily to the buses of an 8080 microprocessor indicates that it is not exactly a new series of devices. Although designed for easy use with an 8080, these chips will operate just as well in the role of conventional analogue-to-digital converters when combined with some simple control logic and an

8-bit input port. The chips in the ADC080X series are essentially the same, and they differ only in their operating temperature ranges, packages, and degree of accuracy.

The ADC0804LCN featured here has a standard 16-pin DIL plastic package, operates over a temperature range of 0°C to 70°C, and has an accuracy of +1 LSB. Its pinout diagram is shown in Fig.4, and the basic circuit for an analogue-to-digital converter using this device is shown in Fig.5.

The circuit is powered from a +5V supply, which must be highly stable as it also acts as the reference voltage when using the basic configuration of Fig.5. The supply current is no more than 2.5mA. D0 to D7 are the eight digital outputs, which are tri-state types. When not used with the data bus of a microprocessor, they can be used with any input port that operates at normal 5V CMOS or TTL logic levels.

There are separate digital and analogue ground terminals, which can help to avoid problems with digital noise being coupled into the analogue circuits. However, in most cases they are simply wired to the 0V supply rail using the shortest possible connections.

The circuit responds to the voltage difference between the two analogue inputs, but differential operation is not needed in most applications. The V In- input is then connected to the 0V supply rail, and the input voltage is applied to the V In+ input.

The reference voltage is normally the 5V supply rail, but the range covered by the converter can be altered by altering the voltage at pin 9, which is normally at half the reference potential. By using this feature and the differential inputs it is possible to

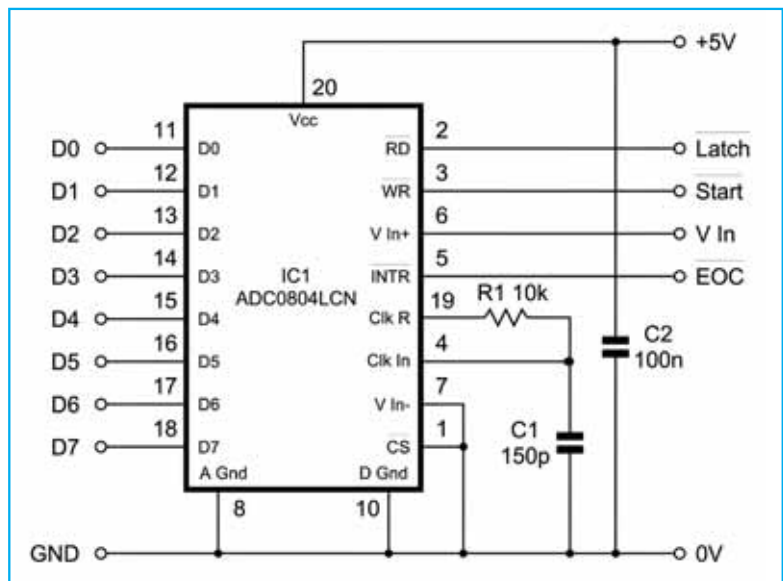


Fig.5. A simple digital-to-analogue converter based on an ADC0804LCN. The +5V supply rail also acts as the voltage reference source

obtain virtually any desired input voltage range, but this is not a topic that will be pursued further here.

Speed

The ADC0804LCN is a successive approximation converter, and as such it is not particularly fast. An external clock signal can be applied to pin 4, or the simple *C-R* clock circuit built into the chip can be used. The built-in clock oscillator will usually suffice, and this is a simple relaxation type.

In Fig.5 the timing components are C1 and R1. The output frequency in hertz is approximately equal to $1/1.1CR$, which is something over 700kHz using the specified values, although it is likely to be a little lower in practice due to the internal capacitance of the chip. Optimum accuracy is achieved at around 640kHz, so the specified values should give good results.

The absolute maximum conversion rate for the ADC0804LCN is just under 10000 conversions per second, and in practice it is likely to be significantly less than this. While a rate of a few thousand conversions per second is clearly inadequate for

some applications, it is more than adequate for most. Anyway, when using a virtual serial port to interface the circuit to a PC, it could well be the port, rather than the converter, that is the limiting factor.

In control

When using a digital-to-analogue converter, it is not normally necessary to have any form of handshaking with the computer, or to have any control logic. It is simply a matter of outputting values to the converter, which almost immediately produces a change in the output voltage.

Matters are not as simple as that with an analogue-to-digital converter. Either the computer must monitor and control the converter circuit via some input and output lines, or some control logic must ensure that everything happens in the right order. The second method is preferable, since it avoids the need for extra input and output lines. An 8-bit input port is all that is needed.

A conversion is initiated by having the CS (chip select) and WR (write) inputs at logic 0. When not interfacing the chip direct to a microprocessors

bus, it is possible to simplify matters by tying the CS input low and applying the start conversion pulse to the WR input.

The INTR (interrupt) output goes low when the conversion has been completed, but in the present context this is used to indicate to the control logic that fresh data is available. A low pulse on the RD (read) input latches the data onto the data outputs and also resets the INTR output.


At this point, a signal must be supplied to the virtual serial port interface so that it transmits the new byte of data. The computer's hardware and software will then detect and read the new data, thus avoiding the need for monitoring of, or handshaking with, the converter circuit via additional input and output lines.

These two chips will feature in future *Interface* articles, but in the meantime it is a good idea for anyone interested in using them to obtain the relevant data sheets. These are readily available as free downloads on the Internet, and any good search engine should locate a number of sources.

USB DrDAQ®

VERSATILE DATA ACQUISITION

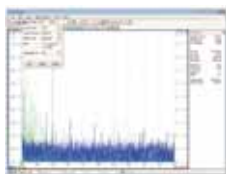- Use DrDAQ as a **Data logger**, an **oscilloscope**, and a **signal generator**
- **Built-in sensors** for light, sound and temperature
- **Measure pH** - just plug in any standard pH electrode
- Sockets for **external sensors**
- **Digital outputs** to control external devices
- **USB** connected and powered
- **Use up to 20 USB DrDAQs** on a single PC




Oscilloscope /
Spectrum Analyzer



Multi-channel
data logger



Arbitrary waveform
generator

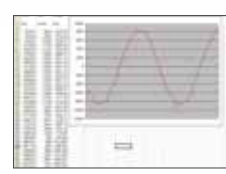

Write your
own software



USB DrDAQ: Making Data Logging Fun!
www.usbdrdaq.com/DD123

pico
Technology

Laser  Why tolerate when you can automate?

X10 Home Automation

KAT5 AV transmission and IR control system

Barix Ethernet based MP3, communications and control systems

www.laser.com

Integrators, Installers, Trade and Retail customers welcome

C-Bus Shop
C-Bus and C-Bus Wireless

www.cbushop.com

Laser Business Systems Ltd
Tel: +44 (0) 20 8441 9788
Fax: +44 (0) 20 8449 0430
Email: info@laser.com
16 Garthland Drive, EN5 3BB

**TO ADVERTISE IN
EVERYDAY PRACTICAL
ELECTRONICS**

PLEASE CONTACT
Stewart Kearn on
01202 880299

or email
stewart.kearn@wimborne.co.uk

e CRICKLEWOOD ELECTRONICS
Established 1981

Frustrated with your supplier?
Visit our component packed website for a vast range of parts - old and new, many unavailable elsewhere!
www.cricklewoodelectronics.com

1000's OF PRICES REDUCED!

Alternatively phone us on 020 8452 0161 with your requirements.

Visit our Shop, Call or Buy online at:
www.cricklewoodelectronics.com
020 8452 0161 Visit our shop at:
40-42 Cricklewood Broadway
London NW2 3ET

SHERWOOD ELECTRONICS

Buy 10 x £1 Special Packs and choose another one FREE

SP1 15 x 5mm Red Leds	SP131 2 x TL071 Op-amps
SP2 12 x 5mm Green Leds	SP132 20 x 1N4004 diodes
SP3 12 x 5mm Yellow Leds	SP133 15 x 1N4007 diodes
SP5 20 x 5mm 1 part Led clips	SP135 5 x Miniature slide switches
SP6 15 x 3mm Red Leds	SP136 3 x BFY50 transistors
SP7 12 x 3mm Green Leds	SP137 4 x W005 1.5A bridge rectifiers
SP8 10 x 3mm Yellow Leds	SP138 20 x 2.263V radial elect caps
SP9 20 x 3mm 1 part Led clips	SP142 2 x Cmos 4017
SP10 100 x 1N4148 diodes	SP143 5 Pairs min. croc.clips (Red+Blk)
SP11 30 x 1N4001 diodes	SP144 5 Pairs min. croc.clips (assorted colours)
SP12 30 x 1N4002 diodes	SP146 10 x 2N3704 transistors
SP16 20 x BC182B transistors	SP151 4 x 8mm Red Leds
SP20 20 x BC184B transistors	SP152 4 x 8mm Green Leds
SP23 20 x BC549B transistors	SP153 4 x 8mm Yellow Leds
SP24 4 x Cmos 4001	SP154 15 x BC548B transistors
SP25 4 x 555 timers	SP160 10 x 2N3904 transistors
SP26 4 x 741 Op-amps	SP161 10 x 2N3906 transistors
SP28 4 x Cmos 4011	SP164 2 x C106D thyristors
SP29 3 x Cmos 4013	SP165 2 x LF351 Op-amps
SP33 4 x Cmos 4081	SP166 20 x 1N4003 diodes
SP34 20 x 1N914 diodes	SP167 5 x BC107 transistors
SP36 25 x 10/25V radial elect caps	SP168 5 x BC108 transistors
SP37 12 x 100/35V radial elect caps	SP172 3 x Standard slide switches
SP38 15 x 47/25V radial elect caps	SP173 10 x 220/25V radial elect caps
SP39 10 x 470/16V radial elect caps	SP174 20 x 22/25V radial elect caps
SP40 15 x BC237 transistors	SP175 20 x 1/63V radial elect caps
SP41 20 x Mixed transistors	SP177 10 x 1A 20mm quick blow fuses
SP42 200 x Mixed 0.25W CF resistors	SP178 10 x 2A 20mm quick blow fuses
SP47 5 x Min. PB switches	SP181 5 x Phono plugs - assorted colours
SP49 4 x 4 metres stranded core wire	SP182 20 x 4.7/63V radial elect caps
SP102 20 x 8 pin DIL sockets	SP183 20 x BC547B transistors
SP103 15 x 14 pin DIL sockets	SP186 6 x 1M horizontal trim pots
SP104 15 x 16 pin DIL sockets	SP189 4 x 4 metres solid core wire
SP109 15 x BC557B transistors	SP192 3 x Cmos 4066
SP112 4 x Cmos 4093	SP195 3 x 10mm Yellow Leds
SP115 3 x 10mm Red Leds	SP197 6 x 20 pin DIL sockets
SP116 3 x 10mm Green Leds	SP198 5 x 24 pin DIL sockets
SP118 2 x Cmos 4047	SP199 4 x 2.5mm mono jack plugs
SP124 20 x Assorted ceramic disc caps	SP200 4 x 2.5mm mono jack sockets
SP130 100 x Mixed 0.5W CF resistors	

RESISTOR PACKS - C.Film

RP3 5 each value - total 365 - 0.25W	£3.55
RP7 10 each value - total 730 - 0.25W	£4.85
RP10 1000 popular values - 0.25W	£6.90
RP4 5 each value - total 305 - 0.5W	£4.45
RP8 10 each value - total 610 - 0.5W	£7.20
RP11 1000 popular values - 0.5W	£9.75

Catalogue available £1 inc. P&P or **FREE** with first order.
P&P £2.25 per order. **NO VAT**
Cheques and Postal Orders to:
Sherwood Electronics,
10 NEWSTEAD STREET,
MANSFIELD, NOTTS.
NG19 6JJ

Technobots
Electronic & Mechanical Components

With over 5,100 products available to order online, Technobots provides one of the widest range of components for the electronics and engineering enthusiast

Opto Electronics

Battery Products
Chargers & PSUs

Passives,
Semiconductors
Sensors
connectors
etc..

Gears, Pulleys
& Cams

Controller Boards
Including Arduino

Breakout Boards
from Sparkfun

Pneumatics

Bearings from 1mm bore

Shafts & Adaptors

Chain & sprockets

Projects & kits

160+ dc motor
motors + speed
controllers

Switches & Relays

Robotics & Wheels

LCD displays

Cable, Fuses & etc..

Tools

Education Accounts
Welcome

Get our 120 page A4 catalogue free with your next order by quoting 'discount coupon code' EPE05 at the checkout

www.technobotsonline.com

Shop callers welcome: Technobots Ltd, 60 Rumbridge Street, Totton, Hampshire SO40 9DS Tel: 023 8086 4891



Max's Cool Beans

By Max The Magnificent

Interesting times

Have you heard the saying 'May you live in interesting times'? I was always under the impression that this was a translation of a Chinese curse (or proverb, depending on your point of view). According to Wikipedia, however, the Chinese language origin of the phrase, if it exists, has not been found. I love Wikipedia; there's always so much to learn. For example, I was interested to discover that the 'interesting times' phrase is actually supposed to be one of three curses of varying severity, the others being 'May you come to the attention of those in authority' and 'May you find what you are looking for.'

Well, earlier this year, I found myself living through some interesting times of my own. As you may or may not recall, I am based in Huntsville, Alabama, USA. I moved here from England twenty-one years ago for the nightlife (that's a little Alabama joke right there [grin]). On Wednesday, 27 April, in addition to torrential rain and raging winds, more than 300 tornadoes ravaged Alabama and nearby states – I've been told that this is the most tornadoes in one day in living memory. Well, a number of these tornadoes ripped through Huntsville and surrounding areas.

It's amazing what one takes for granted in this high-tech world of ours... until things stop working. In addition to numerous power lines coming down, one tornado took out the main towers and power feeds coming out of the local Browns Ferry Nuclear Power Plant. We also lost a lot of wireless towers around the same time. I heard that 600,000+ people ended up without power in north Alabama. No power; no Internet; and virtually no cellphone access – the result was a strange new world.

Tornado warning

I was in my office at work when the first wave of storms hit, mind-locked with my computer and totally unaware of what was going on around me. So it came as something of a surprise when the guy in the office next to mine stuck his head through my door and said: 'There's a tornado headed this way, we're all moving to the safe room downstairs.'

'Oh dear,' I thought (or words to that effect). So I ambled downstairs and was milling around with the other guys when my wife, Gina, called to say that a storm cell had passed right over our house and the power was out and she was not happy. So as soon as we had the all-clear at the office, I leapt into my car and made a break for home. A few miles from my house the gauge on my car started flashing to tell me I was almost out of gas (petrol). 'No worries,' I thought, 'I'll fill her up tomorrow.' Of course, I didn't realise that we were destined to be without power for almost a week and – without power – the gas stations can't pump gas.

Gina and I and our son Joseph and our two stupid cats and our two even more stupid dogs spent the evening camping out on the floor of our laundry room listening to the radio by candlelight. We could hear

the storm raging overhead and feel the house shaking, but we didn't realise just how bad things were out there.

The next morning we discovered that many nearby areas had been totally devastated; for example, if you use Google to look up 'Tornado Anderson Hills Huntsville Alabama' – a subdivision that is located just a few miles from our house – you will be amazed to see just how powerful these storms can be. Our own neighborhood took quite a beating, with lots of trees down and houses missing siding and shingles and suchlike. Much to our amazement, however, our house came through totally unscathed. We were also fortunate in the fact that the main water supply kept working, otherwise we really would have been in dire straits.

We ended up being without power for six long days. Fortunately our families and friends came through this alive, and if this experience has taught me one thing – I will never take the so called small luxuries, hot water, electric lights, TV etc., for granted again!!



Get your magazine 'instantly' anywhere in the world – buy and download from the web.

TAKE A LOOK, A FREE ISSUE IS AVAILABLE

A one year subscription (12 issues) costs just \$19.99(US)



EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS



Flowcode 4 is one of the World's most advanced graphical programming languages for microcontrollers. The great advantage of Flowcode is that it allows those with little experience to create complex electronic systems in minutes.

Flowcode's graphical development interface allows engineers to construct a complete electronic system on-screen, develop a program based on standard flow charts, simulate the system and then produce hex code for PICmicro® microcontrollers, AVR microcontrollers, ARM microcontrollers, dsPIC and PIC24 microcontrollers.



Design

Flowcode contains standard flow chart icons and electronic components that allow you to create a virtual electronic system on screen. Drag icons and components onto the screen to create a program, then click on them to set properties and actions.



Simulate

Once your system is designed you can use Flowcode to simulate it in action. Design your system on screen, test the system's functionality by clicking on switches or altering sensor or input values, and see how your program reacts to the changes in the electronic system.



Download

When you are happy with your design click one button to send the program directly to your microcontroller based target. Targets include a wide range of microcontroller programmers, upstream E-blocks boards, the Formula Flowcode robot, the MIAC industrial controller, or your own system based on ECIO technology.



PRICES

Prices for each of the CD-ROMs above are: *(Order form on third page)*

(UK and EU customers
add VAT to 'plus VAT'
prices)

Hobbyist/Student	£45.95	inc VAT
Professional (Schools/HE/FE/Industry)	£149	plus VAT
Professional and Flowkit bundle	£175	plus VAT



FlowKit

The FlowKit can be connected to hardware systems to provide a real time debug facility where it is possible to step through the Flowcode program on the PC and step through the program in the hardware at the same time. The FlowKit can be connected to your own hardware to provide In-Circuit Debug to your finished designs.

PICmicro TUTORIALS AND PROGRAMMING


HARDWARE

VERSION 3 PICmicro MCU development board

Suitable for use with the three software packages listed below.

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

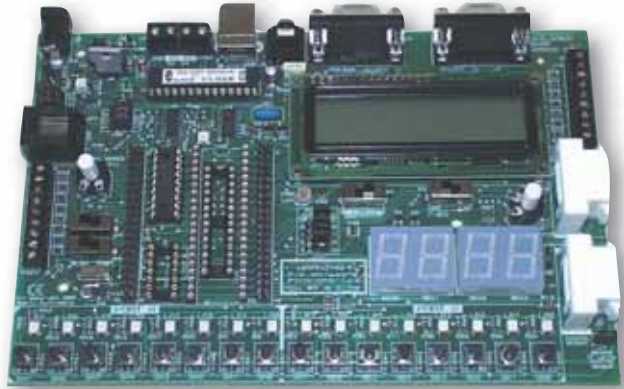- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual LEDs, quad 7-segment display and alphanumeric LCD display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Can be powered by USB (no power supply required)



£161 including VAT and postage, supplied with USB cable and programming software

SOFTWARE

ASSEMBLY FOR PICmicro V3

(Formerly PICTutor)

Assembly for PICmicro microcontrollers V3.0 (previously known as PICTutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes.

The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller, this is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed, which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.



'C' FOR 16 Series PICmicro Version 4

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD-ROM contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.
Flowcode will run on XP or later operating systems

FLOWCODE FOR PICmicro V4

Flowcode is a very high level language programming system based on flowcharts. Flowcode allows you to design and simulate complex systems in a matter of minutes. A powerful language that uses macros to facilitate the control of devices like 7-segment displays, motor controllers and LCDs. The use of macros allows you to control these devices without getting bogged down in understanding the programming. When used in conjunction with the Version 3 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols
- Full on-screen simulation allows debugging and speeds up the development process.
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- 16-bit arithmetic strings and string manipulation
- Pulse width modulation
- I2C.

New features of Version 4 include panel creator, in circuit debug, virtual networks, C code customisation, floating point and new components. The Hobbyist/Student version is limited to 4K of code (8K on 18F devices)



PRICES

Prices for each of the CD-ROMs above are:
(Order form on next page)

(UK and EU customers add VAT to 'plus VAT' prices)

Hobbyist/Student	£45.95	inc VAT
Professional (Schools/HE/FE/Industry)	£99	plus VAT
Professional 10 user (Network Licence)	£350	plus VAT
Site Licence	£699	plus VAT
Flowcode Professional (Schools/HE/FE/Industry)	£149	plus VAT
Flowcode 10 user (Network Licence)	£399	plus VAT
Flowcode Site Licence	£799	plus VAT


CIRCUIT WIZARD

Circuit Wizard is a revolutionary new software system that combines circuit design, PCB design, simulation and CAD/CAM manufacture in one complete package.

Two versions are available, Standard or Professional.

By integrating the entire design process, Circuit Wizard provides you with all the tools necessary to produce an electronics project from start to finish – even including on-screen testing of the PCB prior to construction!

- * Circuit diagram design with component library (500 components Standard, 1500 components Professional)
- * Virtual instruments (4 Standard, 7 Professional)
- * On-screen animation
- * Interactive circuit diagram simulation
- * True analogue/digital simulation
- * Simulation of component destruction
- * PCB Layout
- * Interactive PCB layout simulation
- * Automatic PCB routing
- * Gerber export
- * Multi-level zoom (25% to 1000%)
- * Multiple undo and redo
- * Copy and paste to other software
- * Multiple document support

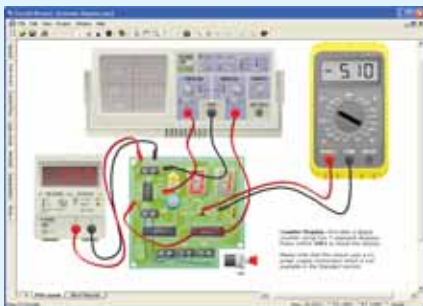


This is the software used in our *Teach-In 2011* series.

Standard £61.25 inc. VAT
Professional £91.90 inc. VAT

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 2000/ME/XP, mouse, sound card, web browser.

EPE PIC RESOURCES V2

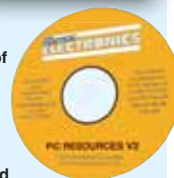Version 2 includes the EPE PIC Tutorial V2 series of Supplements (EPE April, May, June 2003)



The CD-ROM contains the following Tutorial-related software and texts:

- EPE PIC Tutorial V2 complete series of articles plus demonstration software, John Becker, April, May, June '03
- PIC Toolkit Mk3 (TK3 hardware construction details), John Becker, Oct '01
- PIC Toolkit TK3 for Windows (software details), John Becker, Nov '01

Plus 18 useful texts to help YOU get the most out of your PIC programming.

Price £14.75 inc. VAT

ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 jpg images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details).

Now contains Irfan View image software for Windows, with quick-start notes included.

Price £19.95 inc. VAT

Please send me: CD-ROM ORDER FORM



- ☐ Assembly for PICmicro V3
- ☐ 'C' for 16 Series PICmicro V4
- ☐ Flowcode for PICmicro
- ☐ Flowcode for AVR
- ☐ Flowcode for ARM
- ☐ Flowcode for dsPIC & PIC24

Version required:

- ☐ Hobbyist/Student
- ☐ Professional
- ☐ Professional 10 user
- ☐ Professional + Flowkit
- ☐ Site licence

Note: The software on each version is the same, only the licence for use varies.

☐ PICmicro Development Board V3 (hardware)

- ☐ Circuit Wizard – Standard
- ☐ Circuit Wizard – Professional
- ☐ EPE PIC Resources V2
- ☐ Electronic Components Photos

Full name:

Address:

..... Post code: Tel. No:

Signature:

☐ I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

☐ Please charge my Visa/Mastercard/Maestro: £

Valid From: Card expiry date:

Card No: Maestro Issue No.

Card Security Code (The last 3 digits on or just under the signature strip)

ORDERING ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard/Hobbyist Version price includes postage to most countries in the world

EU residents outside the UK add £5 for airmail postage per order

Professional, Multiple User and Site License Versions – overseas readers add £5 to the basic price of each order for airmail postage (**do not add VAT** unless you live in an EU (European Union) country, then add VAT at 20% or provide your official VAT registration number).

Send your order to:
Direct Book Service
Wimborne Publishing Ltd
113 Lynwood Drive, Merley, Wimborne,
Dorset BH21 1UU

To order by phone ring
01202 880299. Fax: 01202 843233

Goods are normally sent within seven days
E-mail: orders@wimborne.co.uk

Online shop:

www.epemag.com



READOUT

Email: editorial@wimborne.co.uk

Matt Pulzer addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

All letters quoted here have previously been replied to directly



WIN AN ATLAS LCR ANALYSER WORTH £79
An Atlas LCR Passive Component Analyser, kindly donated by Peak Electronic Design Ltd, will be awarded to the author of the Letter Of The Month. The Atlas LCR automatically measures inductance from 1mH to 10H, capacitance from 1pF to 10,000µF and resistance from 1Ω to 2MΩ with a basic accuracy of 1%. www.peakelec.co.uk

★ LETTER OF THE MONTH ★

Lightning speed is not what you want!

Dear Editor

I've been running Ethernet cable around the house to couple three computers and a media player, a laptop is also connected via WiFi. Fortunately, I hadn't finished and only one computer was connected because there was a particularly violent thunderstorm during the early hours of one morning. When I switched on the computer I was greeted with a black screen and error messages about a non-standard PCI bus.

I couldn't get past the errors, nor could I access the BIOS. Some time later, I had the computer up and running, however, the on-board Ethernet controller was fried, likewise the modem and the WiFi router. Everything had switched off at the mains, the only connection was via a phone line and Ethernet cable between the computer, modem and router.

It seems likely that a lightening strike, either on or near the overhead phone line caused a surge, which passed through my equipment, destroying everything in its path. I'm connected via WiFi at the moment, I don't get a very good signal, the walls of my house are stone and up to two-feet thick in places, the signal also is much

lower when it's raining – I suspect humidity must be having some effect here – but I think I'll stick to WiFi for the time being.

I also had an external USB hard drive connected to the media player so that I could watch video files, but the Viewsonic media player has just croaked on me. It is under guarantee and it failed some weeks after the lightening strike, so I don't think the two are connected.

One final, but unrelated point – in *Net Work*, Alan Winstanley states that all devices have to share the same phase, the attached pdf [supplied to AW] shows that signals can be copied across phases. Not sure if I'd want to be faffing about with three phase, but at least it's possible, in theory.

Alan Jones, by email

Alan Winstanley replies:

Very interesting comments, thank you. I do sympathise and, although yours is quite an extreme example, I can believe how a lightning-induced surge could be transmitted over the phone lines and through a router, taking out any network equipment connected at the same time.

With Internet-connected large-screen TVs and media network players finding

their way onto home networks, I think the risk of key equipment suffering substantial lightning damage is becoming a real one. As a habit, I try to disconnect everything from my phone lines whenever a major thunderstorm is passing close by.

My desktop PCs have uninterruptible power supplies and sensitive mains equipment is connected through surge-suppressed mains adaptors to offer a modicum of protection. Some suppressed powerstrips have AV or phone line protection too, along with insurance policies to cover the cost of any damage caused to connected equipment. Short of unplugging everything and crossing your fingers, there isn't a lot more that you can do to guard against lightning damage.

You could consider wireless repeater units (aka range extenders) to extend your WiFi coverage through the building. Amazon lists quite a few. TP Link models have been recommended to me.

I had excellent service from Viewsonic when my monitor failed, they have been very good and replaced it without question. I've had two or three Viewsonics and I can generally recommend them.

Thanks for your interest, regards

Alan Winstanley

Cool Beans and Spirules

Dear Editor

A big 'thank you' to Max for pointing out the full potential of Dropbox. It is a utility I've been using for some time, but had singularly failed to spot its potential to create copies and file share across multiple desktops and even my Xperia X10 mobile.

May I also thank you for the current *Teach-In 2011* series, which has provided a useful re-introduction to the world of discrete electronics. I speak as a control engineering graduate from the class of '78, at Sheffield Polytechnic – yes, 1978! Think about it, no PCs, no mobile phones, DEC PDP-8 minicomputers with paper tape and punched cards and only the very earliest microprocessors to play with.

Anyway, the recent rediscovery of your magazine has been a welcome distraction in my world, which these days, is otherwise devoid of anything remotely electronic.

Will you be taking the *Teach-In* series in the direction of control theory and Laplace transforms? (Hmm, perhaps not!)

Keep up the good work!

PS Do you know anyone who wants to buy a second-hand Spirule?

Chris Hodgson, Rochester

I'm pleased to hear that EPE in general and Teach-In in particular has restored and maintained your interest in electronics. I too was a control engineering student, but of a slightly later vintage – mid 80s. However, I do have a Spirule, although I never got to use it that much.

For younger readers and those not familiar with control theory, a spirule was a clever mechanical device for adding angles (and other calculations) which are useful when designing feedback systems – especially if you don't have access to a computer with

relevant software. An interesting history of this device is available at: www.spirule.com/BirthofSpiruleCompany.pdf

Simple Voltage Switch For Car Sensors

Dear Editor

I have just completed building John Clarke's *Simple Voltage Switch For Car Sensors* constructional project (EPE, May 2011). (Incidentally, I sourced the components for this project as a kit.)

The finished project works well and is very pleasing. However, I have found that it has one minor shortcoming. There is very little switch-off hysteresis available at low trigger voltages in the L/H trigger mode.

This project has lots of applications in cars, but also has the capability of being utilised in any application where 12V DC

is available. Consider an application where the unit is to be triggered, by a slowly varying input voltage, at a relatively low signal level of 0.6V. As a result of the voltage divider acting at the signal input, the trigger voltage in this situation, as set by VR1, is required to be as low as 0.3V.

On inspection of the circuit diagram it can be seen that, (with VR1 set to 0.3V, VR2 wound so that it has zero effective resistance and op-amp, IC1a triggered with its output saturated close to the zero volts supply rail), the voltage dropped across D3, a standard 1N4148 signal diode, is so low that the current conduction through D3 and the 10k resistor is insufficient to produce a significant amount of hysteresis. In fact, in this situation when I measured the non-inverting input (Pin 3) of IC1a I found that it had been pulled lower by only about 10mV. That is to say only about 10mV of hysteresis had been produced. This makes things quite critical.

To alleviate this problem, I modified the circuit by replacing D3 with a Schottky diode which, with its low forward current present in this circuit setup, has a lower nominal forward voltage drop of only 0.15V. As a result of this diode substitution, I found that, with 0.3V still set on VR1, the maximum available hysteresis had increased to about 125mV, thus improving circuit operation by reducing the likelihood of relay chatter at a lower trigger level when a slowly varying input signal is present.

Consider just one more measurement example. For an input signal trigger threshold of 1.0V, (ie, 0.5V set as the trigger level on VR1) I measured a maximum of approximately 95mV of hysteresis available with the specified 1N4148 diode installed, whereas with the replacement Schottky diode, the maximum available hysteresis increases to about 285mV.

I would be interested to hear what John Clarke's thoughts are on this minor modification to his circuit design.

While I am putting pen to paper (or fingers to keyboard!), I would just like to mention that I have been aware of some light controversy in the past on *Chat Zone* concerning *EPE*'s policy of publishing constructional projects which have previously been published in *Silicon Chip*. I would like to voice my support and encouragement for the staff at *EPE* in continuing with this policy, as I find these projects to be of an extremely high calibre and contribute much value to our quality magazine. Like many other electronics enthusiasts, I have learned a great deal over the years from *Silicon Chip* contributors such as John Clarke, Jim Rowe and Mauro Grassi, and I hope that their continued input will enable us to carry on learning from them in the future. Keep up the good work at *EPE*!

Chris Hinchcliffe, Dorset

It is always worth considering the Schottky diode and its lower voltage drop. As Chris points out, it can be especially useful in low voltage measurement and measurement applications.

I'm delighted you support our policy of using Silicon Chip material – you are correct, the projects they produce are of a very high quality.

EPE June 2011: Motor Speed Controller – errors

Dear Editor

Is there an error in the value of one of the resistors in the motor speed controller current monitoring? The text says there are two 10k resistors to drop the 1.2V ($48A \times 0.025\Omega$) down to 0.6V into the base of transistor Q4. This makes sense. But Fig.9, Fig.10 and the parts list all indicate a 100k Ω resistor between the base of Q4 and 0V. This would mean that the limit would (theoretically) be in excess of 500A, so unlikely to ever operate!

Dave Reeves, by email

John Clarke replies:

The 100k Ω resistor from base to 0V for Q4 is correct. The use of 10k Ω was from an earlier version of this project and we neglected to change that part of the text. The text should be revised to reflect the change from a 10k Ω resistor to a 100k Ω resistor.

The resistance change reduces the voltage divider effect from 0.5 for a 10k Ω resistor to 0.91 when a 100k Ω resistance is used. This divider works in conjunction with a 10k Ω resistor connecting Q4's base to the current sense resistance.

Voltage from the current sense resistance is therefore reduced by the 0.91. (calculated as 100k Ω divided by (100k Ω plus 10k Ω)) at Q4's base. Current limit will therefore occur at 26.4A when there is 0.66V across the 0.025 Ω current sense resistance. The 0.66V is divided down by 0.91 to deliver 0.6V at Q4's base.

The relevant paragraph in the article should have read as follows:

Current monitoring

R1 is a used to monitor the current flow through the motor and IGBT (Q1). Transistor Q4 directly monitors the current via a voltage divider comprising 10k Ω and 100k Ω resistors. At about 26.4A, there is 0.66V across R1 and the resistive divider reduces this to 0.6V at Q4's base. The transistor conducts and shuts down the PWM comparator (IC1b) to disconnect drive to the IGBT. Thus, Q4 provides for transient current limiting.

John Clarke

Quack quack!

Dear Editor

Bella, aged three, was given a small plastic duck for her birthday. Every time she shakes it, the whole duck lights up and flashes red and white for three seconds. (Bella's great-grandmother bought the small plastic duck for 85p from The Toy Box, Wharf St, Godalming – www.thetoyboxgodalming.co.uk)

No prizes for guessing that inside the duck are two LEDs. Intrigued to find out exactly how it worked, I obtained a duck for myself – well, two actually, one to dissect and one to play with.

Inside there is a transparent plastic sphere of diameter 25mm. And inside the sphere is a small piece of PCB holding a stack of three watch batteries (giving 4V), two LEDs and a blob of material encasing what must be a timer.

A little spiral spring slants up from the PCB. When the duck is shaken, the spring flexes, its tip touches the PCB and sets the LEDs flashing.

Bella loves it, banging her duck down on the table to make it light up. There were no toys like this when I was aged three.

Murray Ward, by email

Interesting! Thank you for that explanation, and I'm pleased to hear Bella's duck was not sacrificed in your experiments.



**IF YOU HAVE A SUBJECT YOU WISH TO DISCUSS IN READOUT
PLEASE EMAIL US AT:**

editorial@wimborne.co.uk



Net Work

Alan Winstanley



TODAY, the mobile phone is the focus of all that's new in convergent internet-based technologies. Over the years it's been hard not to notice the inexorable slide towards mobile communications – gone are the days of being tethered to a laptop or PC for email and web.

Facebook made content management easy and eliminated the problems of managing a personal website. It was soon to be at the heart of social networking. A colleague uploaded onto Facebook photos and video clips of his holiday in Vietnam the day they were taken. Many such applications can be handled on a mobile phone.

Google's free Gmail was another revelation, offering convenience and so much disk space as to make the problem of archiving email forgettable. Google also offers simple template-driven websites (<http://sites.google.com>) which might suit families, local groups or clubs and could be used for company Intranets.

Mobile content is king

Still on a mobile theme, YouTube allows users to upload their own video clips and it contains many gems if you care to spend time searching (eg, an *EPE Chat Zone* user pointed to some fascinating footage on how Mullard valves – vacuum tubes – were made.) Old music videos, techie films, vintage TV ads and more are all there, and can be viewed on a suitably equipped mobile by going to <http://m.youtube.com>.

For many, turning to a mobile phone for answers is a complete no-brainer. Simply Google or Bing for something on a phone (eg, 'liquid smoke' food flavouring, which I googled discretely during a BBQ: I then skipped the burgers!) and you'll get links galore, with map location details, directions, local reviews, photos and more: any amount of information all dished up on a plate. Link it to GPS and a built-in digital camera and you need never be lost again. Sending a 'Tweet' or updating Facebook while on the move are easier than ever thanks to a plethora of mobile apps. for iPhones, Windows Smartphones and Android-based mobiles.

Earlier this year, Nokia decided to align with Windows Mobile, bringing Microsoft's Bing search and Nokia Maps to the Nokia mobile. Google is also experimenting with allied technologies, including postal address and voice recognition. A comprehensive and never-ending listing of Google's various enterprises is at http://en.wikipedia.org/wiki/List_of_Google_products. Always-on mobile video communications only lack the network coverage and bandwidth at the moment, and the time will come when a camera-phone automatically recognises its owner using face and voice recognition. As Google said

about its Calendar scheduler events service, 'All this for free? Yep.'

2D or not 2D

We're all familiar with striped barcodes found on almost every consumer product. An optical scanner reads the stripe's reflections to decode its product code, and then a look-up table is checked to find the price and description. Simple EAN barcodes only contain details of the manufacturer, their product code and a check digit, nothing else. In the UK, product barcodes are controlled by GS1 (www.gs1uk.org).

Increasingly, we're seeing graphics containing square black pixels on a grid – maybe on a poster or in an advertisement. They are the next generation barcode that can be scanned by a suitably-equipped mobile phone.

Known as 2D or QR/Quick Response codes, instead of simple stripes that are read forwards or backwards, 2D hold a two-dimensional grid of pixels, offering many more permutations. You can have great fun with them, as they can encode all sorts of data, from plain text to website addresses, SMS text – almost anything. Suddenly, you have a whole new way of exchanging simple information – perfect for 2D-equipped mobile phones. Take a look at www.qrstuff.com to create your own 2D barcodes that can be emailed or printed out. You can also print them onto sheets of labels.

You'll have to search around for decent software for your phone – some are listed at <http://tinyurl.com/byk4wg>. These are untested by the writer and registration may be required, and you will undoubtedly have to experiment to find a product that's right for your compatible phone. Quickmark offers a highly effective 2D reader for PC users which has screen capture or drag and drop, or use your webcam as a QR code reader. Register and download a version free for personal use from www.quickmark.com.tw.

Mobile phones have more interesting things up their sleeve: using them for micro-payments such as car parking or vending machines is not a new concept, though it's a long time coming to the West. Near Field Communications (NFC) is a Bluetooth-like short distance RF system that will let customers 'pay' for an item or a ticket with the wave of a mobile phone. Devices from Samsung and Nokia promise to bring us this cashless technology, and gone will be the days of feeding coins into a ticket machine. That's the great thing about electronics – there's always something new coming around the corner.

You can email me at: alan@epemag.demon.co.uk or write to the Editor for possible publication in *Readout* at editorial@wimborne.co.uk.



QRStuff is a great online resource to help produce barcodes

DIRECT BOOK SERVICE

NEW

Electronics Teach-In 3

The three sections of this book cover a very wide range of subjects that will interest everyone involved in electronics, from hobbyists and students to professionals. The first 80-odd pages of Teach-In 3 are dedicated to *Circuit Surgery*, the regular *EPE* clinic dealing with readers' queries on various circuit design and application problems – everything from voltage regulation to using SPICE circuit simulation software.

The second section – *Practically Speaking* – covers the practical aspects of electronics construction. Again, a whole range of subjects, from soldering to avoiding problems with static electricity and identifying components, are covered.

Finally, our collection of *Ingenuity Unlimited* circuits provides over 40 different circuit designs submitted by the readers of *EPE*.

The free cover-mounted CD-ROM is the complete *Electronics Teach-In 1* book, which provides a broad-based introduction to electronics in PDF form, plus interactive quizzes to test your knowledge, TINA circuit simulation software (a limited version – plus a specially written TINA Tutorial), together with simulations of the circuits in the Teach-In 1 series, plus Flowcode (a limited version) a high level programming system for PIC microcontrollers based on flowcharts.

The Teach-In 1 series covers everything from Electric Current through to Microprocessors and Microcontrollers and each part includes demonstration circuits to build on breadboards or to simulate on your PC. There is also a MW/LW Radio project in the series.

The contents of the book and Free CD-ROM have been reprinted from past issues of *EPE*.

CD-ROM Order code ET13 £8.50

FREE
CD-ROM

CIRCUITS AND DESIGN

A BEGINNER'S GUIDE TO TTL DIGITAL ICs R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the 'real world'.

142 pages Order code BP332 £5.45

PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M. Bridges the gap between complicated technical theory, and 'cut-and-try' methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias – tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-Current Circuits, Passive Components, Alternating-Current Circuits, Networks and Theorems, Measurements.

256 pages Order code BP53 £5.49

MICROCONTROLLER COOKBOOK Mike James

The practical solutions to real problems shown in this cookbook provide the basis to make PIC and 8051 devices really work. Capabilities of the variants are examined, and ways to enhance these are shown. A survey of common interface devices, and a description of programming models, lead on to a section on development techniques. The cookbook offers an introduction that will allow any user, novice or experienced, to make the most of microcontrollers.

240 pages Order code NE26 £36.99

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER SELECTION
OF BOOKS AND CDROMS
SEE THE UK SHOP ON OUR
WEBSITE

www.epemag.com

All prices include UK
postage

2

COMPUTING AND ROBOTICS

WINDOWS XP EXPLAINED N. Kantaris and P. R. M. Oliver

If you want to know what to do next when confronted with Microsoft's Windows XP screen, then this book is for you. It applies to both the Professional and home editions.

The book was written with the non-expert, busy person in mind. It explains what hardware requirements you need in order to run Windows XP successfully, and gives an overview of the Windows XP environment.

The book explains: How to manipulate Windows, and how to use the Control Panel to add or change your printer, and control your display; How to control information using WordPad, notepad and paint, and how to use the Clipboard facility to transfer information between Windows applications; How to be in control of your filing system using Windows Explorer and My Computer; How to control printers, fonts, characters, multimedia and images, and how to add hardware and software to your system; How to configure your system to communicate with the outside world, and use Outlook Express for all your email requirements; how to use the Windows Media Player 8 to play your CDs, burn CDs with your favourite tracks, use the Radio Tuner, transfer your videos to your PC, and how to use the Sound Recorder and Movie Maker; How to use the System Tools to restore your system to a previously working state, using Microsoft's Website to update your Windows set-up, how to clean up, defragment and scan your hard disk, and how to backup and restore your data; How to successfully transfer text from those old but cherished MS-DOS programs.

264 pages Order code BP514 £7.99

INTRODUCING ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various 'click-together' components supplied in the basic RIS kit. Explains in simple terms how the 'brain' of the robot may be programmed on screen using a PC and 'zapped' to the robot over an infrared link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages + Large Format Order code BP901 £14.99

MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS – Robert Penfold

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands, perform tricks, 'see' and

avoid objects by using 'bats radar', or accurately follow a line marked on the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.COX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an 'intelligent' sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

298 pages Order code BP902 £14.99

THE PIC MICROCONTROLLER YOUR PERSONAL INTRODUCTORY COURSE – THIRD EDITION John Morton

Discover the potential of the PIC microcontroller through graded projects – this book could revolutionise your electronics construction work!

A uniquely concise and practical guide to getting up and running with the PIC Microcontroller. The PIC is one of the most popular of the microcontrollers that are transforming electronic project work and product design.

Assuming no prior knowledge of microcontrollers and introducing the PICs capabilities through simple projects, this book is ideal for use in schools and colleges. It is the ideal introduction for students, teachers, technicians and electronics enthusiasts. The step-by-step explanations make it ideal for self-study too; this is not a reference book – you start work with the PIC straight away.

The revised third edition covers the popular reprogrammable Flash PICs: 16F54/16F84 as well as the 12F508 and 12F675.

270 pages Order code NE36 £25.00

INTRODUCTION TO MICROPROCESSORS AND MICROCONTROLLERS – SECOND EDITION John Crisp

If you are, or soon will be, involved in the use of microprocessors and microcontrollers, this practical introduction is essential reading. This book provides a thoroughly readable introduction to microprocessors and microcontrollers. Assuming no previous knowledge of the subject, nor a technical or mathematical background. It is suitable for students, technicians, engineers and hobbyists, and covers the full range of modern micros.

After a thorough introduction to the subject, ideas are developed progressively in a well-structured format. All technical terms are carefully introduced and subjects which have proved difficult, for example 2's complement, are clearly explained. John Crisp covers the complete range of microprocessors from the popular 4-bit and 8-bit designs to today's super-fast 32-bit and 64-bit versions that power PCs and engine management systems etc.

222 pages Order code NE31 £29.99

EASY PC CASE MODDING R.A. Penfold

Why not turn that anonymous grey tower, that is the heart of your computer system, into a source of visual wonderment and fascination. To start, you need to change the case or some case panels for ones that are transparent. This will then allow the inside of your computer and it's working parts to be clearly visible.

There are now numerous accessories that are relatively inexpensive and freely available, for those wishing to customise their PC with added colour and light. Cables and fans can be made to glow, interior lights can be added, and it can all be seen to good effect through the transparent case. Exterior lighting and many other attractive accessories may also be fitted.

This, in essence, is case modding or PC Customising as it is sometimes called and this book provides all the practical details you need for using the main types of case modding components including: Electro luminescent (EL) 'go-faster' stripes; Internal lighting units; Fancy EL panels; Data cables with built-in lighting; Data cables that glow with the aid of 'black' light from an ultraviolet (UV) tube; Digital display panels; LED case and heatsink fans; Coloured power supply covers.

192 pages + CD-ROM Order code BP542 £8.99

ROBOT BUILDERS COOKBOOK Owen Bishop

This is a project book and guide for anyone who wants to build and design robots that work first time.

With this book you can get up and running quickly, building fun and intriguing robots from step-by-step instructions. Through hands-on project work, Owen introduces the programming, electronics and mechanics involved in practical robot design-and-build. The use of the PIC microcontroller throughout provides a painless introduction to programming – harnessing the power of a highly popular microcontroller used by students, hobbyists and design engineers worldwide.

Ideal for first-time robot builders, advanced builders wanting to know more about programming robots, and students tackling microcontroller-based practical work and labs.

The book's companion website at <http://books.elsevier.com/companions/9780750665568> contains: downloadable files of all the programs and subroutines; program listings for the Quester and the Gantry robots that are too long to be included in the book.

366 pages Order code NE46 £26.00

NEWNES INTERFACING COMPANION Tony Fischer-Cripps

A uniquely concise and practical guide to the hardware, applications and design issues involved in computer interfacing and the use of transducers and instrumentation. Newnes Interfacing Companion presents the essential information needed to design a PC-based interfacing system from the selection of suitable transducers, to collection of data, and the appropriate signal processing and conditioning.

Contents: Part 1 – Transducers; Measurement systems; Temperature; Light; Position and motion; Force, pressure and flow. Part 2 – Interfacing; Number systems; Computer architecture; Assembly language; Interfacing; A to D and D to A conversions; Data communications; Programmable logic controllers; Data acquisition project. Part 3 – Signal processing; Transfer function; Active filters; Instrumentation amplifier; Noise; Digital signal processing.

295 pages Order code NE38 £41.00

THEORY AND REFERENCE

THE AMATEUR SCIENTIST CD-ROM

The complete collection of The Amateur Scientist articles from Scientific American magazine. Over 1,000 classic science projects from a renowned source of winning projects. All projects are rated for cost, difficulty and possible hazards. Plus over 1,000 pages of helpful science techniques that never appeared in Scientific American.

Exciting science projects in: Astronomy; Earth Science; Biology; Physics; Chemistry; Weather . . . and much more! The most complete resource ever assembled for hobbyists, and professionals looking for novel solutions to research problems.

Suitable for Mac, Windows, Linux or UNIX. 32MB RAM minimum, Netscape 4.0 or higher or Internet Explorer 4.0 or higher.

Over 1,000 projects

Order code AS1 CD-ROM £19.95



UNDERSTANDING ELECTRONIC CONTROL SYSTEMS

Owen Bishop

Owen Bishop has produced a concise, readable text to introduce a wide range of students, technicians and professionals to an important area of electronics. Control is a highly mathematical subject, but here maths is kept to a minimum, with flow charts to illustrate principles and techniques instead of equations.

Cutting edge topics such as microcontrollers, neural networks and fuzzy control are all here, making this an ideal refresher course for those working in industry. Basic principles, control algorithms and hardwired control systems are also fully covered so the resulting book is a comprehensive text and well suited to college courses or background reading for university students.

The text is supported by questions under the headings Keeping Up and Test Your Knowledge so that the reader can develop a sound understanding and the ability to apply the techniques they are learning.

228 pages

Order code NE35 £36.99

OSCILLOSCOPES - FIFTH EDITION

Ian Hickman

Oscilloscopes are essential tools for checking circuit operation and diagnosing faults, and an enormous range of models are available.

This handy guide to oscilloscopes is essential reading for anyone who has to use a 'scope for their work or hobby; electronics designers, technicians, anyone in industry involved in test and measurement, electronics enthusiasts . . . Ian Hickman's review of all the latest types of 'scope currently available will prove especially useful for anyone planning to buy - or even build - an oscilloscope.

The contents include a description of the basic oscilloscope; Advanced real-time oscilloscope; Accessories; Using oscilloscopes; Sampling oscilloscopes; Digital storage oscilloscopes; Oscilloscopes for special purposes; How oscilloscopes work (1): the CRT; How oscilloscopes work (2): circuitry; How oscilloscopes work (3): storage CRTs; plus a listing of Oscilloscope manufacturers and suppliers.

288 pages

Order code NE37 £36.99

**ALL PRICES INCLUDE
UK POST & PACKING**

**FOR MORE BOOKS VISIT
WWW.EPEMAG.COM**

FULL COLOUR COMPUTING BOOKS

HOW TO FIX YOUR PC PROBLEMS

R.A. Penfold

What do you do when your laptop or desktop stops working properly. Do you panic, try to find the answer on the page of fault finding tips you may find at the back of the manufacturers manual. Or do you spend hours trying to get through to a telephone helpline or waste even more time waiting for an email reply from a helpdesk.

Well help is now at hand! This book will assist you in identifying the type of problem, whether it's hardware, software or a peripheral that is playing up? Once the fault has been identified, the book will then show you how to go about fixing it. This book uses plain English and avoids technical jargon wherever possible. It is also written in a practical and friendly manner and is logically arranged for easy reference.

The book is divided into four main sections and among the many topics covered are: Common problems with Windows Vista operating system not covered in other chapters. Also covers to a lesser extent Windows XP problems. Sorting out problems with ports, peripherals and leads. Also covers device drivers software and using monitoring software. Common problems with hard disc drives including partitioning and formatting a new drive. Using system restore and recovering files. Also covers CD-ROM and Flash drives. Common problems with sound and video, including getting a multi-speaker system set up correctly.

An extremely useful addition to the library of all computer users, as you never know when a fault may occur!

Printed in full colour on high quality non-reflective paper

128 pages

Order code BP705 £8.49

AN INTRODUCTION TO WINDOWS VISTA

P.R.M. Oliver and N. Kantarris

If you have recently bought a new desktop or laptop it will almost certainly have Windows as its operating system. Windows Vista manages the available resource of a computer and also 'controls' the programs that run on it.

To get the most from your computer, it is important that you have a good understanding of Vista. This book will help you achieve just that. It is written in a friendly and practical way and is suitable for all age groups from youngsters to the older generation. It has been assumed that Vista is installed and running on your computer.

Among the numerous topics explained are: The Vista environment with its many windows. How to organise your files, folders and photos. How to use Internet Explorer for your web browsing. How to use Microsoft Mail for your emails. How to control your PC and keep it healthy. How to use Vista's Accessibility features if you have poor eye sight or difficulty in using the keyboard or mouse. And much more besides...

With the help of this book you will easily and enjoyably gain a better understanding of Microsoft's amazing Windows Vista operating system.

Printed in full colour on high quality non-reflective paper

120 pages

Order code BP703 £8.49

COMPUTING WITH A LAPTOP FOR THE OLDER GENERATION

R.A. Penfold

Laptop computers have rapidly fallen in price, increased in specification and performance and become much lighter in weight. They can be used practically anywhere, then stored away out of sight. It is therefore, not surprising that laptop sales now far exceed those of desktop machines and that they are increasingly becoming the machine of choice for the older generation.

You may want to use your laptop as your main computer or as an extra machine. You may want to use your laptop on the move, at home, at work or on holiday. Whatever your specific requirements are, the friendly and practical approach of this book will help you to understand and get

the most from your laptop PC in an easy and enjoyable way. It is written in plain English and wherever possible avoids technical jargon.

Among the many topics covered are: Choosing a laptop that suits your particular needs. Getting your new computer set up properly. Customising your computer so that it is optimised for your particular needs. Setting up and dealing with user accounts. Using the Windows 'Ease of Access Center'. Optimising the life and condition of your battery. Keeping the operating system and other software fully up-to-date. Troubleshooting common problems. Keeping your computer and data safe and secure. And much more besides...

Even though this book is written for the older generation, it is also suitable for anyone of any age who has a laptop or is thinking of buying one. It is written for computers that use Windows Vista as their operating system but much will still apply to Windows XP machines. Printed in full colour on high quality non-reflective paper

120 pages

Order code BP702

£8.49

AN INTRODUCTION TO EXCEL SPREADSHEETS

Jim Gatenby

The practical and friendly approach of this book will help newcomers to easily learn and understand the basics of spreadsheets. This book is based on Microsoft's Excel 2007 spreadsheet, but much of the book will still apply to earlier versions of Excel. The book is written in plain English, avoiding technical and mathematical jargon and all illustrations are in full colour. It is suitable for all age groups from youngsters to the older generation.

Among the many topics explained are how to: Install the software. Use the exciting new features of Excel 2007. Create and use a spreadsheet. Enter, edit and format text, numbers and formulae. Insert and delete columns and rows. Save and print a spreadsheet. Present the information on a spreadsheet as a graph or chart. Manage and safeguard Excel files on disc. Use Excel as a simple database for names and addresses.

This book will help you to quickly gain confidence and get to grips with using spreadsheets. In fact, you will wonder how you ever managed without them.

Printed in full colour on high quality non-reflective paper.

118 pages

Order code BP701

£8.49

AN INTRODUCTION TO DIGITAL PHOTOGRAPHY WITH VISTA

R.A. Penfold

The friendly and practical approach of this book will help newcomers to digital photography and computing to easily learn the basics they will need when using a digital camera with a laptop or desktop PC. It is assumed that your PC uses Windows Vista, however, if it is a Windows XP machine the vast majority of this book will still apply. The book is written in plain English, avoiding technical jargon and all illustrations are in full colour. It is suitable for all age groups from youngsters to the older generation.

Among the many topics explained are how to: Understand the basic features of a digital camera. Transfer photographs from your digital camera to your computer. View your photographs. Save, sort and file your photographs. Manipulate, crop and carry out simple corrections to your photographs. Copy your photographs on to CD or DVD. Print your photographs. Share images with family and friends anywhere in the world by email or with an online album.

This book will help you quickly get to grips with, gain confidence and expand your horizons in the fascinating hobby of digital photography.

Printed in full colour on high quality non-reflective paper.

120 pages

Order code BP700

£8.49



PROJECT BUILDING

ELECTRONIC PROJECTS FOR EXPERIMENTERS

R. A. Penfold

Many electronic hobbyists who have been pursuing their hobby for a number of years seem to suffer from the dreaded "seen it all before" syndrome. This book is fairly and squarely aimed at sufferers of this complaint, plus any other electronics enthusiasts who yearn to try something a bit different.

The subjects covered include:- Magnetic field detector, Basic Hall effect compass, Hall effect audio isolator, Voice scrambler/descrambler, Bat detector, Bat style echo location, Noise cancelling, LED stroboscope, Infra-red "torch", Electronic breeze detector, Class D power amplifier, Strain gauge amplifier, Super hearing aid.

Temporarily out of print

BUILDING VALVE AMPLIFIERS

Morgan Jones

The practical guide to building, modifying, fault-finding and repairing valve amplifiers. A hands-on approach to valve electronics – classic and modern – with a minimum of theory. Planning, fault-finding, and testing are each illustrated by step-by-step examples.

A unique hands-on guide for anyone working with valve (tube in USA) audio equipment – as an electronics experimenter, audiophile or audio engineer.

Particular attention has been paid to answering questions commonly asked by newcomers to the world of the vacuum tube, whether audio enthusiasts tackling their first build, or more experienced amplifier designers seeking to learn the ropes of working with valves. The practical side of this book is reinforced by numerous clear illustrations throughout.

368 pages

Order code NE40 £29.00

THEORY AND REFERENCE

GETTING THE MOST FROM YOUR MULTIMETER


R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages

Order code BP239 £5.49

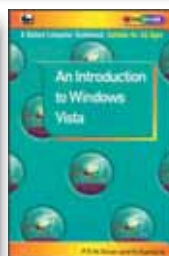

PRACTICAL FIBRE-OPTIC PROJECTS

R. A. Penfold

While fibre-optic cables may have potential advantages over ordinary electric cables, for the electronics enthusiast it is probably their novelty value that makes them worthy of exploration. Fibre-optic cables provide an innovative interesting alternative to electric cables, but in most cases they also represent a practical approach to the problem. This book provides a number of tried and tested circuits for projects that utilize fibre-optic cables.

The projects include:- Simple audio links, F.M. audio link, P.W.M. audio links, Simple d.c. links, P.W.M. d.c. link, P.W.M. motor speed control, RS232C data links, MIDI link, Loop alarms, R.P.M. meter.

All the components used in these designs are readily available, none of them require the constructor to take out a second mortgage.

132 pages

Order code BP374 £5.45

HOW TO BUILD A COMPUTER

R. A. Penfold

To build your own computer is, actually, quite easy and does not require any special tools or skills. In fact, all that it requires is a screwdriver, pliers and some small spanners rather than a soldering iron! The parts required to build a computer are freely available and relatively inexpensive.

Obviously, a little technical knowledge is needed in order to buy the most suitable components, to connect everything together correctly and to set up the finished PC ready for use. This book will take you step-by-step through all the necessary procedures and is written in an easy to understand way. The latest hardware components are covered as is installing the Windows Vista operating system and troubleshooting.

320 pages

Order code BP591 £8.99

VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard. There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

Temporarily out of print

BOOK ORDERING DETAILS

All prices include UK postage, for postage to Europe (air) and the rest of the world (surface) please add £2 per book. For the rest of the world airmail add £3 per book. **Note: Overseas surface mail postage can take up to 10 weeks.** CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard or Maestro to:


DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LIMITED, 113 LYNWOOD DRIVE, MERLEY, WIMBORNE, DORSET, BH21 1UU.

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery – more for overseas orders. Please check price and availability (see latest issue of *Everyday Practical Electronics*) before ordering from old lists.

For a further selection of books see the next two issues of *EPE*.

Tel 01202 880299 Fax 01202 843233. Email: dbs@wimborne.co.uk

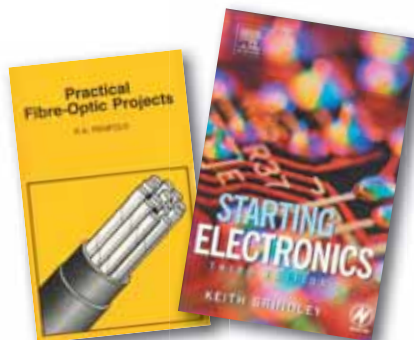Order from our online shop at: www.epemag.com. Go to the 'UK store'.



STARTING ELECTRONICS

Third Edition

Keith Brindley

A punchy practical introduction to self-build electronics. The ideal starting point for home experimenters, technicians and students who want to develop the real hands-on skills of electronics construction.

A highly practical introduction for hobbyists, students, and technicians. Keith Brindley introduces readers to the functions of the main component types, their uses, and the basic principles of building and designing electronic circuits.

Breadboard layouts make this very much a ready-to-run book for the experimenter, and the use of multimeter, but not oscilloscopes, and readily available, inexpensive components makes the practical work achievable in a home or school setting as well as a fully equipped lab.

288 pages

Order code NE42 £15.99

BOOK ORDER FORM

Full name:

Address:

.....

.....

..... Post code: Telephone No:

Signature:

☐ I enclose cheque/PO payable to DIRECT BOOK SERVICE for £

☐ Please charge my card £ Card expiry date:

Card Number Maestro Issue No.

Card Security Code Card valid from date

(the last three digits on or just below the signature strip)

Please send book order codes:

.....

Please continue on separate sheet of paper if necessary

PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the *PCB Service*, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. Double-sided boards are **NOT plated through hole** and will require 'vias' and some components soldering to both sides. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU. Tel: 01202 880299; Fax 01202 843233; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.com.** Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail. Back numbers or photocopies of articles are available if required – see the Back Issues page for details. WE DO NOT SUPPLY KITS OR COMPONENTS FOR OUR PROJECTS.

Please check price and availability in the latest issue.
A large number of older boards are listed on, and can be ordered from, our website.

Boards can only be supplied on a payment with order basis.

PROJECT TITLE	ORDER CODE	COST
JULY '10		
★ ColdAlert Hypothermia Alarm	761	£7.68
★ Swimming Pool Alarm	762	£8.37
AUGUST '10		
★ PIC-Based Flexitimer (double-sided)	763	£12.91
DSP Musicolour – Remote Control Receiver	764	£5.93
★ UV Lightbox – Exposure Controller	765	} set £9.77
– Display/Timer	766	
Ultra LD 200W Power Amplifier (double-sided)	767	£15.52
SEPTEMBER '10		
Ultra-LD 200W Power Amplifier – Power Supply	768	£8.37
Low-Voltage Adjustable Regulator	769	£6.81
Balanced/Unbalanced Converter	770	£7.68
Planet Jupiter Receiver (double-sided)	771	£15.00
OCTOBER '10		
Bridge Adaptor For Stereo Power Amps	770	£7.68
CDI Module For Small Motors	772	£6.63
★ LED Strobe and Tachometer – 1	775	} pair £8.37
– Main Board	776	
– Switch Board		
NOVEMBER '10		
★ Railpower – Main Board	773	} pair £14.83
– Display Board	774	
★ LED Strobe and Tachometer – 2		
– Photo-Interrupter	777	} pair £7.15
– IR Reflect Amp	778	
★ USB Clock with LCD Readout – 1	779	£7.85
Balanced MIC Preamp for PCs and MP3 Players	780	£8.72
DECEMBER '10		
12V Speed Controller or 12V Lamp Dimmer	781	£6.99
★ Digital RF Level & Power Meter		
– Main Board	783	} set £10.81
– Head-end Board	784	
– RF Attenuator Board	785	
JANUARY '11		
★ Multi-Purpose Car Scrolling Display		
– Main Board	786	} pair £12.21
– Display Board	787	
USB-Sensing Mains Power Switch	788	£9.77
★ 433MHz UHF Remote Switch		
– Transmitter	789	} pair £10.12
– Receiver	790	
FEBRUARY '11		
Time Delay Photoflash Trigger	791	£9.72
Tempmaster Mk.2	792	£8.59
MARCH '11		
★ GPS Synchronised Clock	793	£8.02
★ Digital Audio Millivoltmeter	794	£11.34
Theremin	795	£10.53
USB Printer Share Switch	796	£6.80

PROJECT TITLE	ORDER CODE	COST
APRIL '11		
Multi-Message Voice Recorder	797	£7.53
PIR-Triggered Mains Switch	798	£8.00
★ Intelligent Remote-Controlled Dimmer	799	£6.97
MAY '11		
★ 6-Digit GPS Clock	800	£10.69
Simple Voltage Switch For Car Sensors	801	£6.80
The μ Current (double-sided, surface mount)	802	£11.50
★ Digital Audio Oscillator (double-sided)	803	£11.83
JUNE '11		
230V AC 10A Full-Wave Motor Speed Controller	804	£8.91
Precision 10V DC Voltage Reference	805	£6.48
6-Digit GPS Clock Driver (Pt.2)	806	£6.80
Musicolour IRDA Accessory	807	£6.15
JULY '11		
Beam-Break Flash Trigger – IR Source	808	} pair £8.10
– Detector	809	
Metal Locator	810	£7.13
Multi-Function Active Filter	812	£8.34
Active AM Loop Antenna and Amp		
– Antenna/Amp	813	} pair £8.89
– Radio Loop (inc. Varicaps)	814	
AUGUST '11		
Input Attenuator for the Digital Audio Millivoltmeter	811	£6.32
★ SD Card Music & Speech Recorder/Player	815	£11.34
★ Deluxe 3-Chan. UHF Rolling Code Remote Control – Transmitter	816	} pair £10.36
– Receiver	817	

EPE SOFTWARE

★ All software programs for *EPE* Projects marked with a star, and others previously published can be downloaded free from the Library on our website, accessible via our home page at: www.epemag.com

PCB MASTERS

PCB masters for boards published from the March '06 issue onwards can also be downloaded from our website (www.epemag.com); go to the 'Library' section.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code Project Quantity Price

Name

Address

Tel. No.

I enclose payment of £ (cheque/PO in £ sterling only) to:

**Everyday Practical
Electronics**



Card No.

Valid From Expiry Date

Card Security No. Maestro Issue No.

Signature

Note: You can also order PCBs by phone, Fax or Email or via the Shop on our website on a secure server:

<http://www.epemag.com>

CLASSIFIED

ADVERTISEMENTS

If you want your advertisements to be seen by the largest readership at the most economical price our classified page offers excellent value. The rate for semi-display space is £10 (+VAT) per centimetre high, with a minimum height of 2.5cm. All semi-display adverts have a width of 5.5cm. The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, 113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU. Phone: 01202 880299. Fax: 01202 843233. Email: epeads@wimborne.co.uk. For rates and information on display and classified advertising please contact our Advertisement Manager, Stewart Kearn as above.

Everyday Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last twenty-five years.

Robot Bits
Robots, Arduino & more!
www.RobotBits.co.uk
0845 5 191 282

**LOOKING FOR
A MAINS TRANSFORMER**
Visit Section 16C
www.partridgeelectronics.co.uk

BOWOOD ELECTRONICS LTD
Suppliers of Electronic Components
Place a secure order on our website or call our sales line
All major credit cards accepted
Web: www.bowood-electronics.co.uk
Unit 10, Boythorpe Business Park, Dock Walk, Chesterfield,
Derbyshire S40 2QR. Sales: 01246 200222
Send 60p stamp for catalogue

**BTEC ELECTRONICS
TECHNICIAN TRAINING**
**NATIONAL ELECTRONICS
VCE ADVANCED ICT
HNC AND HND ELECTRONICS
FOUNDATION DEGREES
NVQ ENGINEERING AND IT
DESIGN AND TECHNOLOGY**
LONDON ELECTRONICS COLLEGE
20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: (020) 7373 8721
www.lec.org.uk

CANTERBURY WINDINGS
UK manufacturer of toroidal transformers
(10VA to 3kVA)
All transformers made to order. No design fees.
No minimum order.
www.canterburywindings.co.uk
01227 450810

MISCELLANEOUS
VALVES AND ALLIED COMPONENTS IN STOCK. Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

Spinvent
Invent with the
Propeller 8-core
32-bit microcontroller
www.spinvent.co.uk
01603 611 216

**ADVERTISE HERE
CALL
STEWART KEARN
ON 01202 880299**
STEWART.KEARN@WIMBORNE.CO.UK

If you would like to advertise on the Classified page then please call:

Stewart Kearn on
01202 880299

or email stewart.kearn@wimborne.co.uk

ADVERTISERS INDEX

CRICKLEWOOD ELECTRONICS	67	QUASAR ELECTRONICS	2/3
DISPLAY ELECTRONICS	80	SHERWOOD ELECTRONICS	67
ESR ELECTRONIC COMPONENTS	6	STEWART OF READING	Cover (iii)
JAYCAR ELECTRONICS	4/5	TECHNOBOTS	67
JPG ELECTRONICS	80		
L-TEK POSCOPE	17		
LABCENTER	Cover (iv)		
LASER BUSINESS SYSTEMS	67		
MATRIX MULTIMEDIA	58		
MICROCHIP	Cover (ii)		
MIKROELEKTRONIKA	55		
PEAK ELECTRONIC DESIGN	Cover (iii)		
PICO TECHNOLOGY	66		

ADVERTISEMENT OFFICES:

113 LYNWOOD DRIVE, MERLEY, WIMBORNE,
DORSET BH21 1UU

PHONE: 01202 880299 FAX: 01202 843233

EMAIL: epeads@wimborne.co.uk WEB: www.epemag.com

For editorial address and phone numbers see page 7

Next Month

Build a high-quality stereo DAC for superb sound from your DVD player

Do you listen to CDs via your DVD player? Is your listening pleasure suffering from the DVD player's average sound quality? Worse still, do you get buzz and hum problems when hooked up to your hi-fi? If so, you need this high-quality stereo digital-to-analogue converter (DAC) – it will transform your listening experience to first-class sound and zero hum.

Using a wideband O2 sensor in your car – Part 1

This wideband controller is designed to be used with a Bosch Wideband LSU4.2 oxygen sensor and our wideband sensor display to accurately measure air/fuel ratios over a wide range – from rich to lean. Use it for precise engine tuning!

Deluxe 3-channel UHF Rolling Code Remote Control – Part 2

In this, the August issue we introduced our new high security remote control and completed both the receiver/relay driver and transmitter. Next month, we'll put it all together and get the two parts talking to each other – *securely!*

Recycle It!

Six fun uses for salvaged parts – electronic fun for free!

Teach-In 2011 – Part 11

You can't keep a good idea down, and Mike and Richard Tooley have provided us with one more instalment of *Teach-In 2011!* Next month, we'll round off the series with some fun revision and a selection of electronic projects that you can build and test using Circuit Wizard.

SEPTEMBER '11 ISSUE ON SALE 11 AUGUST

Content may be subject to change



Europe's Largest Surplus Store

20,000,000 Items on line NOW !
New items added daily

Established for over 25 years, UK company Display Electronics prides itself on offering a massive range of electronic and associated electro-mechanical equipment and parts to the Hobbyist, Educational and Industrial user. Many current and obsolete hard to get parts are available from our vast stocks, which include:

- ◆ 6,000,000 Semiconductors
- ◆ 5,000 Power Supplies
- ◆ 25,000 Electric Motors
- ◆ 10,000 Connectors
- ◆ 100,000 Relays & Contactors
- ◆ 2000 Rack Cabinets & Accessories
- ◆ 4000 Items of Test Equipment
- ◆ 5000 Hard Disk Drives

We Ship Worldwide

Surplus Wanted

www.distel.co.uk

Display Electronics
29 / 35 Osborne Road
Thornton Heath
Surrey UK CR7 8PD

Telephone
[44] 020 8653 3333
Fax [44] 020 8653 8888

Rechargeable Batteries With Solder Tags

NIMH

AA 2000mAh	£2.82
C 4Ah	£4.70
D 9Ah	£7.60
PP3 150mAh	£4.95

NICAD

AA 650mAh	£1.41
C 2.5Ah	£3.60
D 4Ah	£4.95

Instrument case with edge connector and screw terminals

Size 112mm x 52mm x 105mm tall

This box consists of a cream base with a PCB slot, a cover plate to protect your circuit, a black lid with a 12 way edge connector and 12 screw terminals built in (8mm pitch) and 2 screws to hold the lid on. The cream bases have minor marks from dust and handling price £2.00 + VAT (=£2.35) for a sample or £44.00+VAT (=£51.70) for a box of 44.



866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + VAT = **£8.77**



Please add £1.66 + VAT = £1.95 postage & packing per order

JPG Electronics

Shaws Row, Old Road, Chesterfield, S40 2RB.

Tel 01246 211202 Fax 01246 550959

www.JPGElectronics.com

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday



PRE-PRODUCTION CHECK

Board Edge Defined - **CHECK**

All Components Placed - **CHECK**

All Connections Routed - **CHECK**

Power Planes Generated - **CHECK**

No Design Rule Violations - **CHECK**

PROTEUS 7

Design with Confidence:

The latest version of the Proteus PCB Design Software provides a multi-stage Pre-Production Check which will detect and prevent a variety of common mistakes prior to your boards being sent for manufacture.

PROTEUS DESIGN SUITE Features:

- Hardware Accelerated Performance.
- Unique Thru-View™ Board Transparency.
- Over 35k Schematic & PCB library parts.
- Integrated Shape Based Auto-router.
- Flexible Design Rule Management.
- Polygonal and Split Power Plane Support.
- Board Autoplacement & Gateswap Optimiser.
- Direct CAD/CAM, ODB++, IDF & PDF Output.
- Integrated 3D Viewer with 3DS and DXF export.
- Mixed Mode SPICE Simulation Engine.
- Co-Simulation of PIC, AVR, 8051 and ARM7.
- Direct Technical Support at no additional cost.

All levels of the **Proteus Design Suite** include a world class, fully integrated shape-based autorouter at no additional cost - prices start from just £150 exc. VAT & delivery

labcenter  www.labcenter.com
Electronics

Labcenter Electronics Ltd. 53-55 Main Street, Grassington, North Yorks. BD23 5AA.
Registered in England 4692454 Tel: +44 (0)1756 753440, Email: info@labcenter.com

Visit our website or
phone 01756 753440
for more details



**Designed in the UK,
Made in the UK.**

Tel. 01298 70012
www.peakelec.co.uk
sales@peakelec.co.uk

West Road House
West Road
Buxton
Derbyshire
SK17 6HF

PEAK®
electronic design ltd

Atlas DCA - Semiconductor Analyser with Carry Case!



Order Code
ATPK1



The famous Peak Atlas and even better value in this carry case!

Fitted with sturdy universal premium gold probes. Just connect any way round to identify the type of part, pinout and lots of parameters.

Supplied with battery, comprehensive user guide and padded hard carry case (choose either blue or black).

Supports bipolar transistors, darlingtons, MOSFETs, diodes, LEDs and more...

£42.50 + VAT

=£51 inc VAT. Limited Offer.

Please add £3 for UK P&P

Case available in black or blue.

www.stewart-of-reading.co.uk

Check out our website, 1,000's of items in stock.



HP8563E SPECTRUM ANALYSER
9KHZ - 26.5GHZ Synthesised..... £20A



HP33120A FUNCTION GENERATOR
100 MicroHZ - 15MHZ
Unused Boxed £595
Used, No Moulding, No Handle £395



MARCONI 2955 RADIO
COMMUNICATION TEST SET
ONLY £625
Also available Marconi 2955A & 2955B



ENI 3200L RF POWER AMPLIFIER
250KHZ-150MHZ 200W 55db

AGILENT E4402B Spectrum Analyser
100KHz - 3GHz with Option 1DN Tracking
Gen; 1 DR Narrow Res; A4H GPIB,
UKB.....£5800
HP 35670A FFT Dynamic Signal Analyser
2 Channel. Unused in original box.....£4000
AGILENT 83752B Synthesised Sweeper
0.01-20GHZ.....£6000
HP83711B Synthesised 1-20GHZ with
Opt IEI Attenuator.....£5000
AGILENT/HP E4431B Signal Generator
250KHZ-20GHZ Digital Modulation.....£2750
MARCONI 2024 Signal Generator 9KHZ-
2.4GHZ Opt 04.....£1250
MARCONI/IFR 2030 Signal Generator
10KHZ-1.35 GHz.....£395
MARCONI 2022E Synthesised AM/FM
Signal Generator 10KHZ-1.01GHZ.....£500
HP8566A Spectrum Analyser 100KHZ-
22GHZ.....£1950
HP8568A Spectrum Analyser 100KHZ-
1500MHZ.....£1250
AVCOM PSA-37D Spectrum Analyser
1MHZ-4.2GHZ.....£-
IFR 1200S Service Communication
Monitor.....£1500
HP6624A Power Supply 0-20V 0-2A
Twice, 0-7V 0-5A; 0-50V 0.8A
Special price.....350
AVO/MEGGAR FT6/12 AC/DC
breakdown tester.....£-
MARCONI/IFR AEROFLEX 2025 Signal
Gen 9KHZ-2.51GHZ Opt 04 High Stab
Opt 11 High Power etc As New.....£2500
SOLARTRON 1250 Frequency Response
Analyser 10uHZ-85KHZ.....£995
HP3324A Synthesised Function
Generator 21MHz.....£500
HP41800A Active Probe 5KHZ-500MHZ.....£750
ANRITSU MS2601A Spectrum Analyser
10KHZ-2.2GHZ 50ohm.....£750



AGILENT E4421B 250KHZ-3GHZ
Signal Generator £2500

HP53131A Universal Counter Opt 001
Unused Boxed 3GHZ.....£850
Unused Boxed 225MHZ.....£595
Used 225MHZ.....£495
HP8569B Spectrum Analyser 0.01-
22GHZ.....£1000
HP54616C Oscilloscope Dual Trace
500MHZ 2GS/S Colour.....£1250
QUART LOCK 10A-R Rubidium
Frequency Standard.....£1000
PENDULUM CNT90 Timer/Counter
/Analyser 20GHZ.....£1950
ADVANTEK R3465 Spectrum
Analyser 9KHZ-8GHZ.....£-
HP Programmable Attenuators £300
each
33320H DC-18GHZ 11db
33321G DC-18GHZ 70db
Many others available
AGILENT E3610A Power Supply 0-8v
0-3A/0-15v 0-2A Unused
AGILENT E3611A Power Supply 0-20V
0-1.5A/0-35V 0-0.85V Unused
CIRRUS CRL254 Sound Level Meter
with Calibrator.....£95
CEL328 Digital Sound Level Meter with
CEL284/2 Acoustical Calibrator.....
CEL 269 Digital Sound Level Meter with
CEL282 Acoustical Calibrator

FLUKE SCOPEMETERS
90B Series II 2Ch 100MHZ 5GS/G from
£325
97 2Ch 50MHZ 25MS/S from £225

STEWART OF READING

17A King Street, Mortimer,
Near Reading RG7 3RS
Telephone: 0118 933 1111
Fax: 0118 933 2375
9am - 5pm Monday - Friday

Used Equipment - GUARANTEED
Prices plus Carriage and VAT

Please check availability before
ordering or CALLING IN



MARCONI 2945 RADIO COMMUNICATION TEST

SET with....

Opt 01 - 600 ohm Matching Unit
Opt 03 - High Stability OCXO
Opt 06 - Memory Card Drive with Real
Time Clock Opt 08 - SSB Demodulator
Opt 21 Demodulation Filters
Opt 22 POCSAG Decode
Only £3,000



HP 8569B
Spectrum Analyser 0.01-22GHZ
£995



HP6269B Power Supply
0-40V 0-50A £400

AMPLIFIER RESEARCH
POWER AMPLIFIER 1000LAMB £20A